

EE251

Lectures


Circuit Analysis

Section 04

Ohm's Law

- A current through a resistor is proportional to the voltage across its terminals
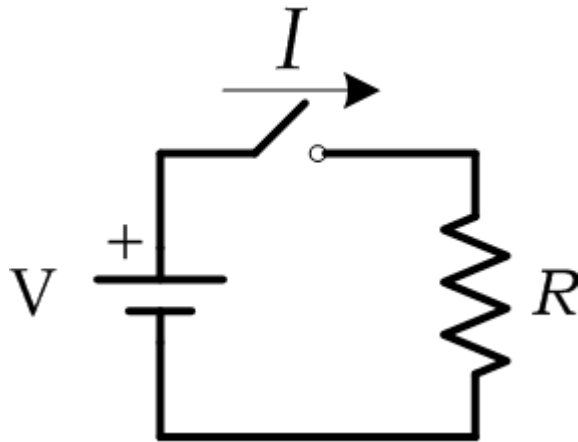
$$V = I \cdot R \quad \text{or} \quad I = \frac{V}{R}$$




$$R \rightarrow \infty \quad I = 0$$

$$R \rightarrow 0 \quad I = \infty$$




Short a 1.5 battery, what will happen?

Internal Resistance

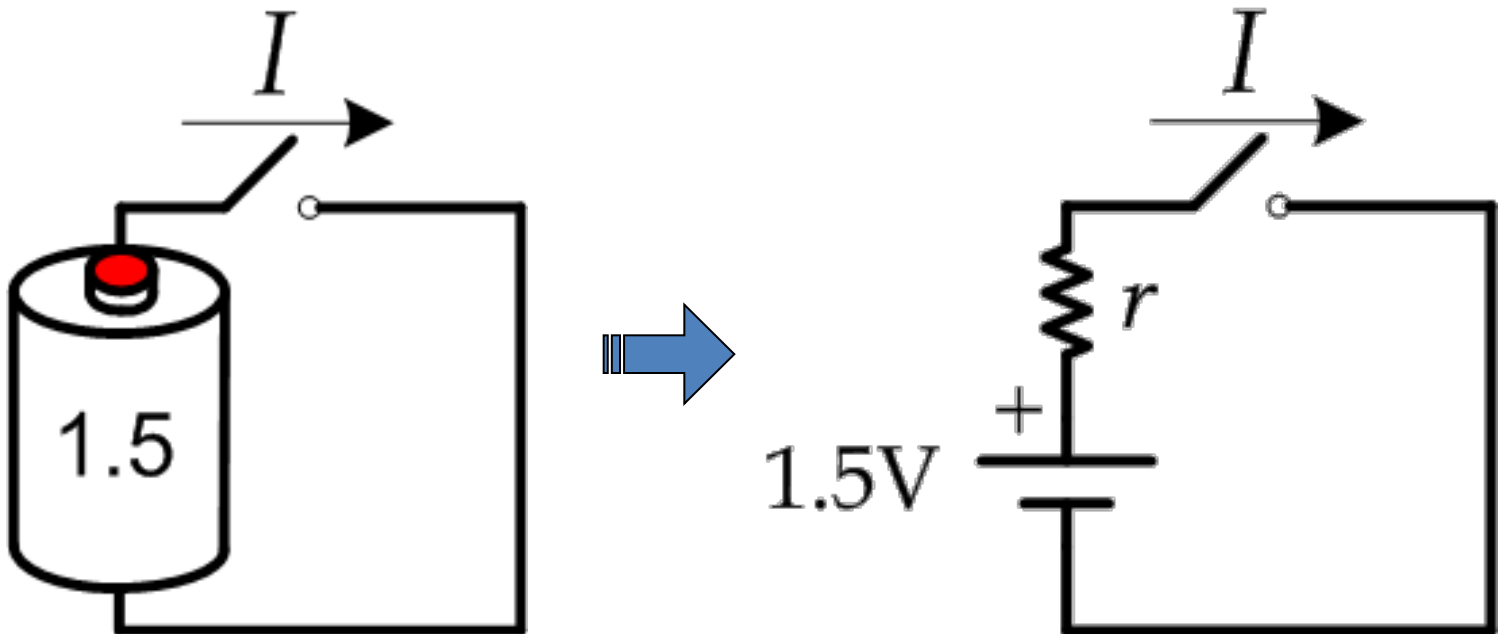- If you short a 1.5V battery, how much current will pass?





Overloading

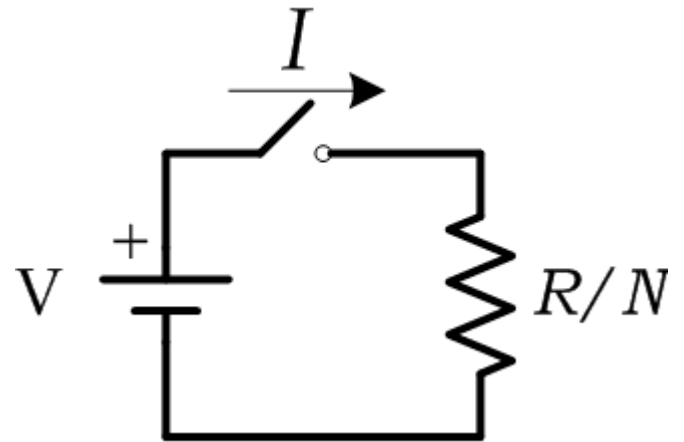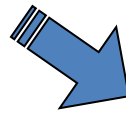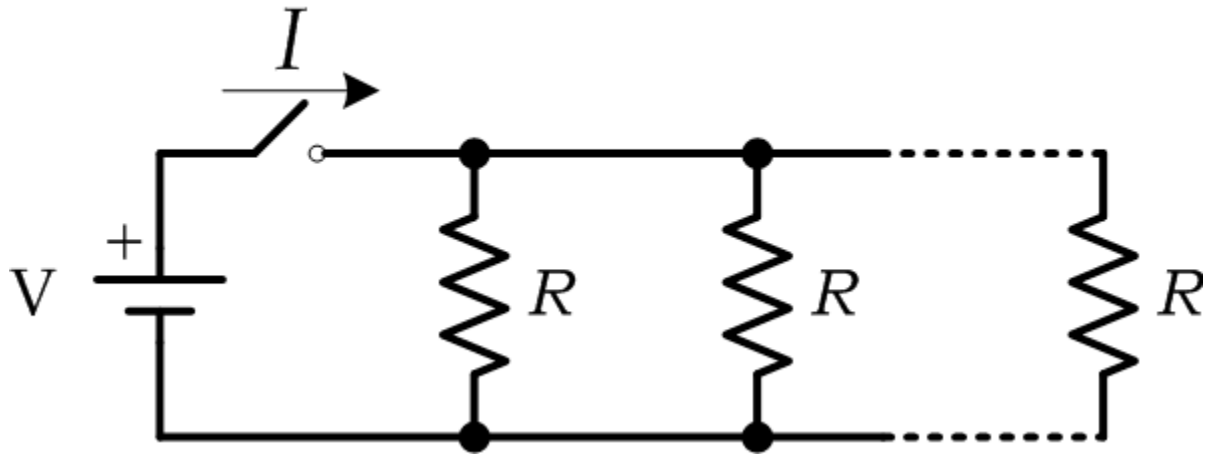

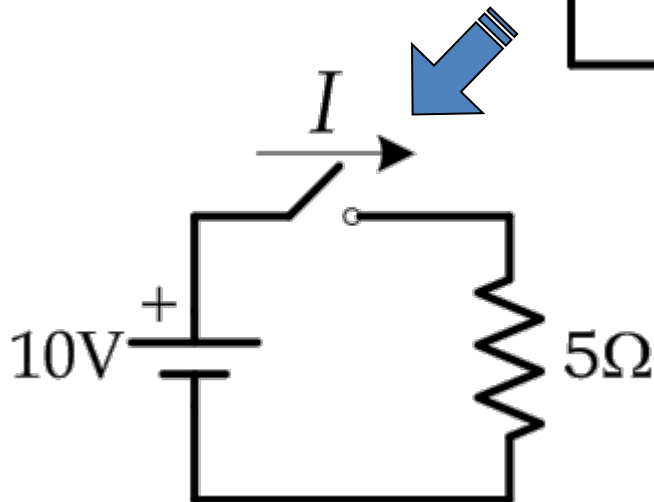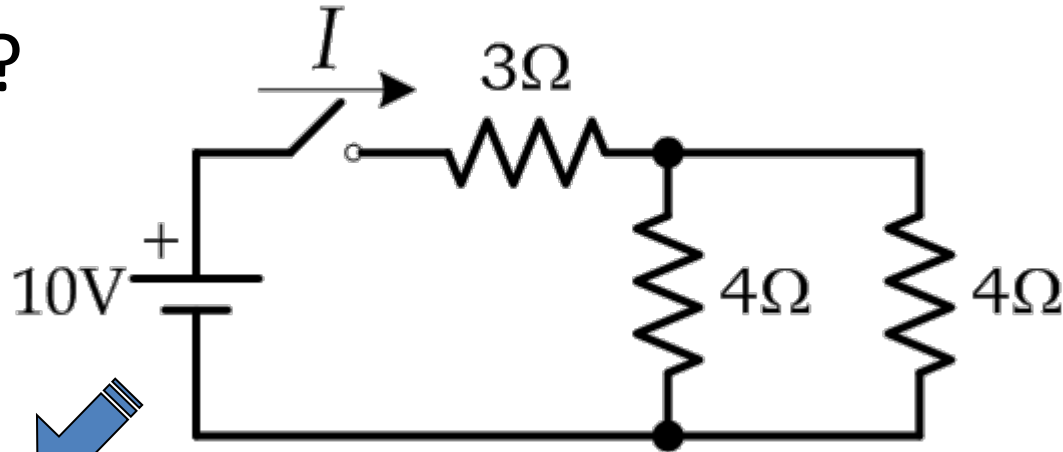Question


- What is the total current drawn from the source?



$$R_L = 4 // 4 + 3 = 2 + 3 = 5\Omega$$

$$I = \frac{V}{R} = \frac{10}{5} = 2A$$


Voltage Divider

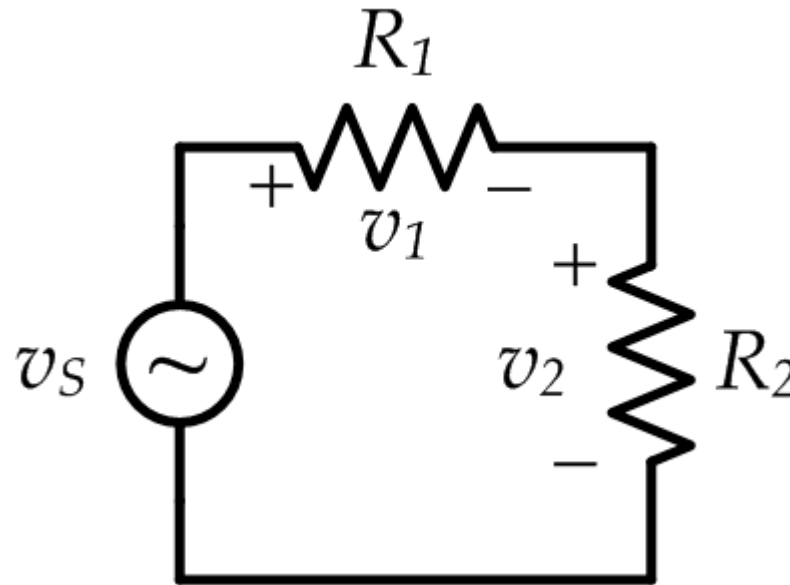

$$v_1 = v_s \frac{R_1}{R_1 + R_2}$$

$$v_2 = v_s \frac{R_2}{R_1 + R_2}$$


Current Divider

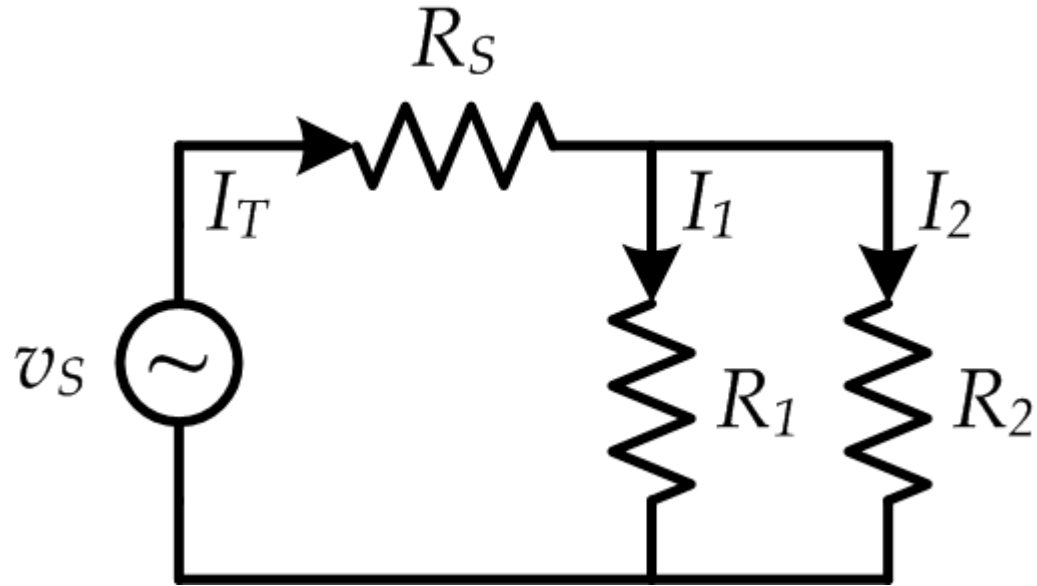

$$I_1 = I_T \frac{R_2}{R_1 + R_2}$$


$$I_2 = I_T \frac{R_1}{R_1 + R_2}$$

Multiple Loads

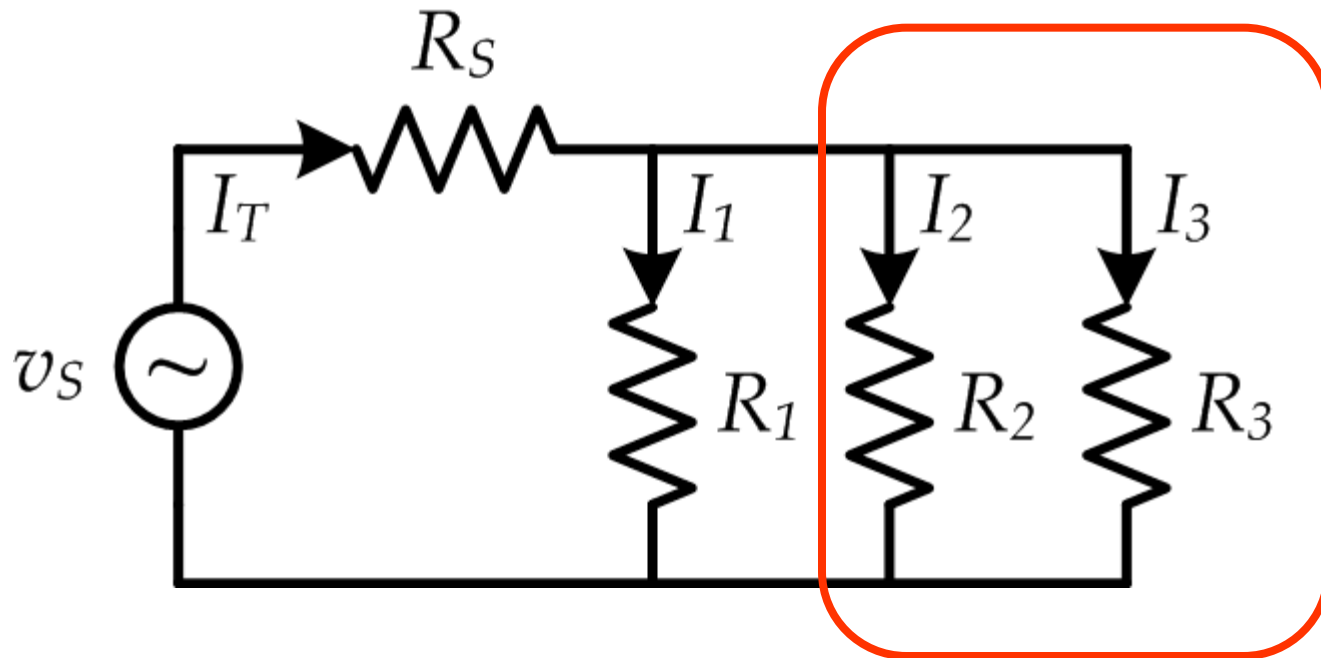

Combine Parallel Loads


Multiple Loads

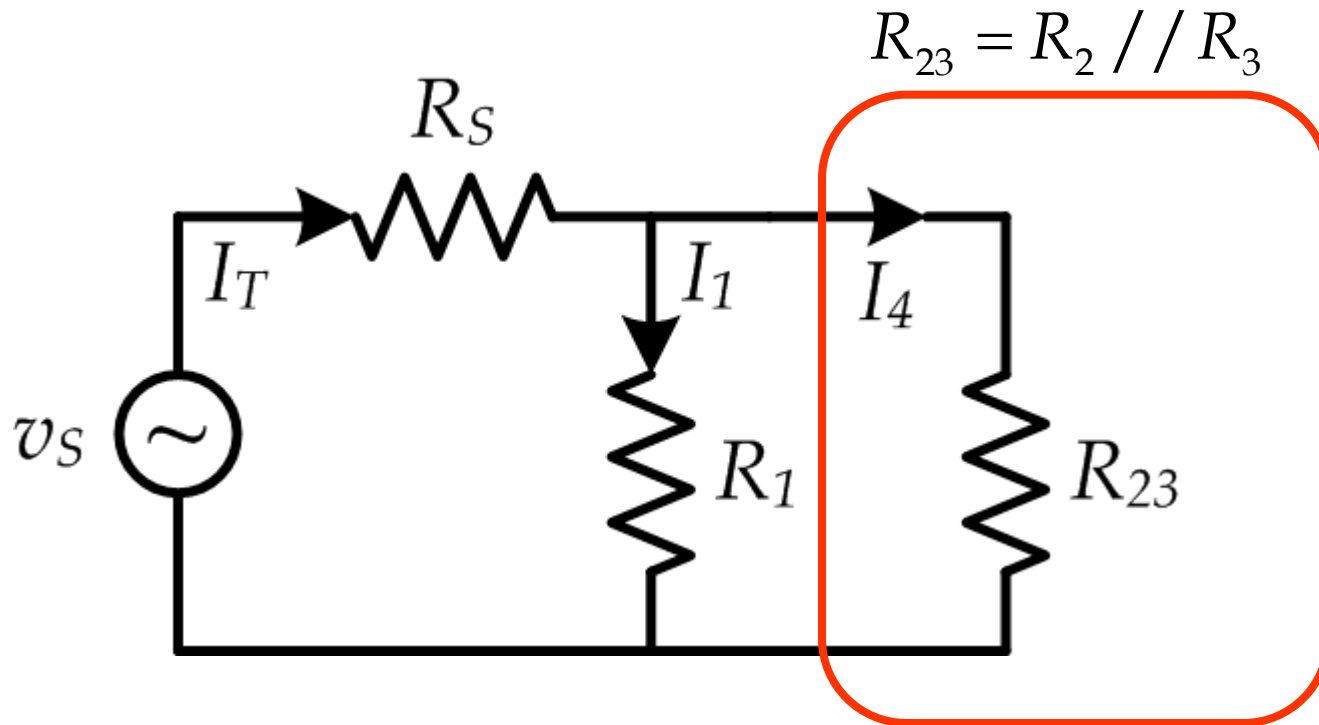

$$I_1 = I_T \frac{R_{23}}{R_1 + R_{23}}$$

$$I_4 = I_T \frac{R_1}{R_1 + R_{23}}$$


Multiple Loads

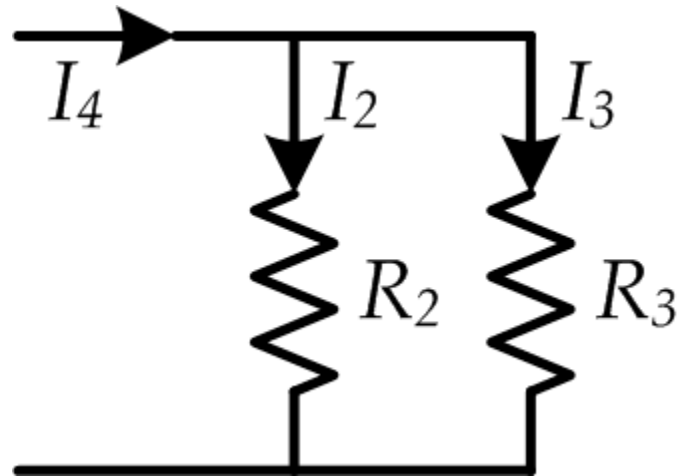

$$I_2 = I_4 \frac{R_3}{R_2 + R_3}$$

$$I_3 = I_4 \frac{R_2}{R_2 + R_3}$$

Current Divider

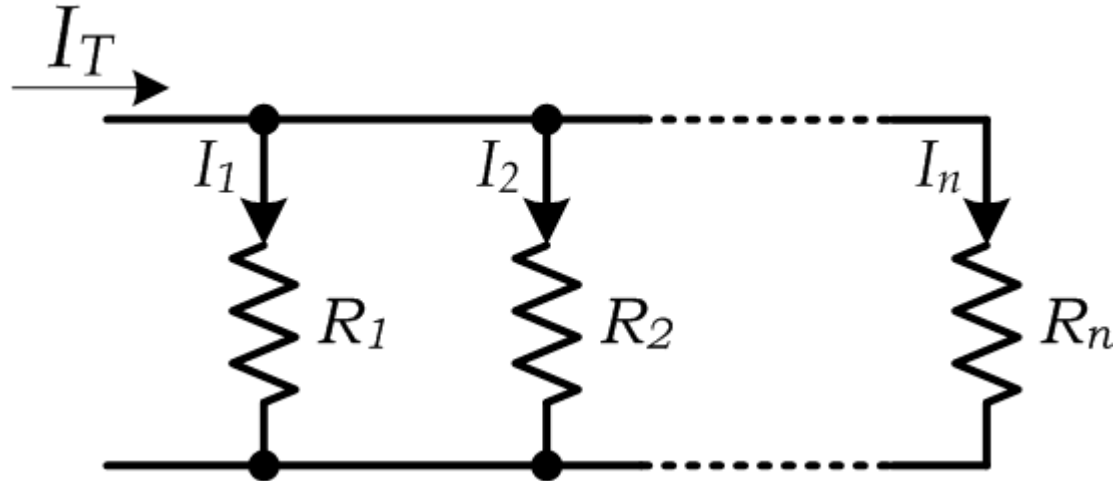


$$R_p = R_1 // R_2 // \cdots // R_n$$

$$I_k = I_T \frac{R_p}{R_k}$$


Process Check

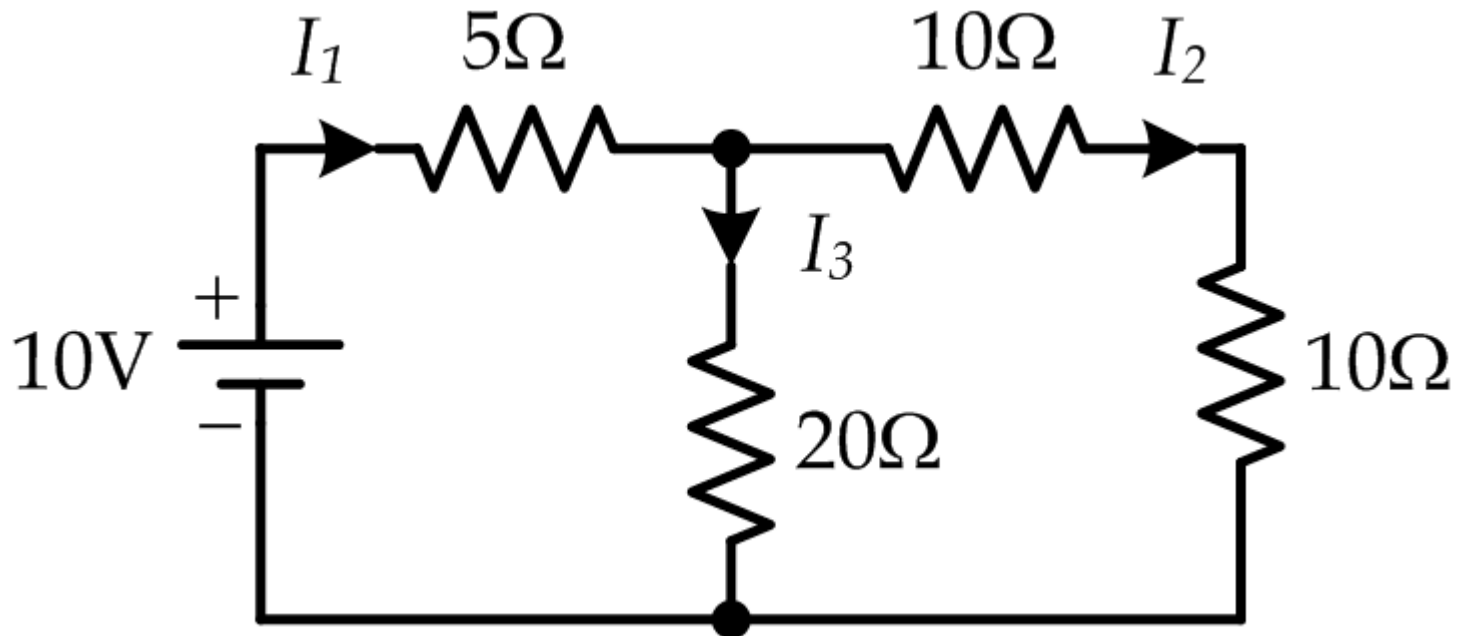- Calculate all currents in the circuit..
 - What is your plan?!




Multiple Sources

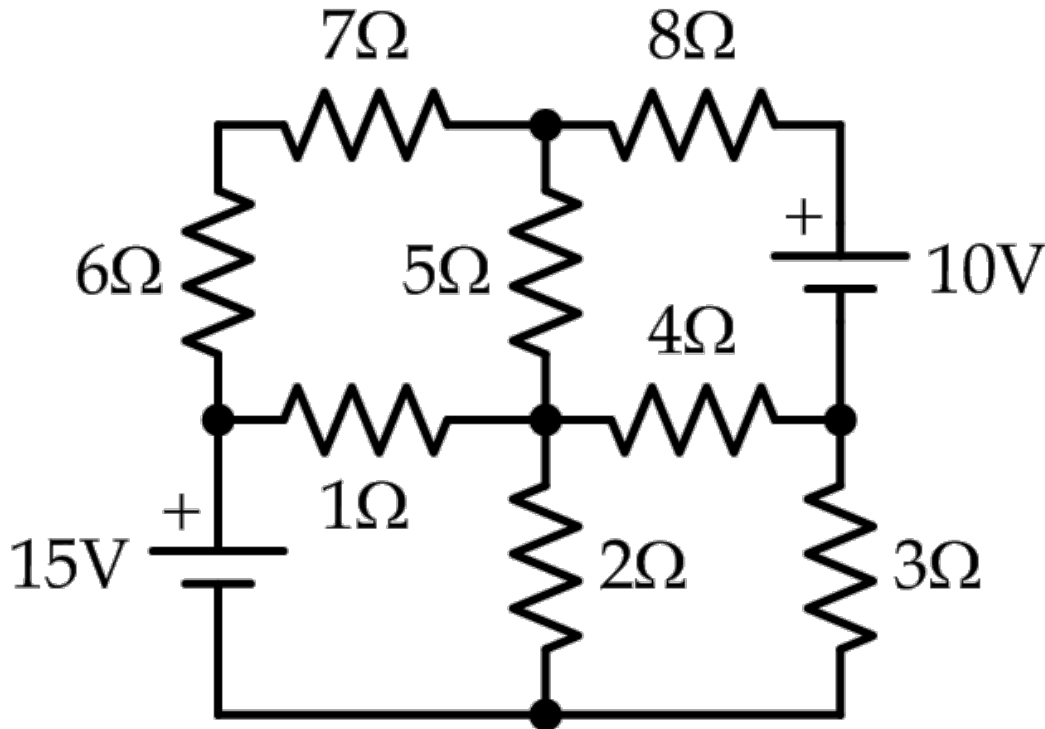- What if more than one source in the circuit?
 - How to solve for all currents?




Nodes and Loops

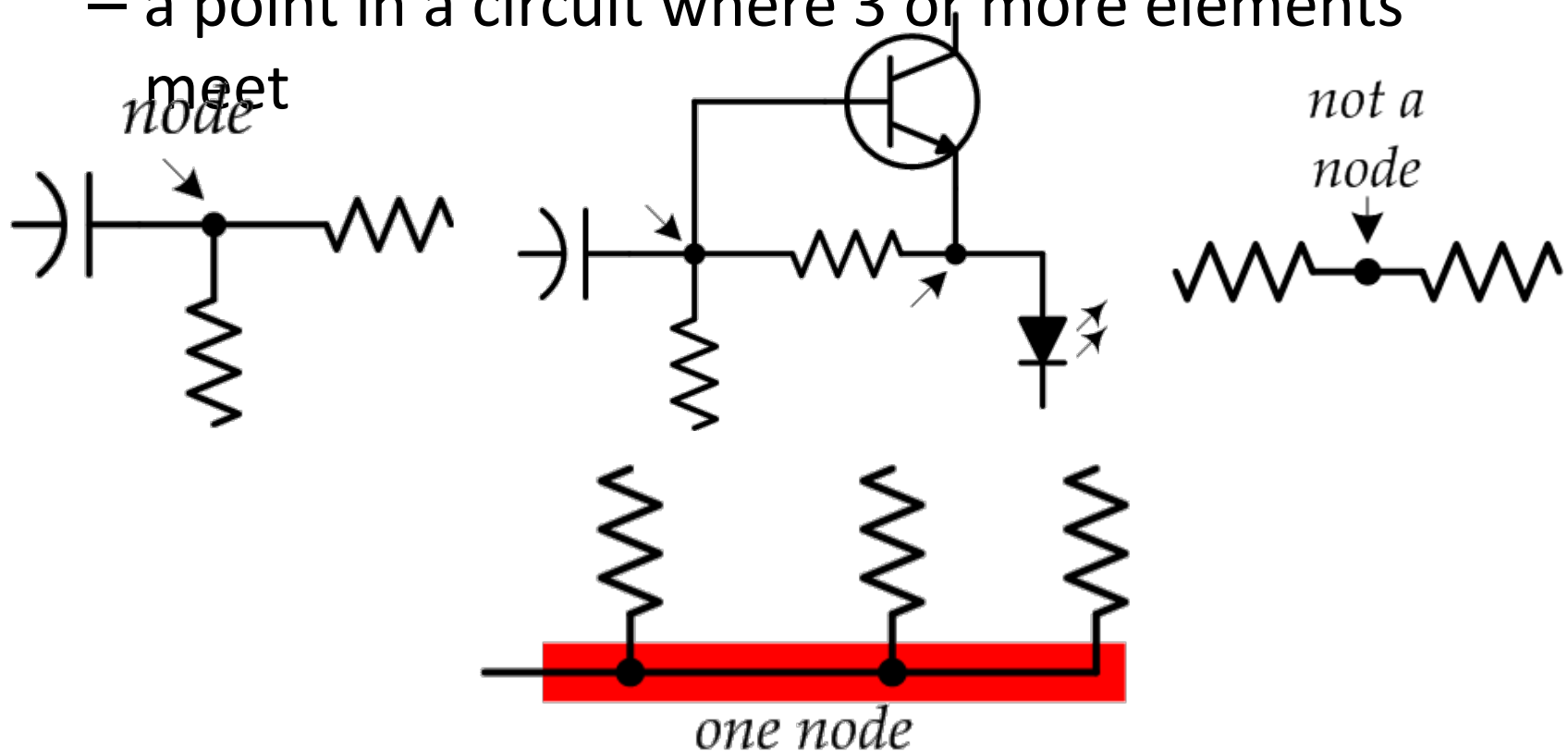- A Node
 - a point in a circuit where 3 or more elements meet





Nodes and Loops

- How many nodes in the circuits?



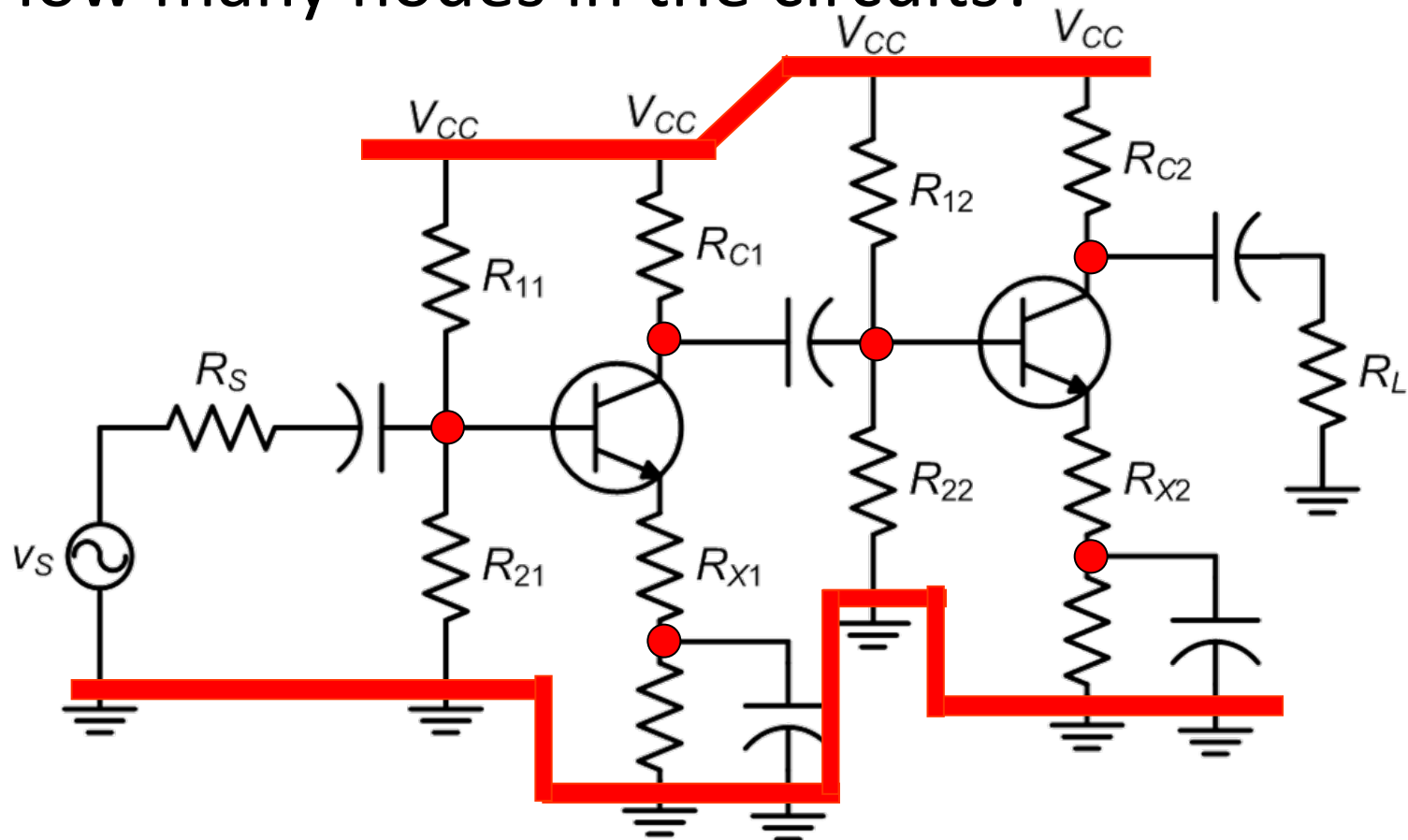


Nodes and Loops

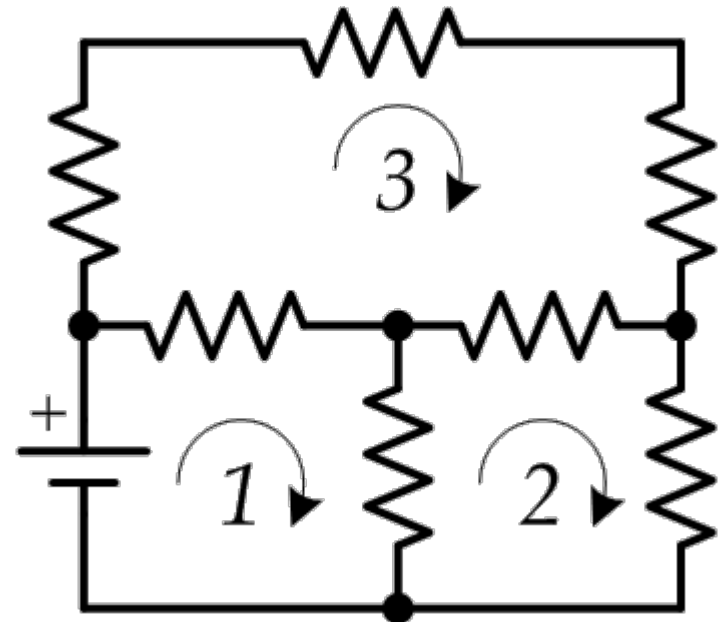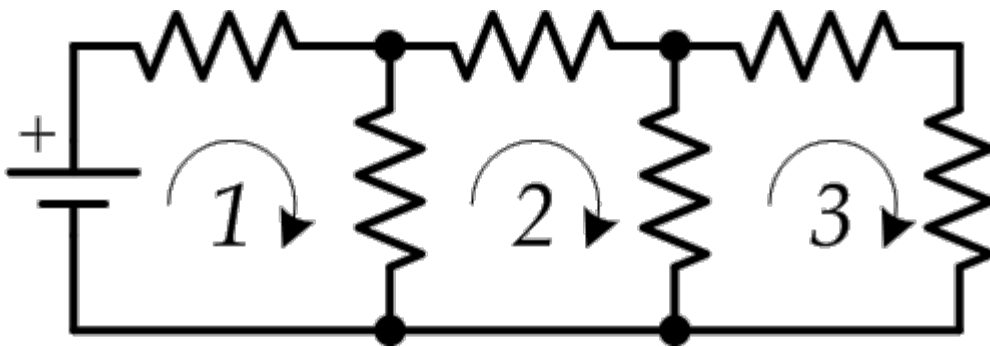- A Loop:
 - a closed ring in a planer circuit





Planer Circuit

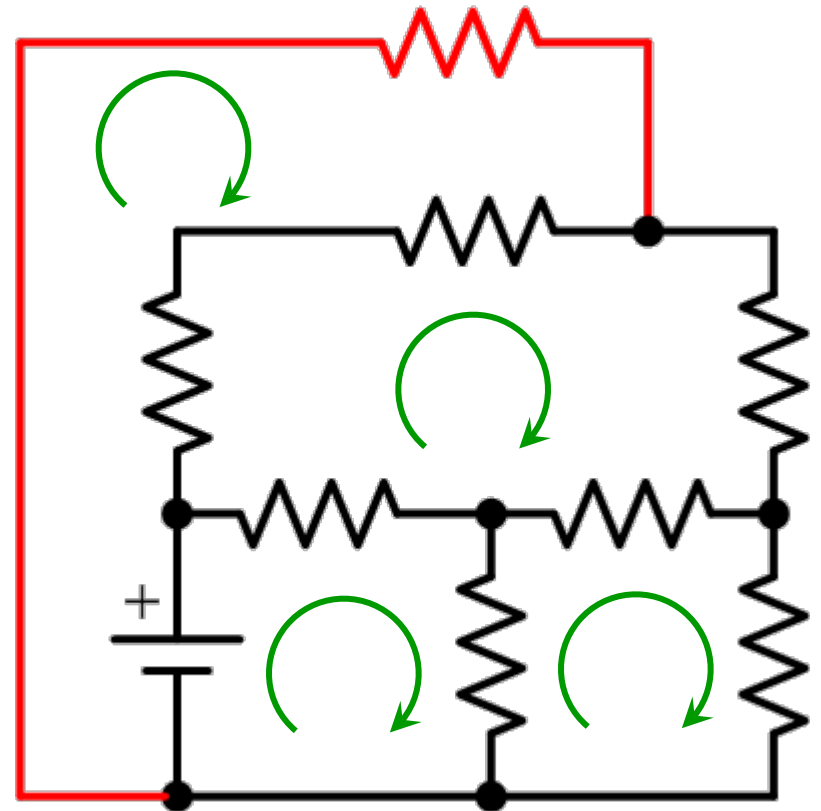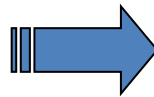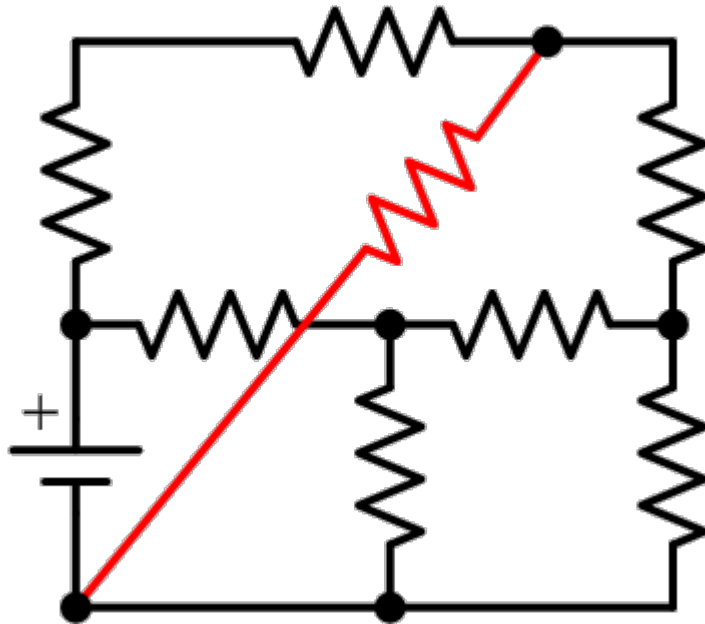

Voltage Drop

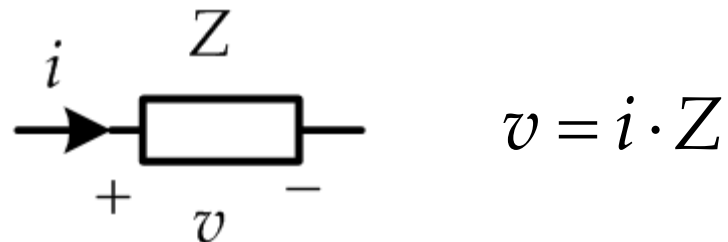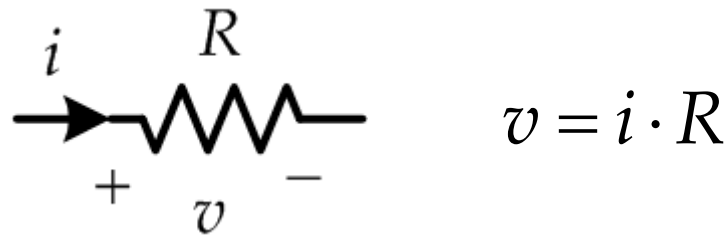- A current passing through a load generates a voltage drop




KVL and KCL

- *(nodes, loops, planner circuit, voltage drop) then what?*
- To solve for all currents and volts in a circuit:
 - KVL: Kirchhoff's Voltage Law
 - the sum of voltage drops in a loop is zero
 - KCL: Kirchhoff's Current Law
 - the sum of currents into a node is zero


Circuit Analysis

1. count nodes minus one (possible ground)
2. mark a current for each branch
3. write KCL equations
4. count loops
5. write KVL equations

Example

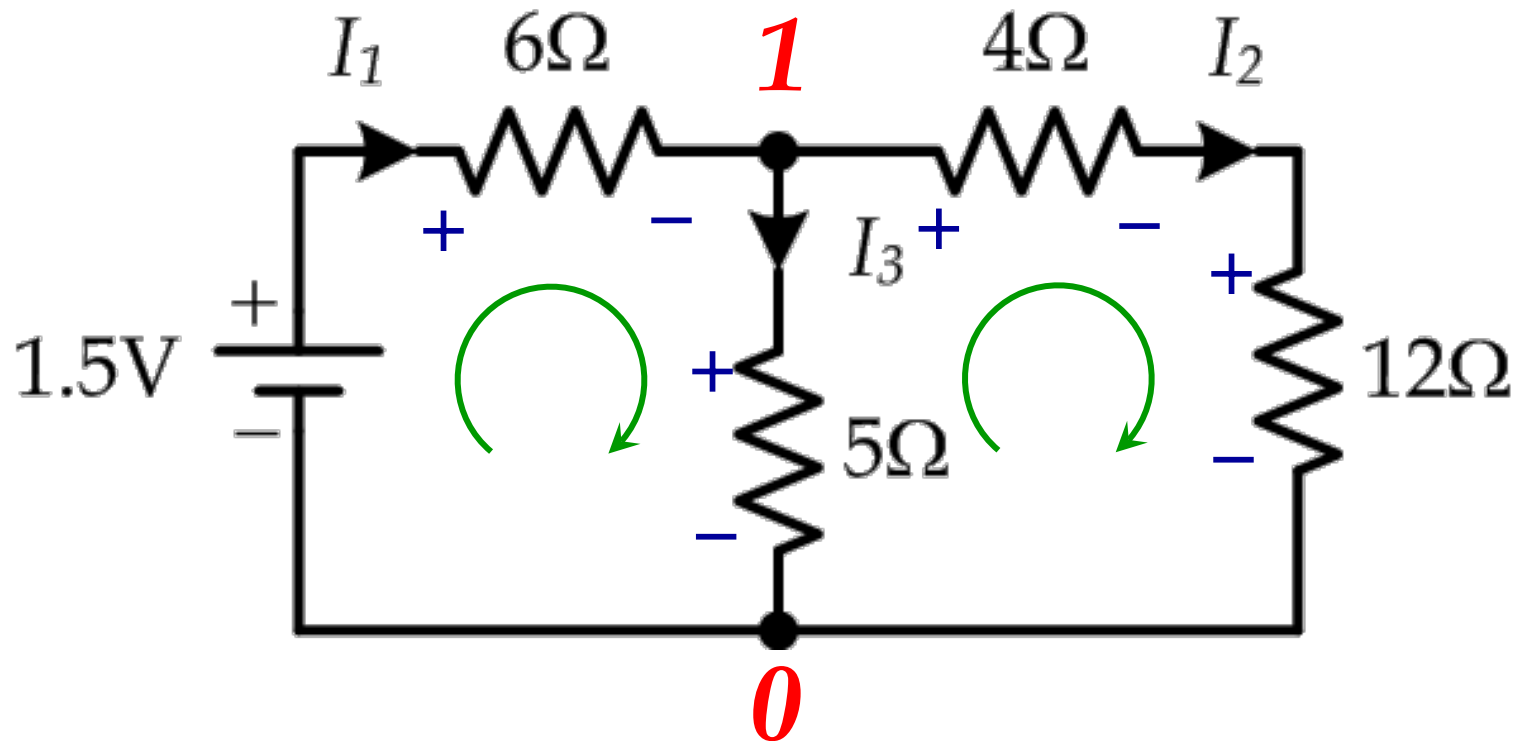


Example

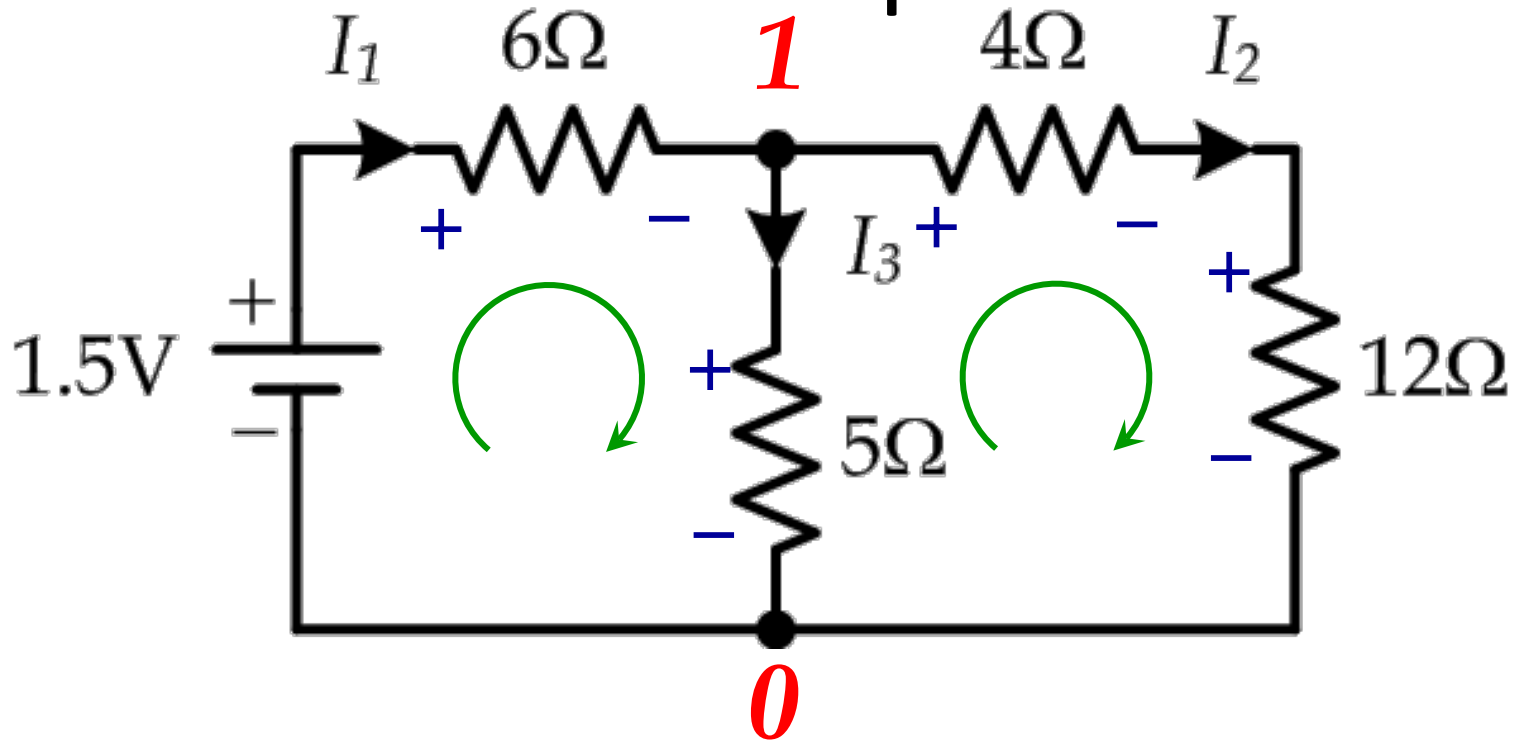

$$KCL: I_1 = I_2 + I_3$$


$$KVL: -1.5 + 6I_1 + 5I_3 = 0$$

$$-5I_3 + 4I_2 + 12I_2 = 0$$

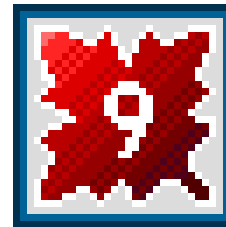

$$\begin{aligned} I_1 &= 152.9 \text{ mA} \\ \Rightarrow I_2 &= 36.4 \text{ mA} \\ I_3 &= 116.5 \text{ mA} \end{aligned}$$

Example

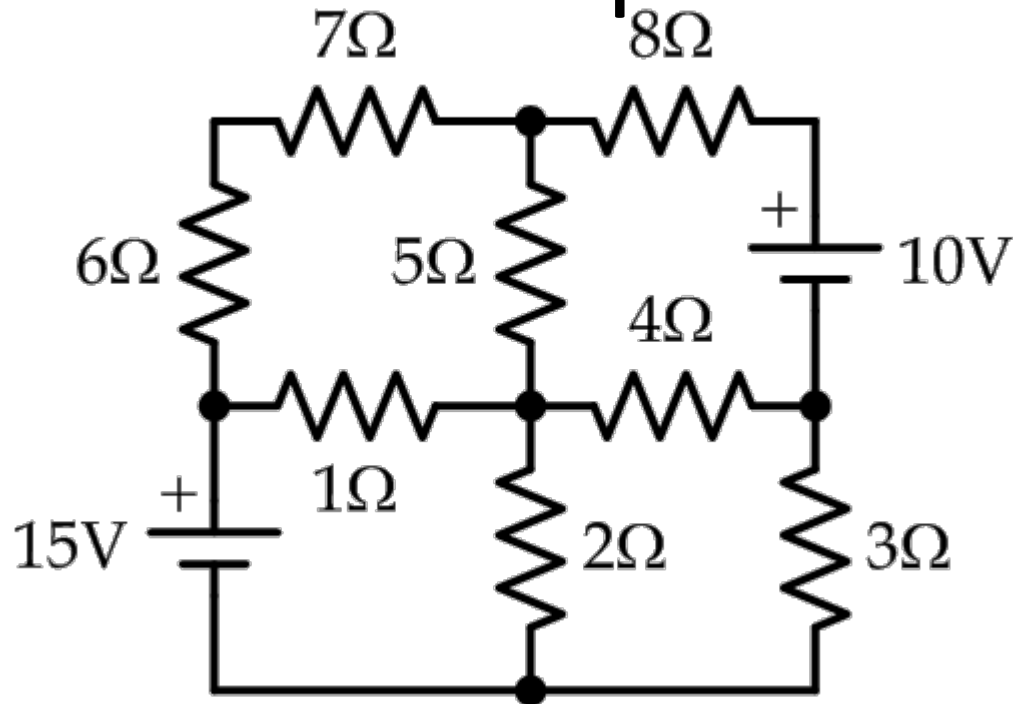


8 branches \rightarrow 8 currents $I_1..I_8 \rightarrow$ 8 equations

4 nodes \rightarrow 4 eqs

4 loops \rightarrow 4 eqs

Impedance

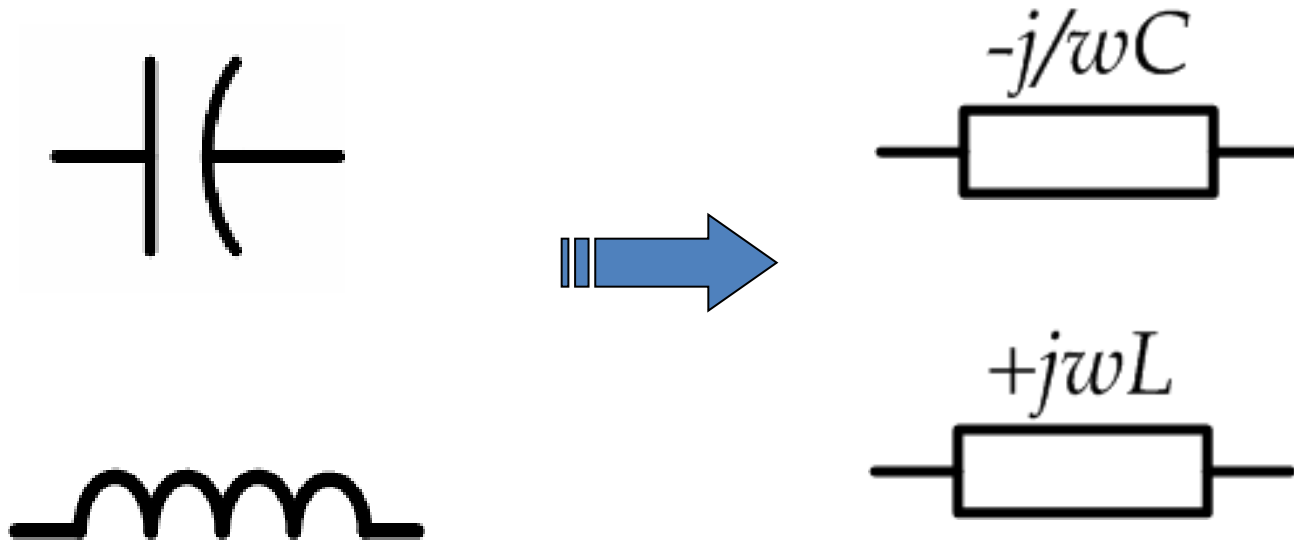- treat all passive components as resistors
 - but with *complex* resistances



Impedance

- What is the impedance of a 10μF capacitor when operated at 60Hz?

$$Z_C = -\frac{j}{\omega C} = -\frac{j}{2\pi \times 60 \times 10 \times 10^{-6}} = -j265.25\Omega$$


- What is the impedance of a 2mH inductor when operated at 60Hz?

$$Z_L = j\omega L = j2\pi \times 60 \times 2 \times 10^{-3} = +j0.754\Omega$$

Laplace Domain

- When
 - Mixing AC and DC sources
 - Multiple different frequencies
- use Laplace instead of Fourier
 - $j\omega \rightarrow s$
 - *Initial conditions*


Example

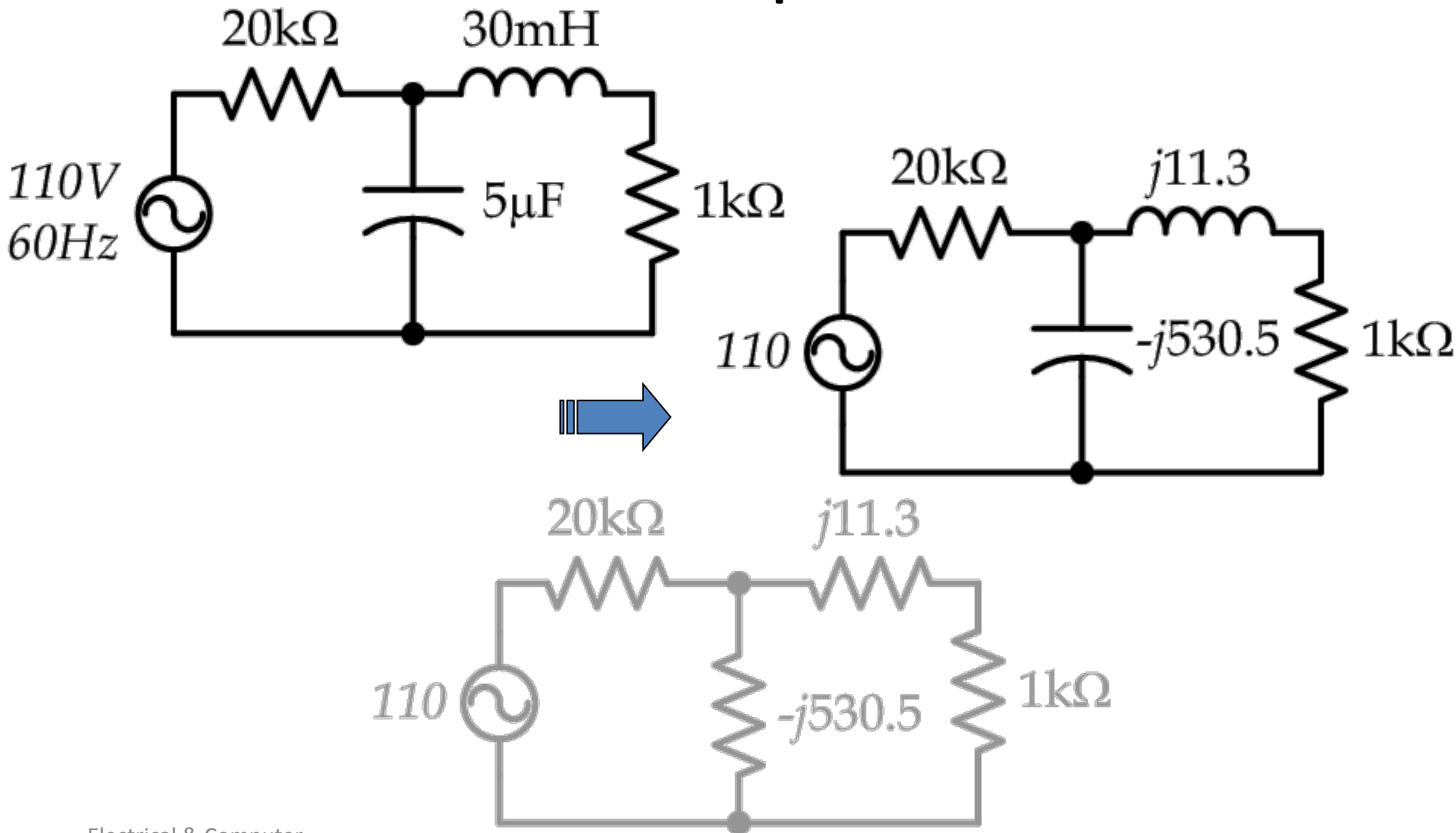

Current Source


- Voltage Source

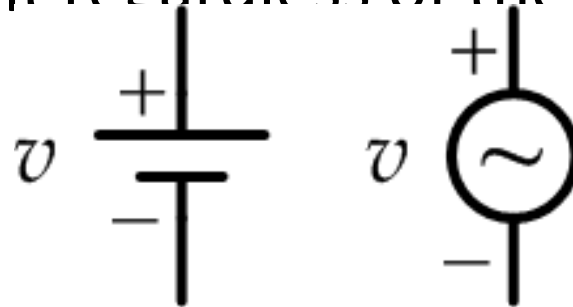- Generates **constant** volt regardless of the load




- Current Source

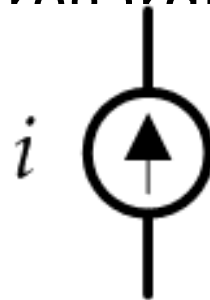- Generates **constant** current regardless of the load




W A T E R

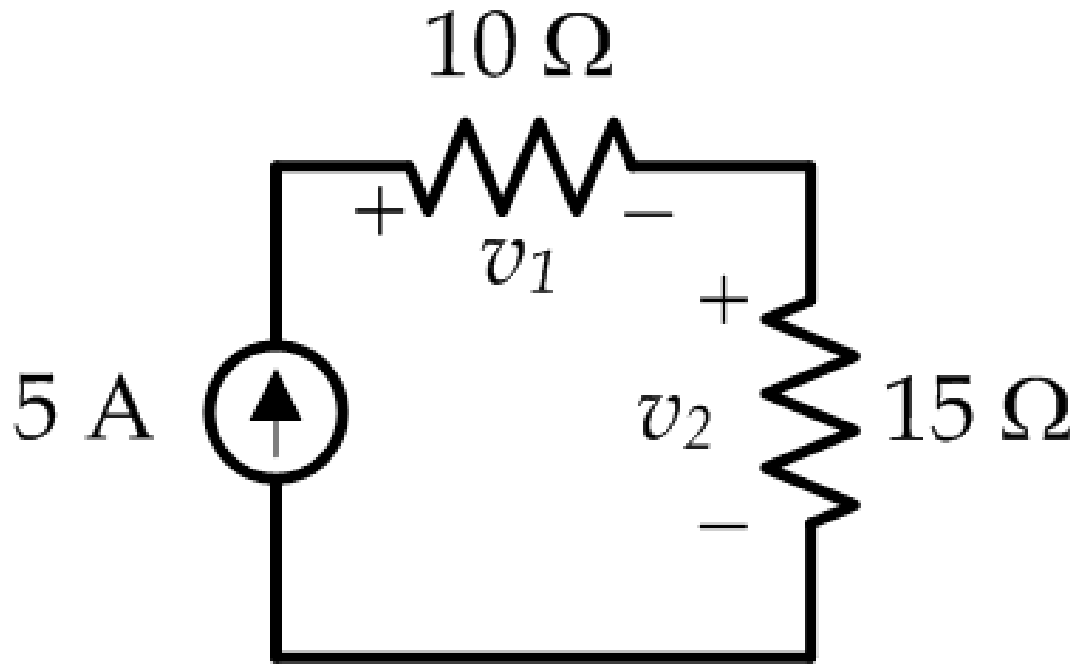

$$v_1 = 5 \times 10 = 50V$$

$$v_2 = 5 \times 15 = 75V$$

Example

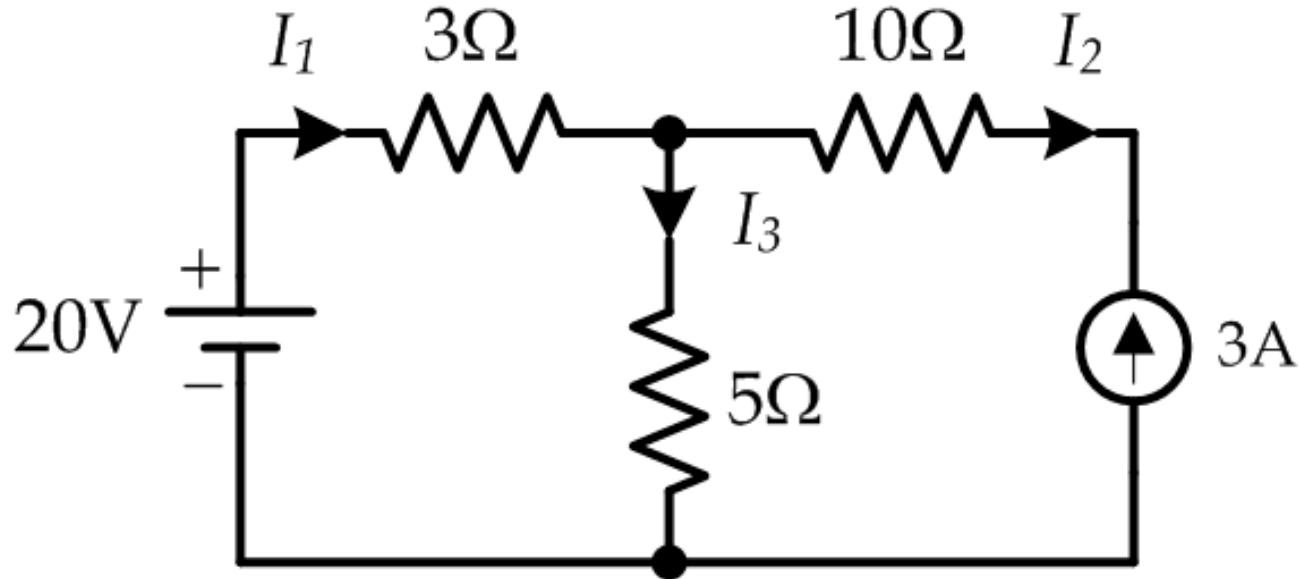

$$KCL: I_1 = I_2 + I_3$$

$$KVL: -20 + 3I_1 + 5I_3 = 0$$

$$-5I_3 + 10I_2 + v_i = 0$$

$$IS: I_2 = -3A$$

$$I_1 = 0.625 \quad A$$


$$\Rightarrow I_2 = -3 \quad A$$

$$I_3 = 3.625 \quad A$$

$$v_i = 48.125 \quad V$$

Complex AC Source

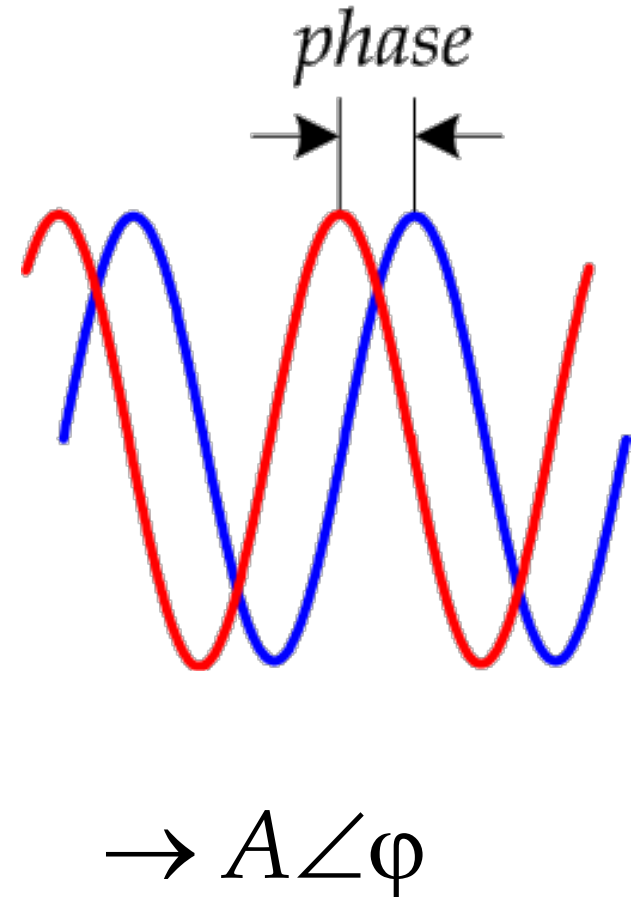- AC Volt or Current has:
 - Amplitude
 - Frequency
 - Phase
- Phase can be expressed in Complex Number
$$A \cos(2\pi f \cdot t + \varphi)$$



Complex AC Source

$$A \cos(2\pi f \cdot t + \varphi)$$

$$A \angle \varphi \quad \rightarrow \quad A \cdot (\cos \varphi + j \sin \varphi)$$

$$\begin{aligned} 110 \angle 30^\circ &\rightarrow 110 \cdot (\cos 30^\circ + j \sin 30^\circ) \\ &= 95.26 + j55 \end{aligned}$$


Power

- Power = rate of energy transfer
 - measured in Watts (W)

$$P = I \cdot V$$

$$P = I \cdot V = I^2 \cdot R$$

$$P = I \cdot V = \frac{V^2}{R}$$

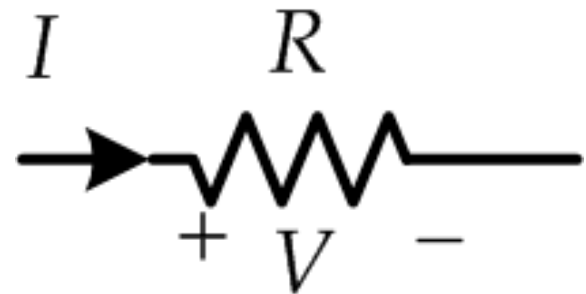


Reactive Power


- Actual Power
 - On resistors only
 - $P = I \times V$
- Reactive Power
 - Imaginary Part of IV
 - $S = I^* \times V = P + j Q$
 - *RMS Values of (V) and (I)*

Process Check

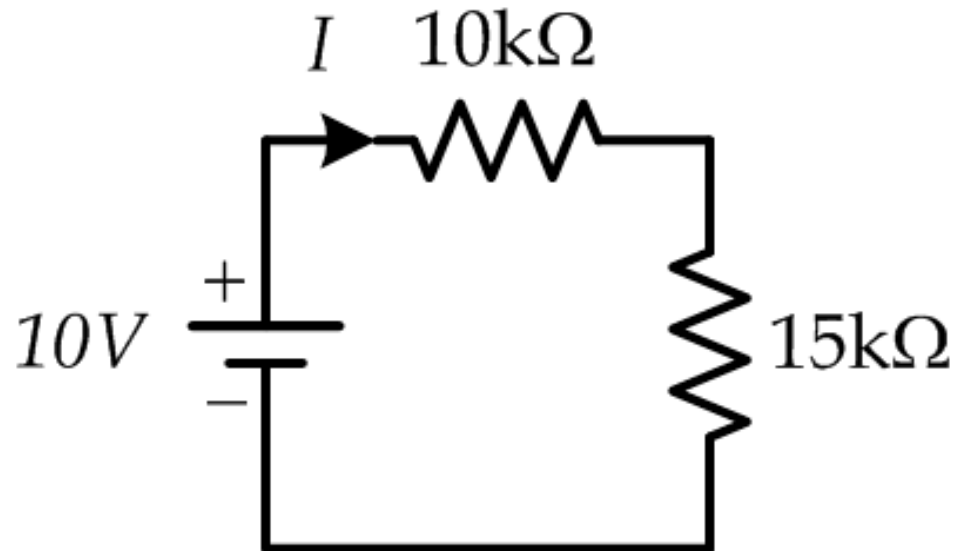- Solve the circuit shown and find the power consumption of each component



Solution (1)

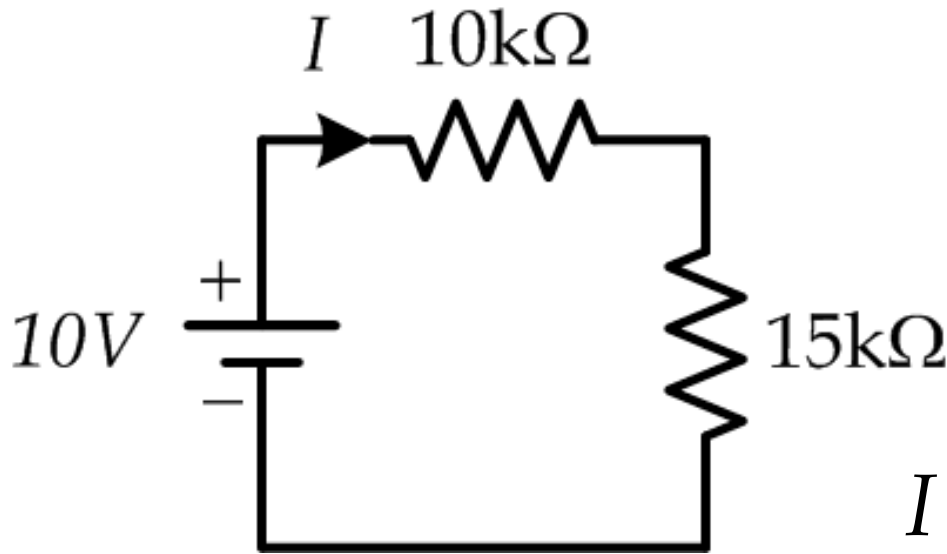


$$I = \frac{10}{10k + 15k} = 400\mu A$$

$$P_1 = I^2 \cdot R_1 = (400 \times 10^{-6})^2 \cdot 10 \times 10^3 = 1.6mW$$

$$P_2 = I^2 \cdot R_2 = (400 \times 10^{-6})^2 \cdot 15 \times 10^3 = 2.4mW$$

Solution (2)

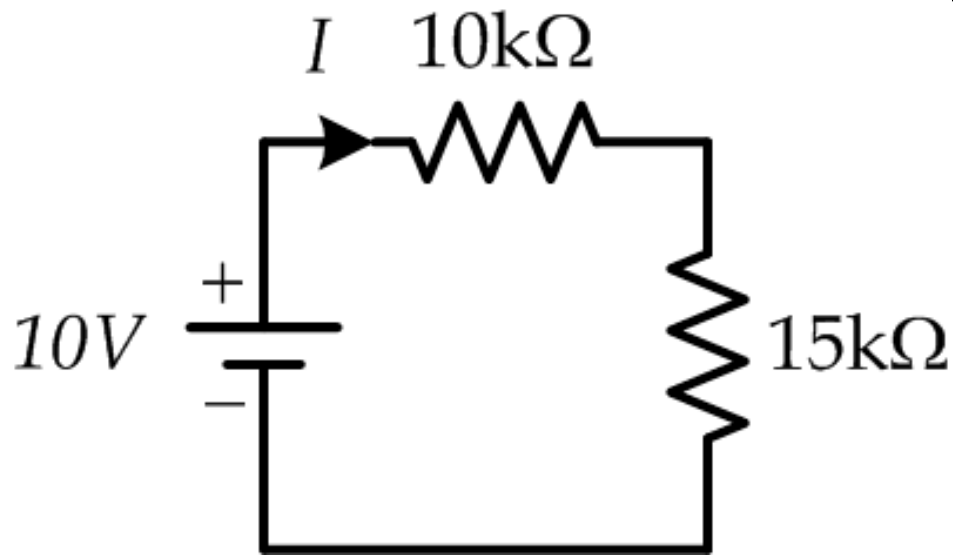


$$V_1 = 10 \frac{10k}{10k + 15k} = 4V$$

$$V_2 = 10 \frac{15k}{10k + 15k} = 6V$$

$$P_1 = \frac{V_1^2}{R_1} = \frac{4^2}{10 \times 10^3} = 1.6mW$$

$$P_2 = \frac{V_2^2}{R_2} = \frac{6^2}{15 \times 10^3} = 2.4mW$$

Total Power = 0

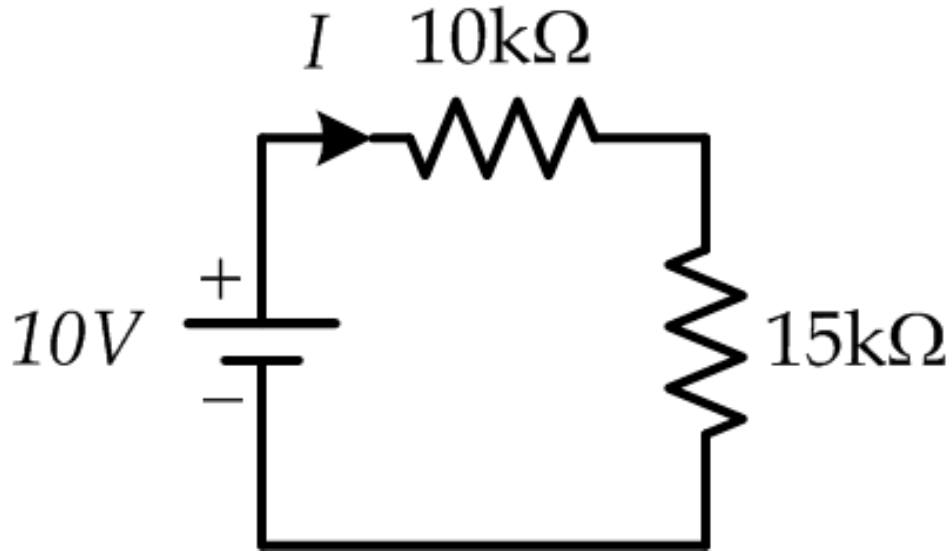

$$P_s = I \cdot V = -400 \times 10^{-6} \cdot 10 = -4mW$$

$$P_1 + P_2 = 4mW$$

Total Power = Zero