

EE251

Lectures

Electronic Measurements



Section 05

Measurements



- How to measure voltage?
- How to measure current?
- How to measure resistance?
- How to view a signal?

Bread Boards

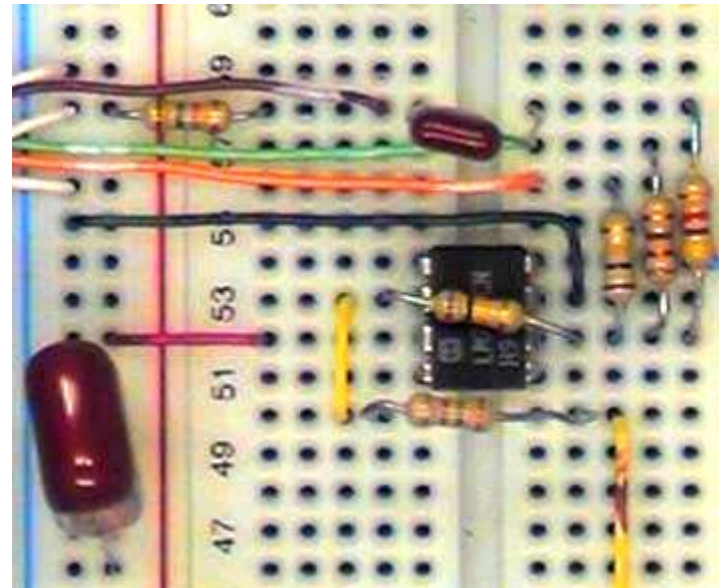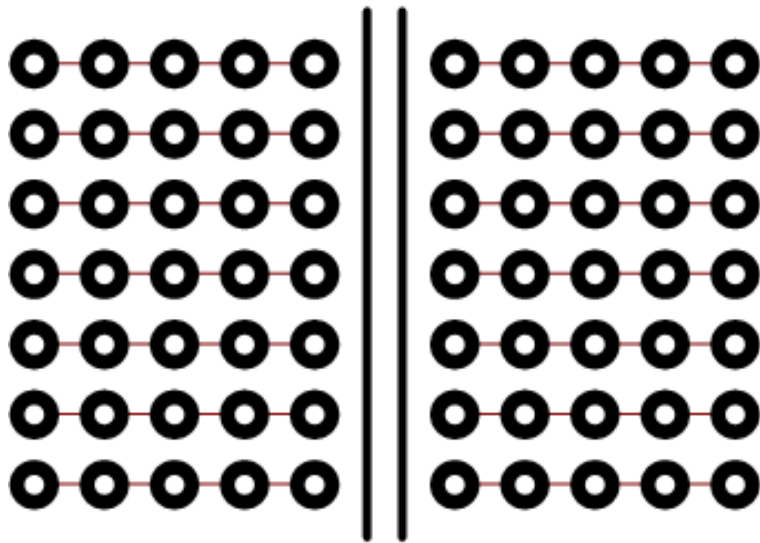
- A board with spring contact holes to hold components; no soldering is required
- Holes of each row are internally connected



Example

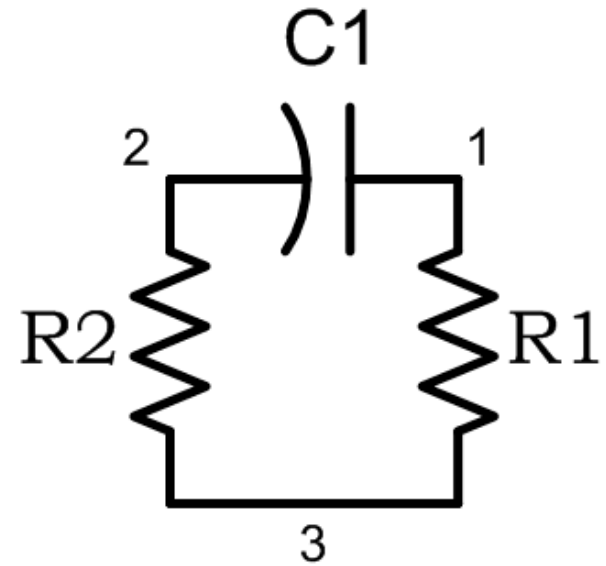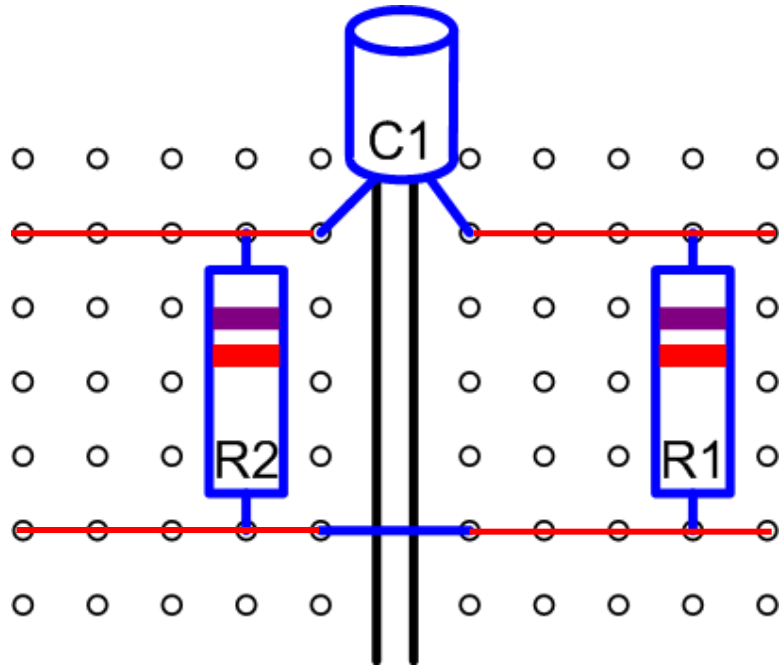


Example

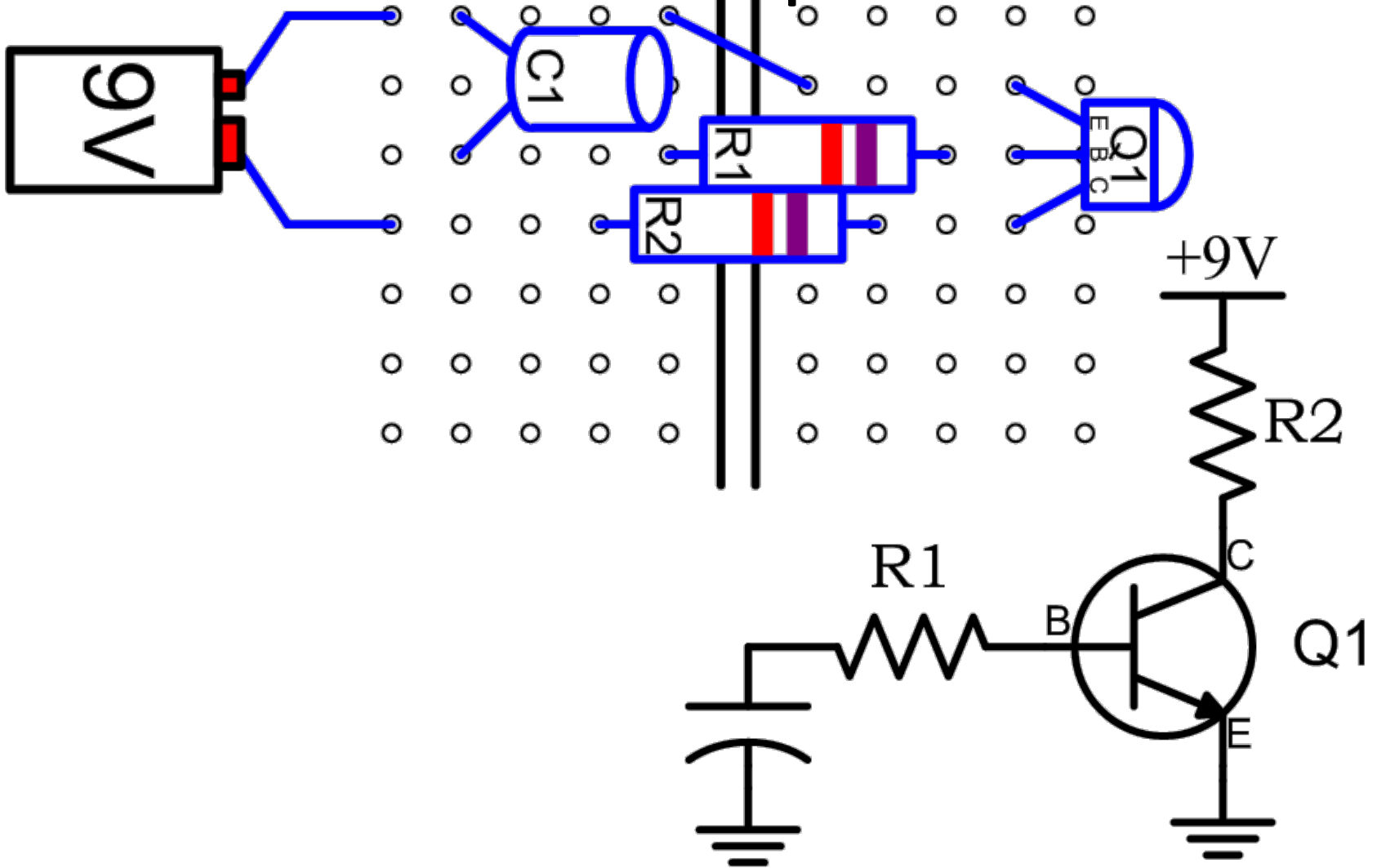

Rules


- Study Circuit
- Collect all components
- Start at the middle
- Power must be off
- Careful with sensitive components
- Nice wiring

Bad Example

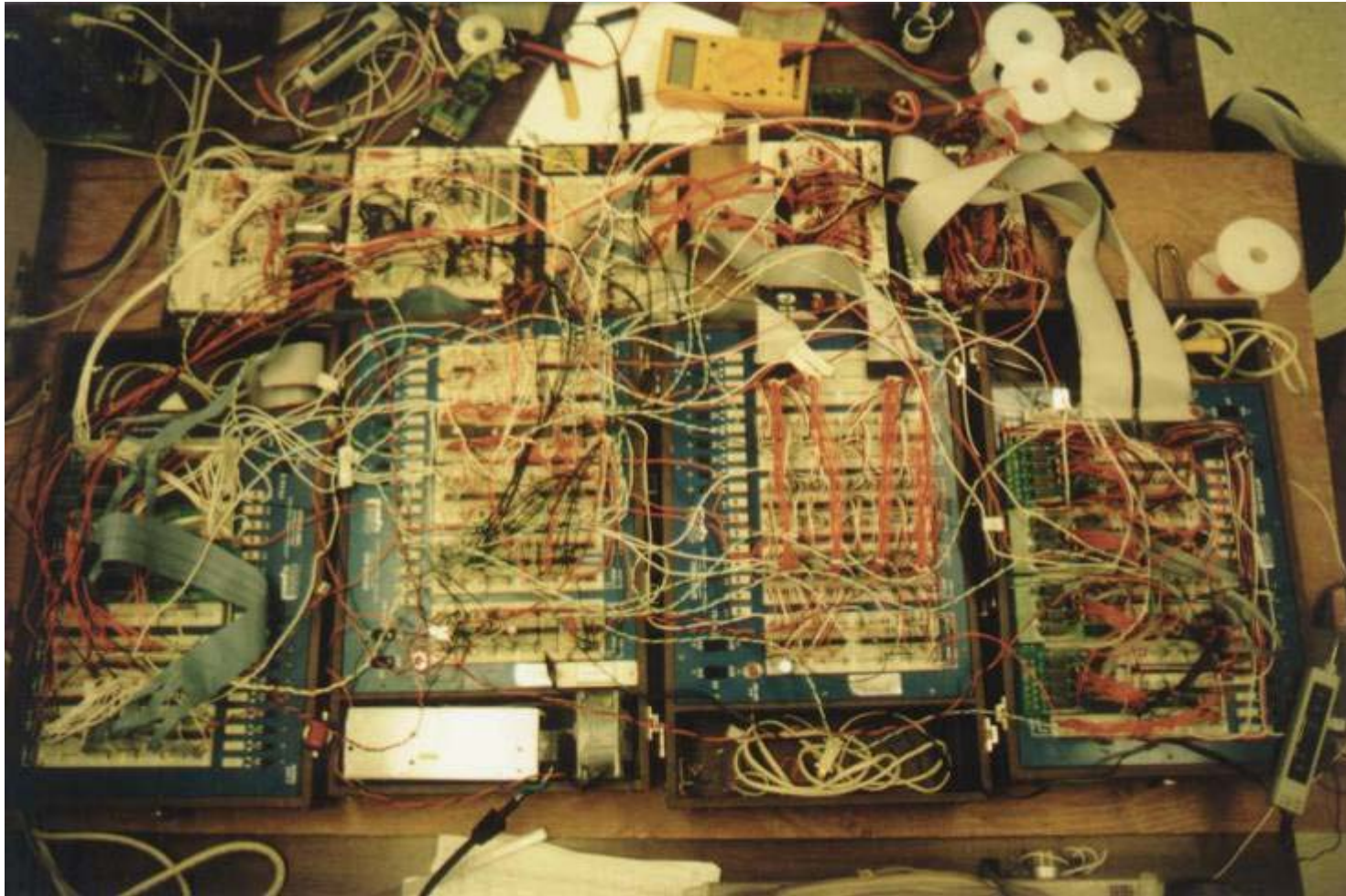


Measuring Volt

- Measure the voltage drop on R_{22}

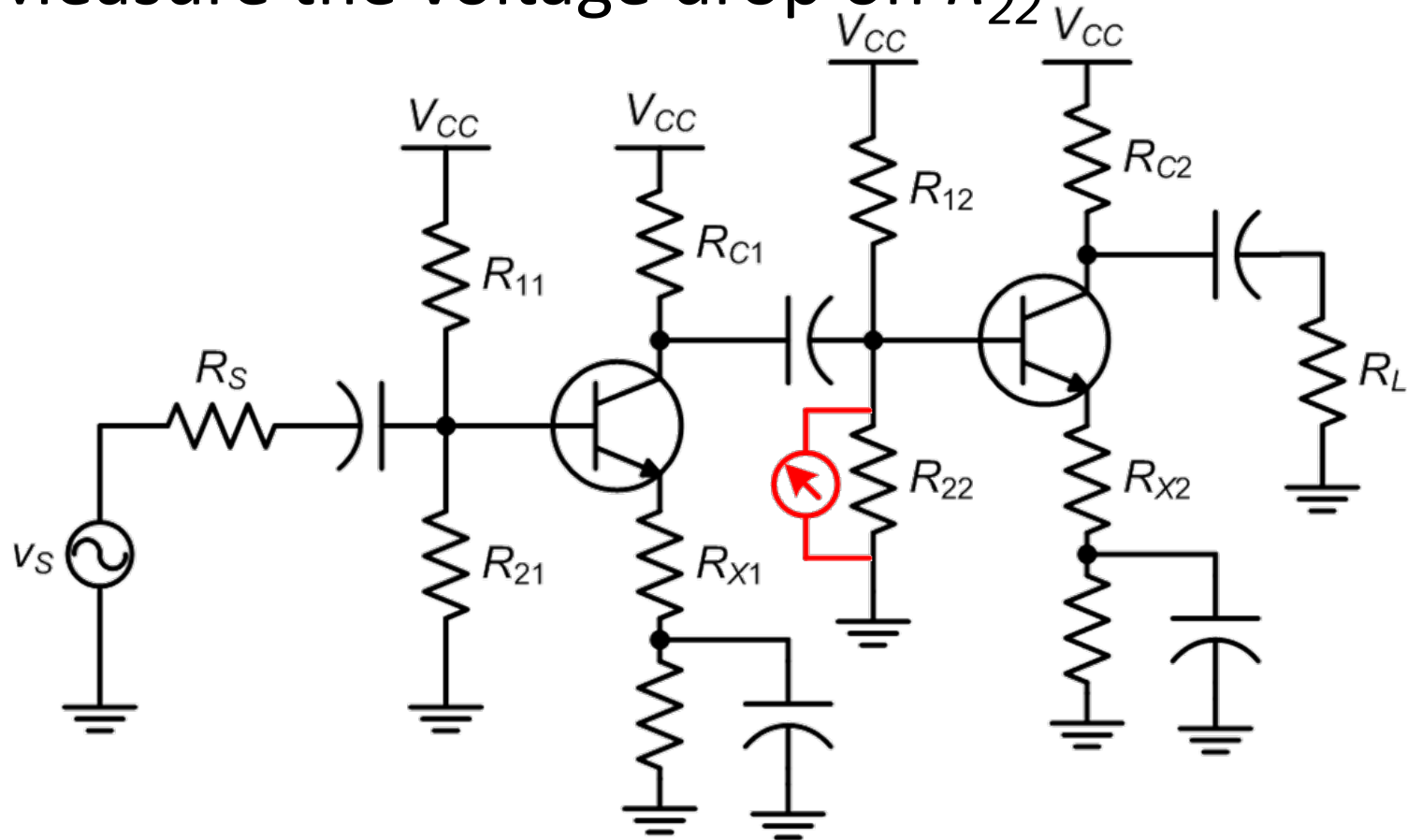


Measuring Current

- Measure the current through R_{X1}

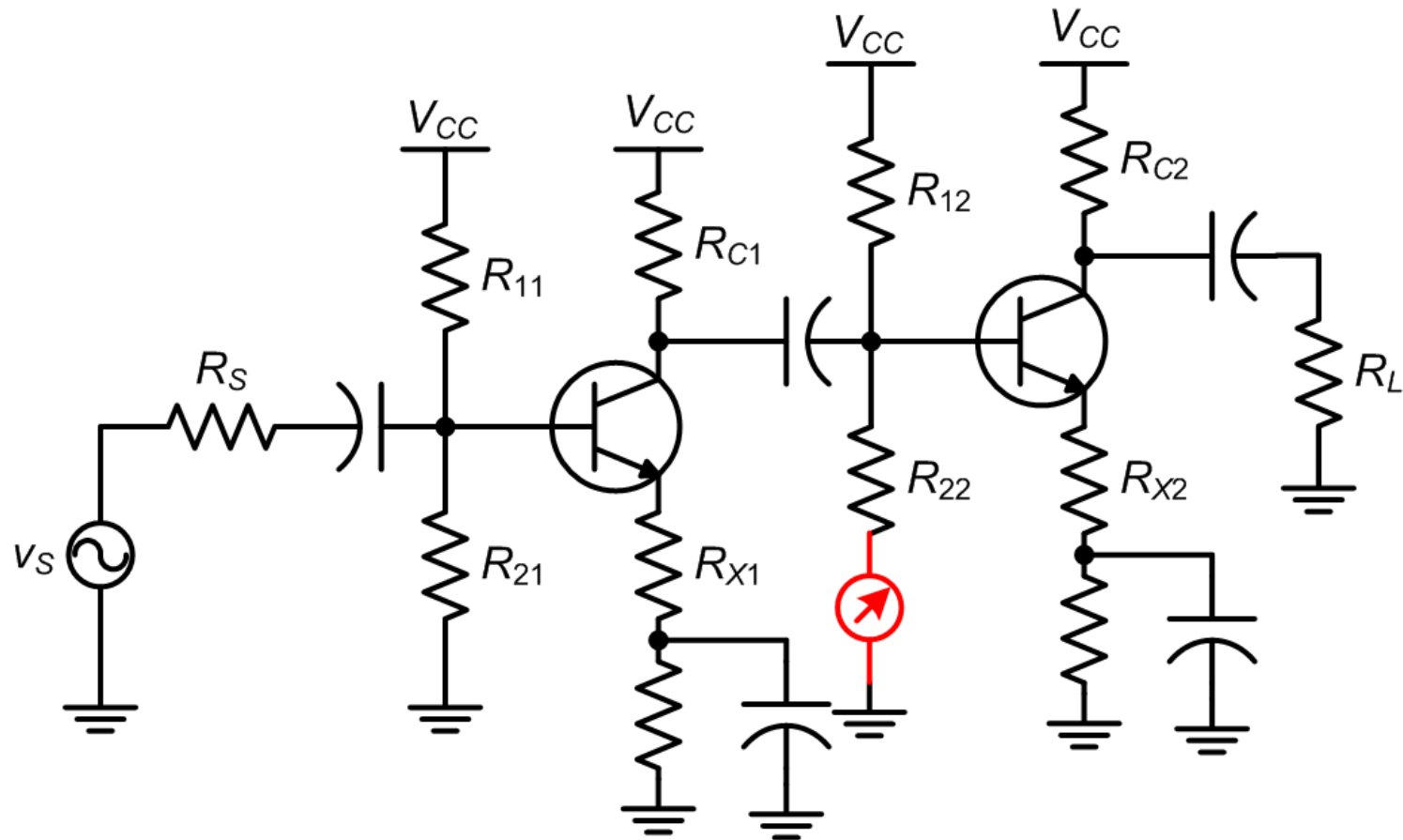

Measuring Resistance


- Measure the resistance of R_{22}

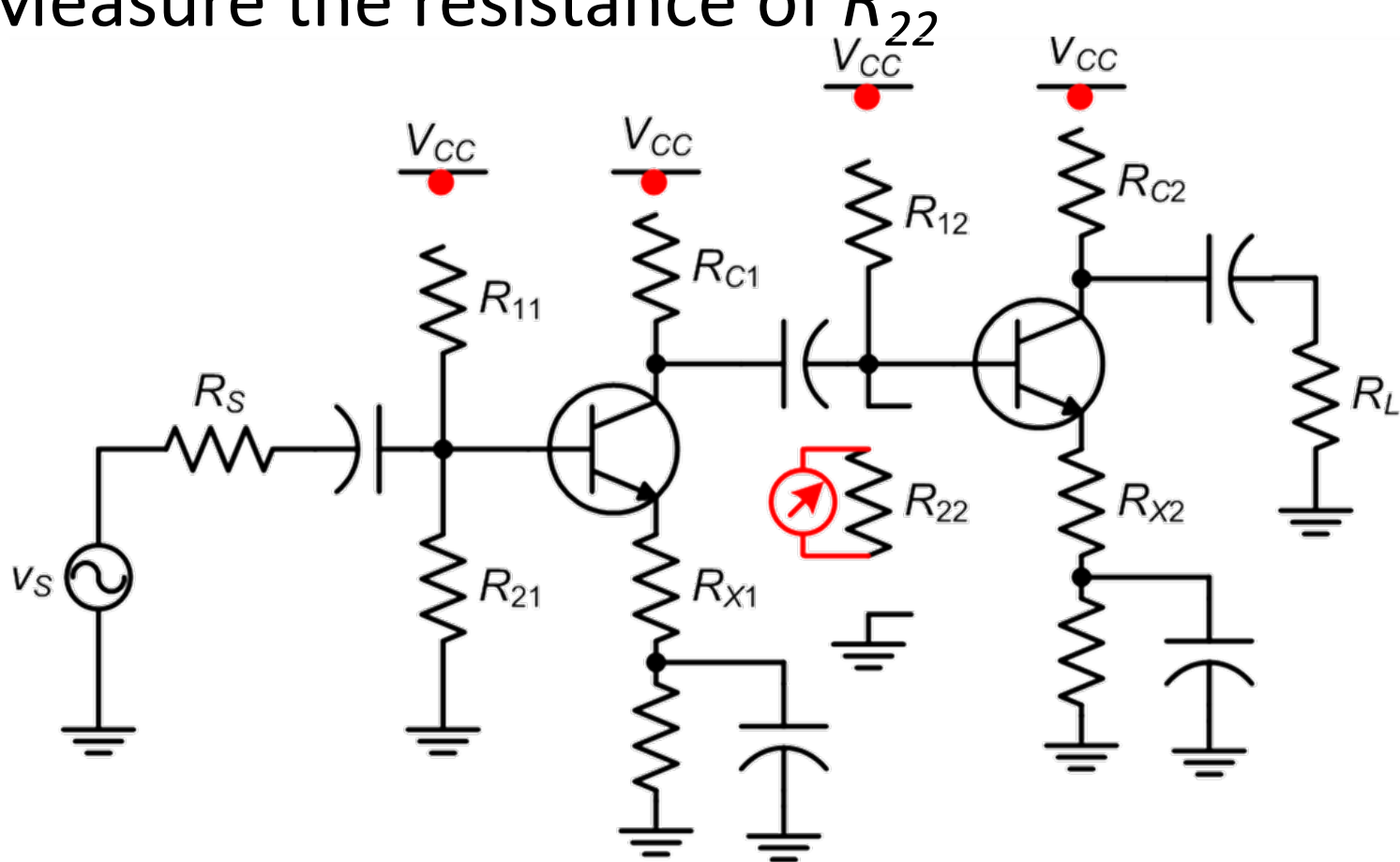

Oscilloscopes




Karl Ferdinand Braun
(1897)

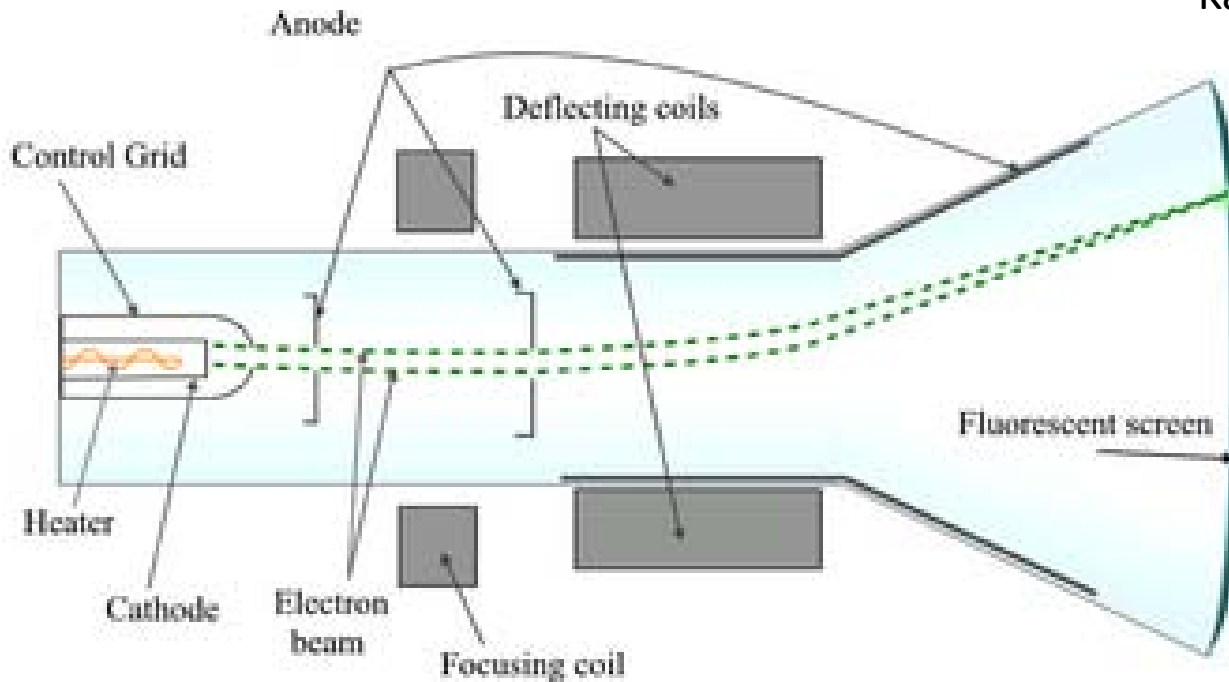

Cathode Ray Tube



Oscilloscopes

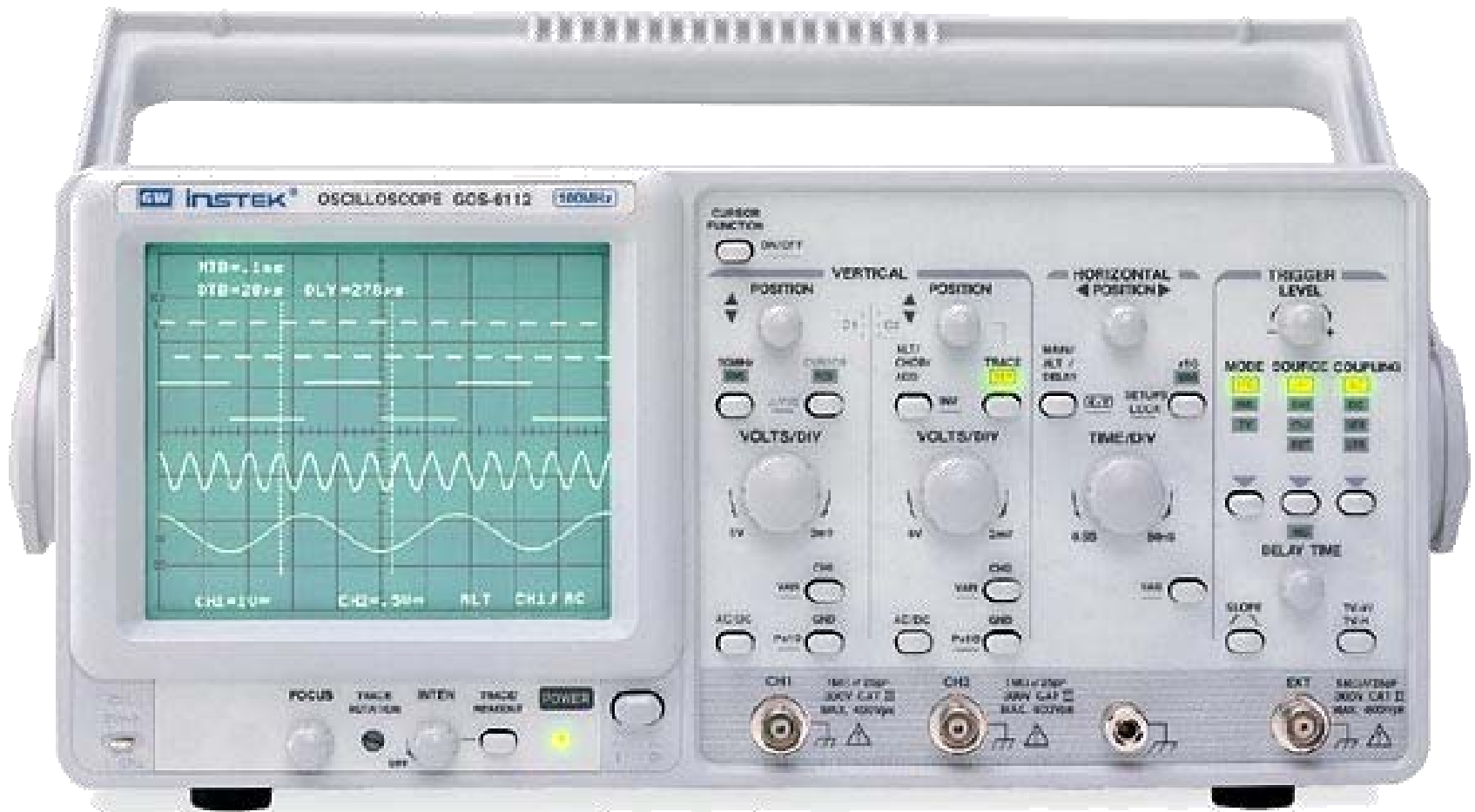


Selection Criteria


- Analog vs. Digital
 - Digital: Sample and Hold
- Bandwidth, Sampling Rate, Resolution (Accuracy)
 - 5x the maximum signal frequency
- Number of Channels
 - 2-4 for correlations
- Memory Depth
 - Recording Time
- Triggering Capability
 - Display Signal after Trigger
- Display Capability
 - phase shift, rise time, fall time
 - delay, pulse width, duty cycle, frequency and period
- Analysis Capabilities
 - Math, FFT



CAD Simulators (Demo)

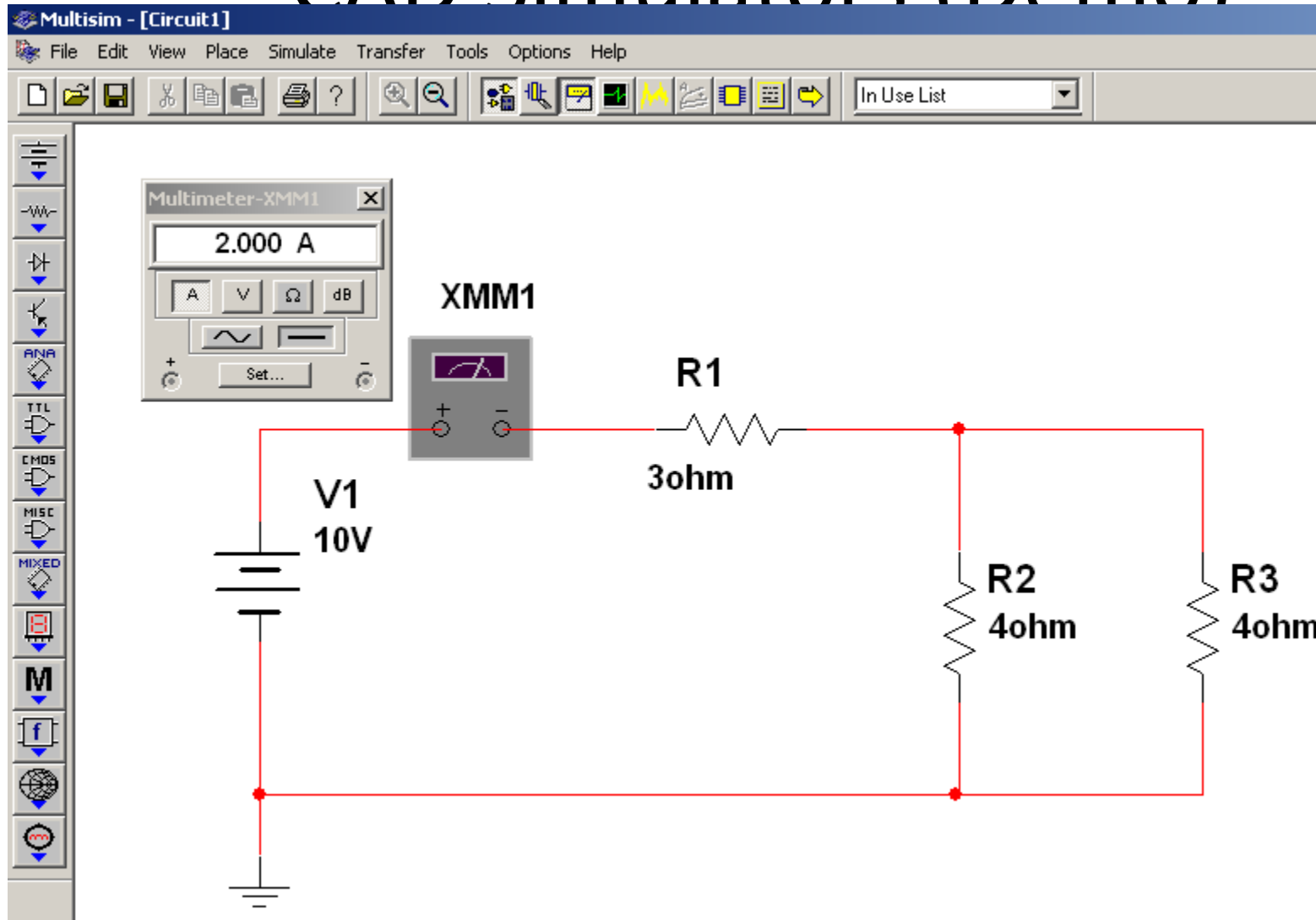

Example

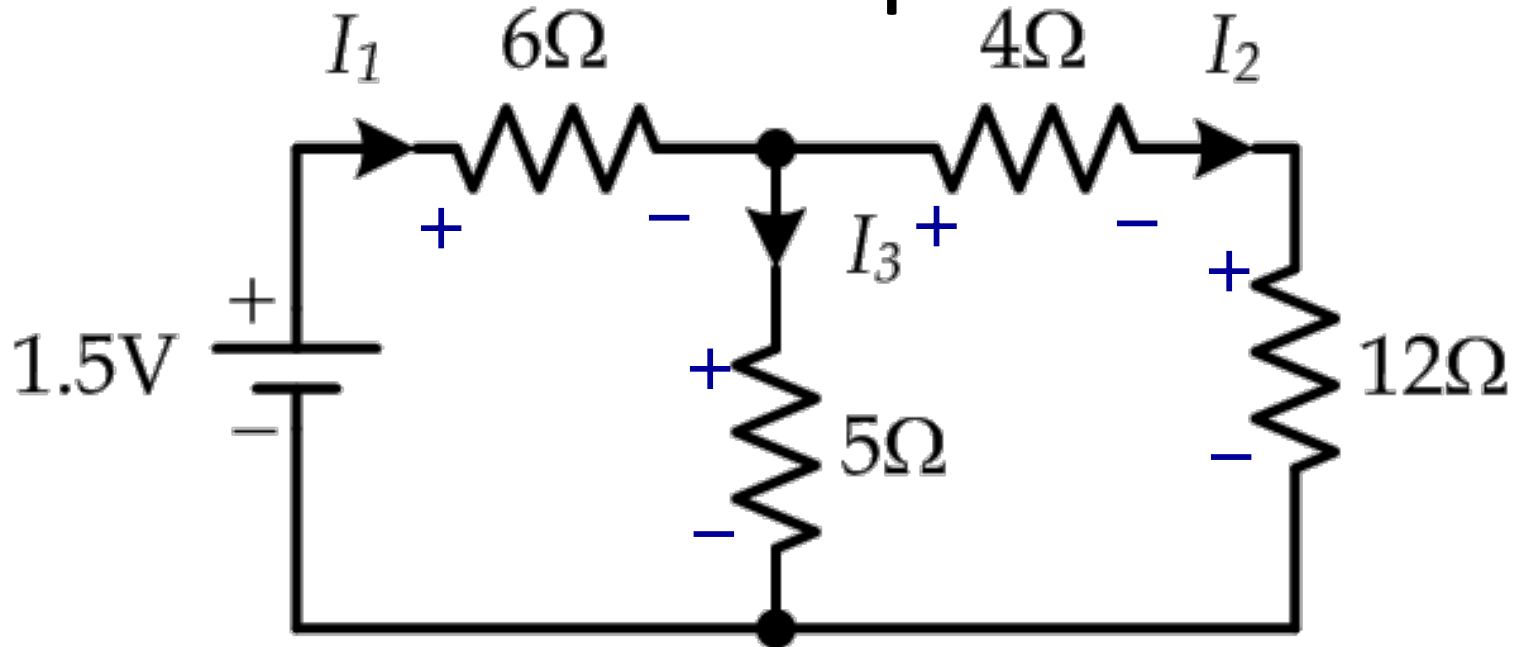

$$KCL: I_1 = I_2 + I_3$$

$$I_1 = 152.9 \text{ mA}$$


$$KVL: -1.5 + 6I_1 + 5I_3 = 0$$

$$\Rightarrow I_2 = 36.4 \text{ mA}$$

$$-5I_3 + 4I_2 + 12I_2 = 0$$

$$I_3 = 116.5 \text{ mA}$$

Simulation

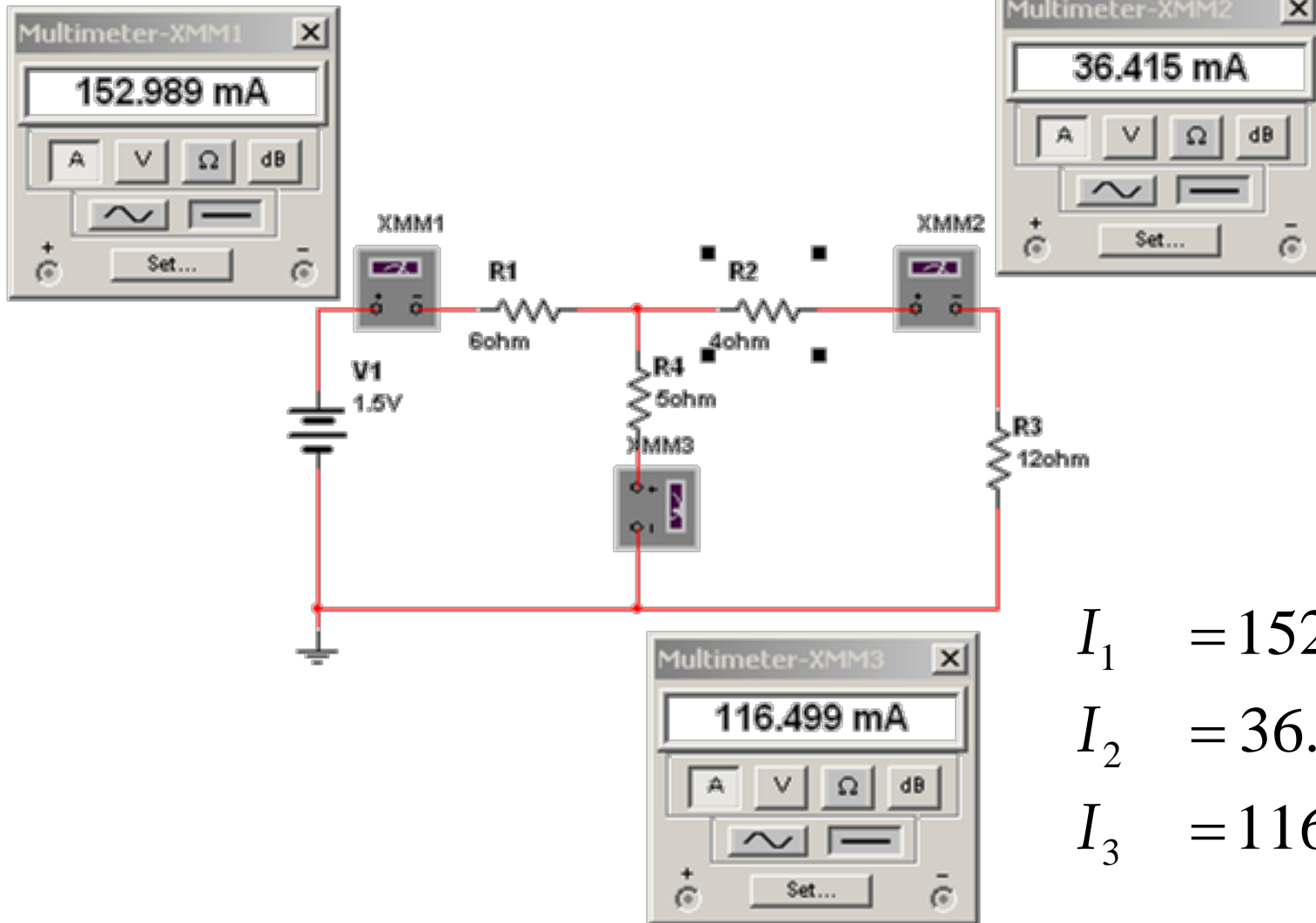


$$I_1 = 152.9 \text{ mA}$$

$$I_2 = 36.4 \text{ mA}$$

$$I_3 = 116.5 \text{ mA}$$

Non-Ideal Instruments

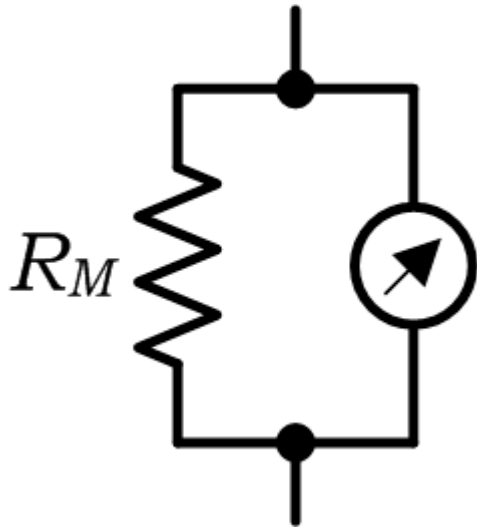

voltmeter


$$R_M \gg R_L$$




ammeter

$$r_m \ll R_L$$


Measurement Error

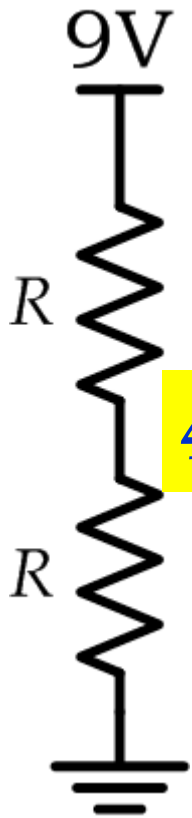

4.50V

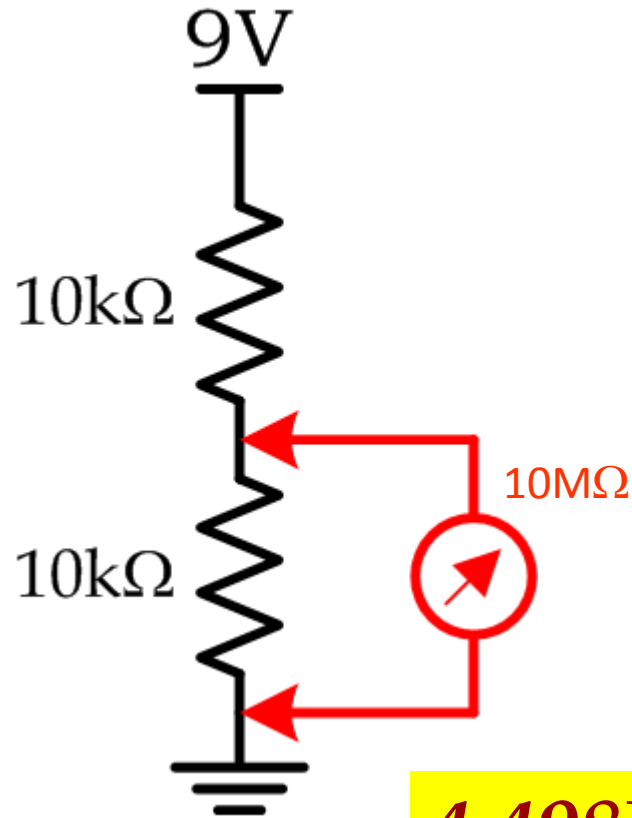

4.498V

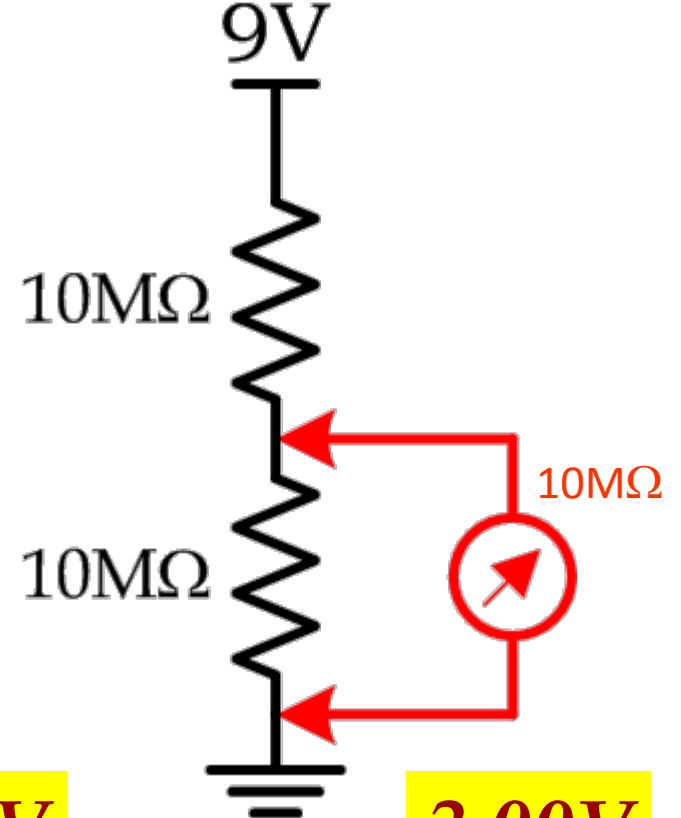


3.00V

Range Extension

- A voltmeter of maximum range of 50V
 - Can it read 100V safely?
- Voltage Divider

$$V = v_{meter} \times \left(1 + \frac{R_g}{R_M} \right)$$
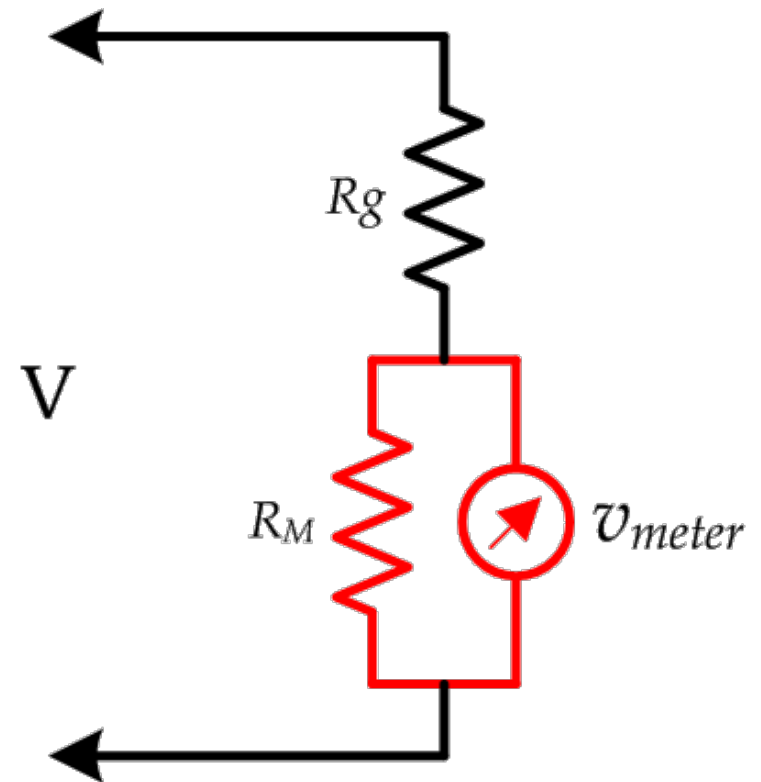
$$er = er_{meter} \times \left(1 + \frac{R_g}{R_M} \right)$$



Non-Ideal OSX (Harmonics)

