

EE251



Lectures

3-Phase Systems

Section 09


3-Phase Generators

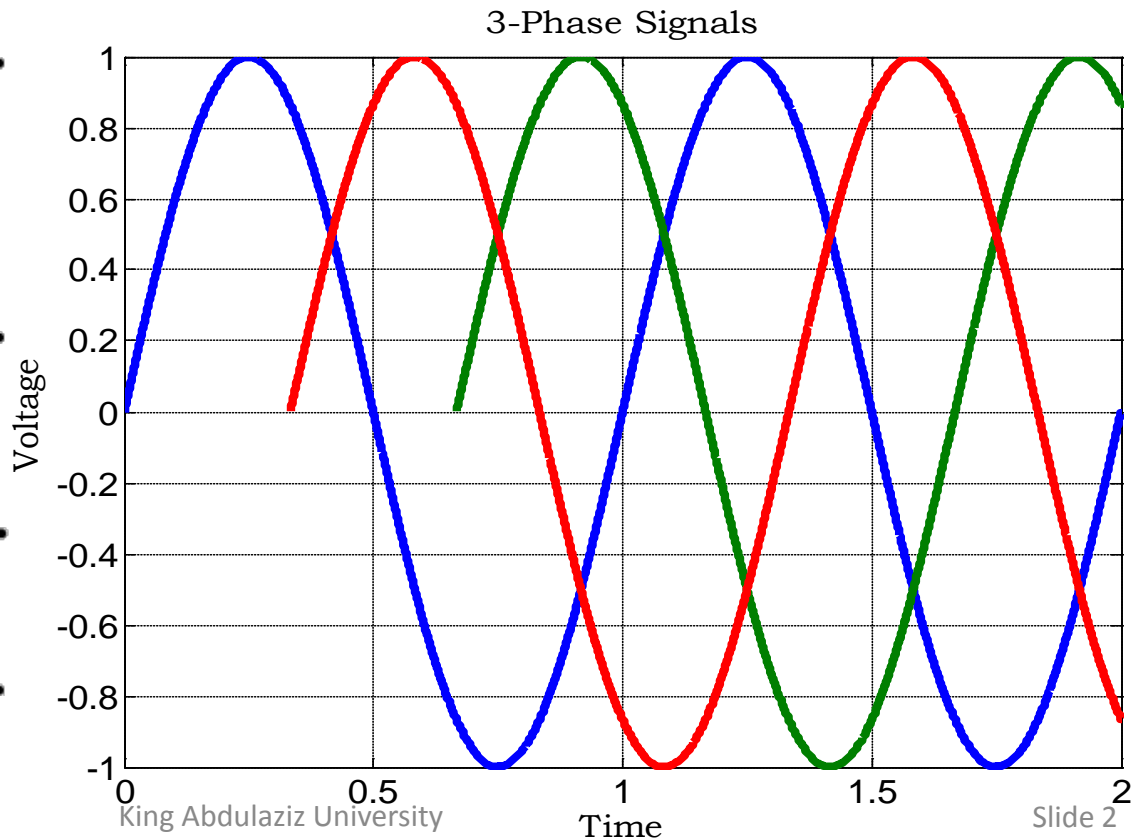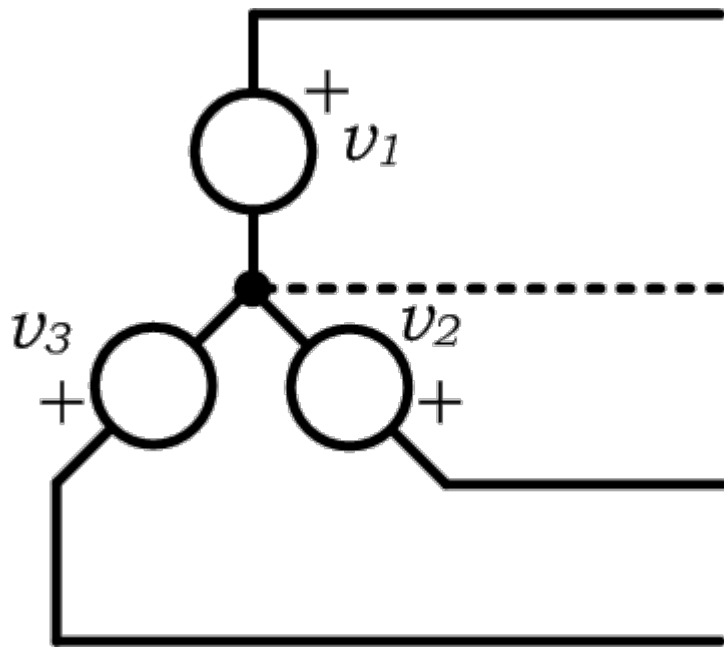- Method for transmitting alternating power
- Three conductors carrying three alternating currents with $360/3=120^\circ$ shift between them





Why 3 ϕ System?

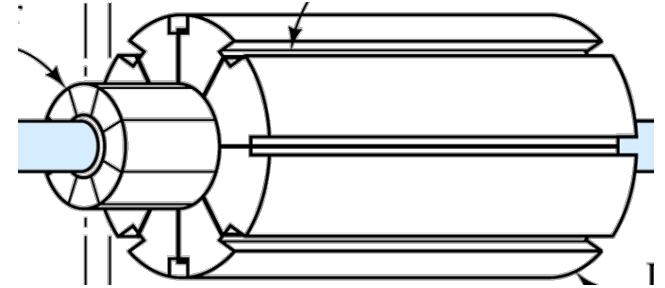- Single Phase Generation
 - push power
 - then stop
 - then drain power → breaks down
- n-Phase Generation
 - constant power generation all the time
 - cost effective
- Usage
 - 1 ϕ of each phase at homes
 - 3 ϕ loads at industry



Vector Representation

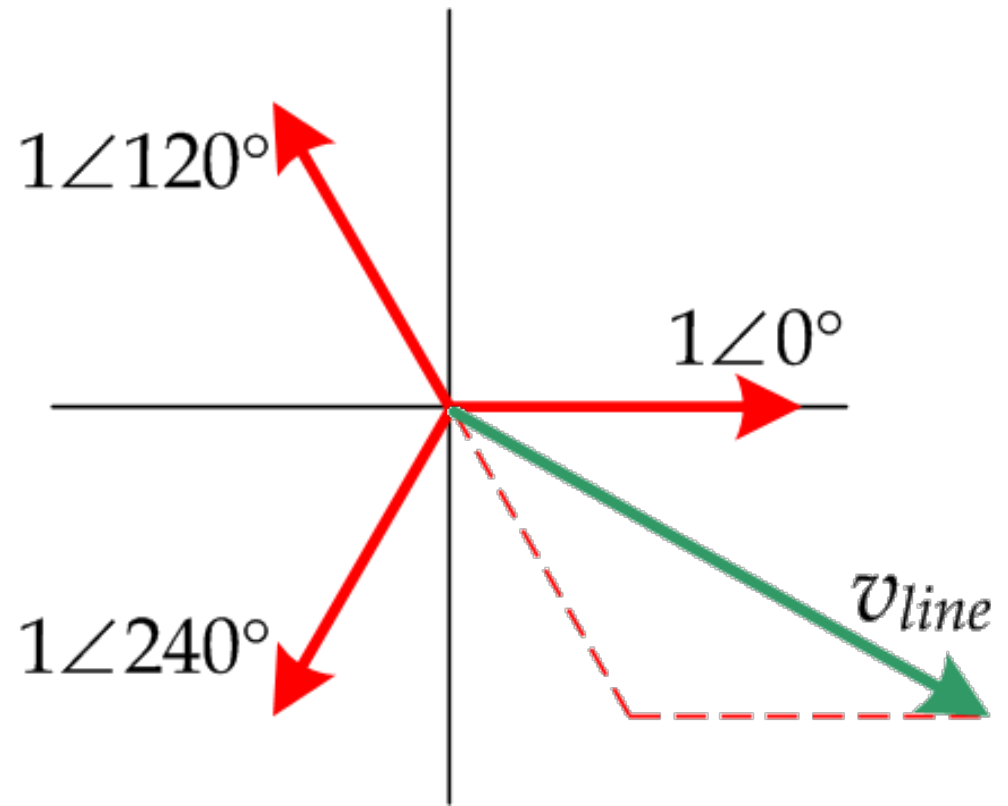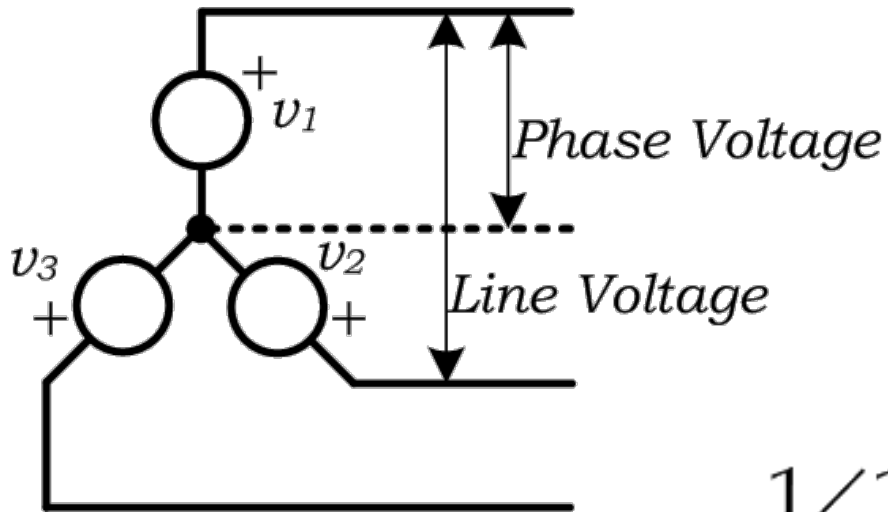

Line Voltage

$$\begin{aligned}v_{12} &= v_1 - v_2 \\&= 1 \angle 0^\circ - 1 \angle 120^\circ \\&= 1 - (\cos 120 + j \sin 120) \\&= \frac{3}{2} - j \frac{\sqrt{3}}{2}\end{aligned}$$

$$v_{12} = \sqrt{3} \angle -30^\circ$$

$$v_{23} = \sqrt{3} \angle +90^\circ$$

$$v_{31} = \sqrt{3} \angle -150^\circ$$

Examples

- If a phase voltage is $120V \sim$

– Line Voltage = $120 \cdot \sqrt{3} = 208V \sim$

- If a line voltage is $220V \sim$


– Phase Voltage = $220 / \sqrt{3} = 127V \sim$

More Advantages


- Using Line Voltages
 - Higher voltage → Less Currents
 - Two different voltage ratings

- Single Phase
 - 6 wires instead of 4 (sometimes 3)
 - More line losses


Star-Start Connection

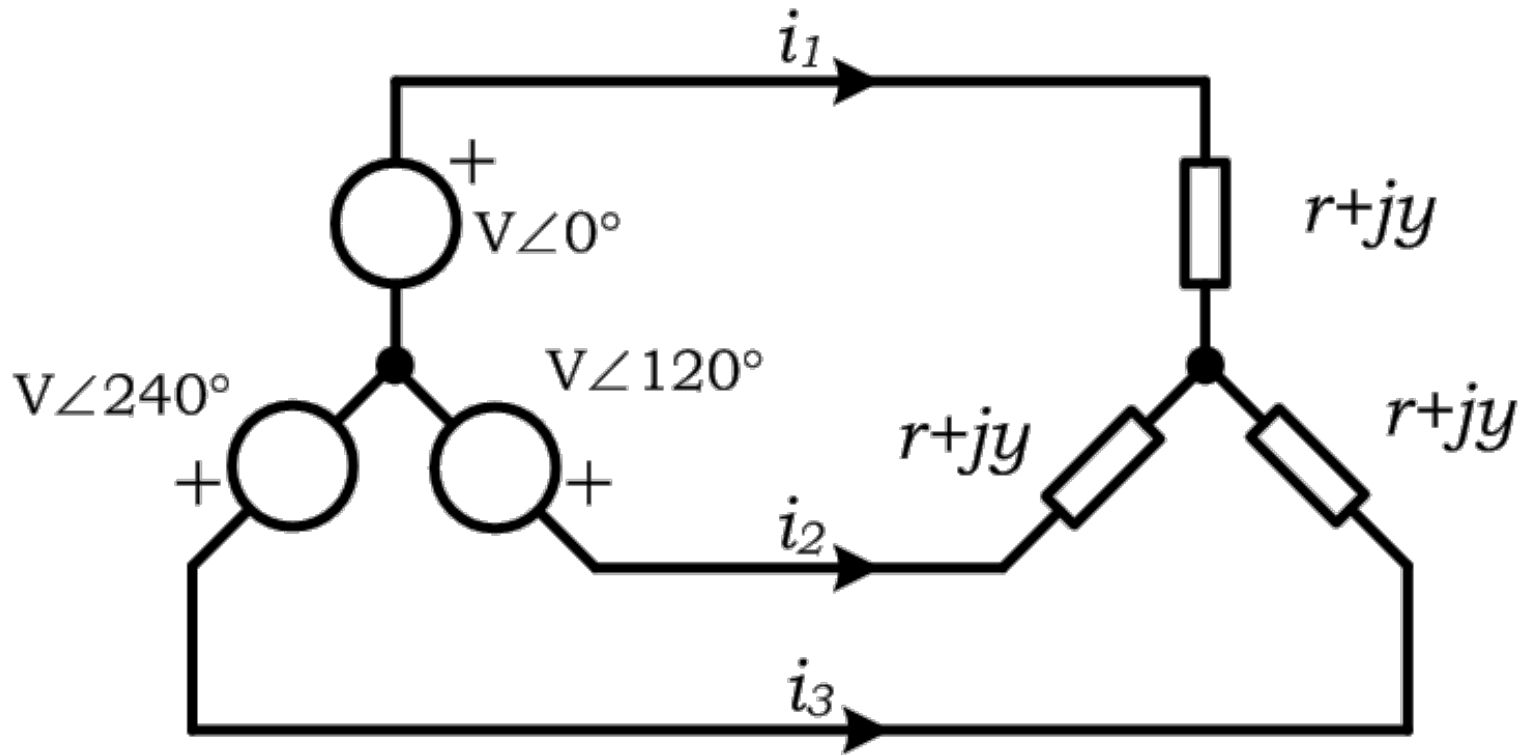

Star-Delta Connection

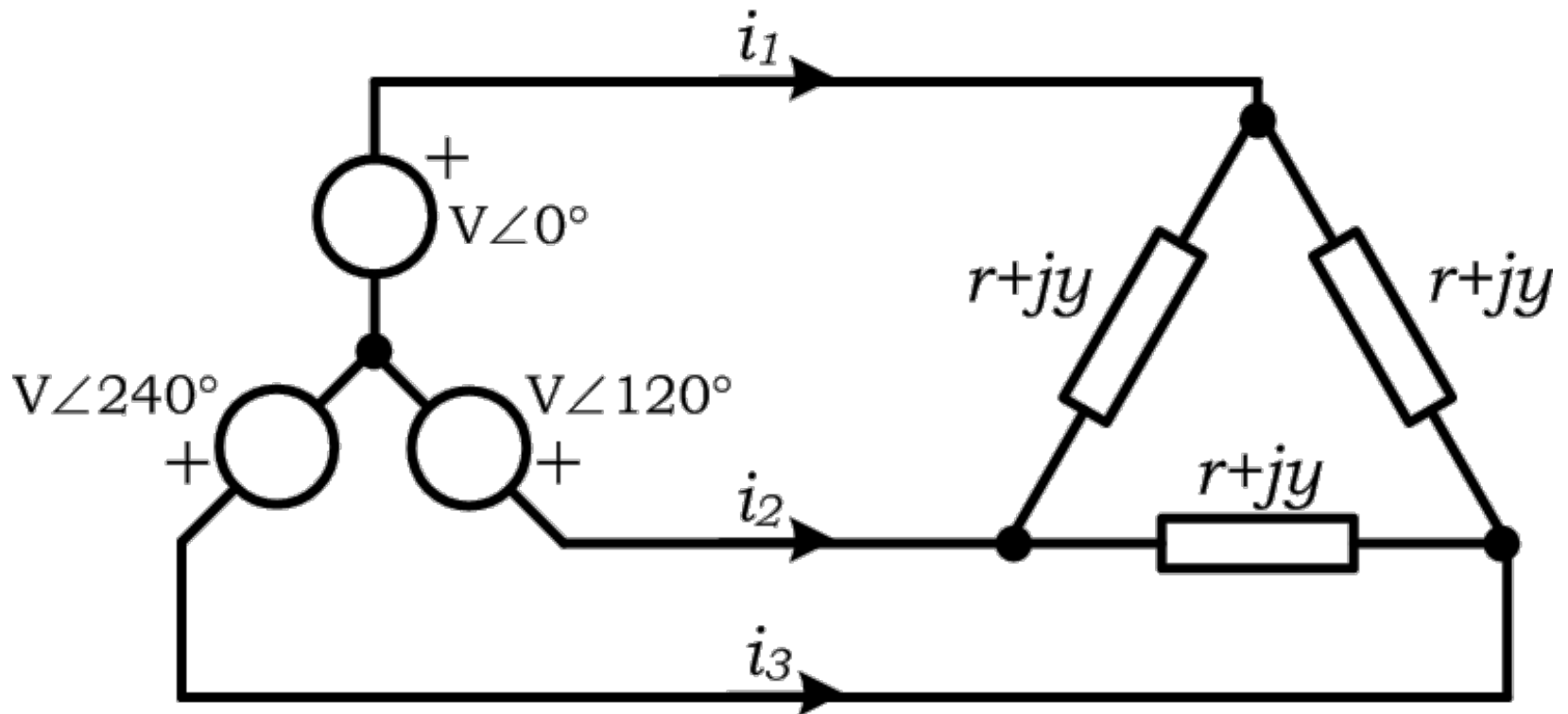

Balanced Load

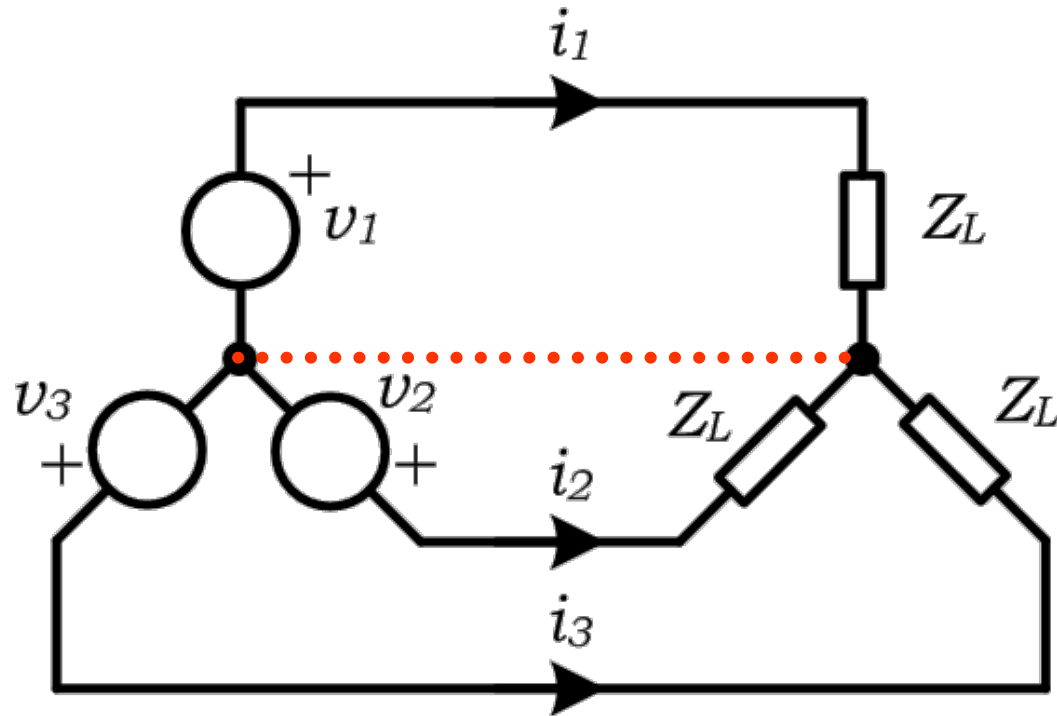

$$i_1 = I \angle 0^\circ, i_2 = I \angle 120^\circ, i_3 = I \angle 240^\circ$$


$$I_n = 0$$

Power Factor (PF)

- Best Network when $Q=0$
- Let the angle between Voltage and Current be θ


$$PF = \cos \theta = \begin{cases} 1 & \theta = 0^\circ \\ 0 & \theta = 90^\circ \end{cases}$$

Power Factor Correction (Y)

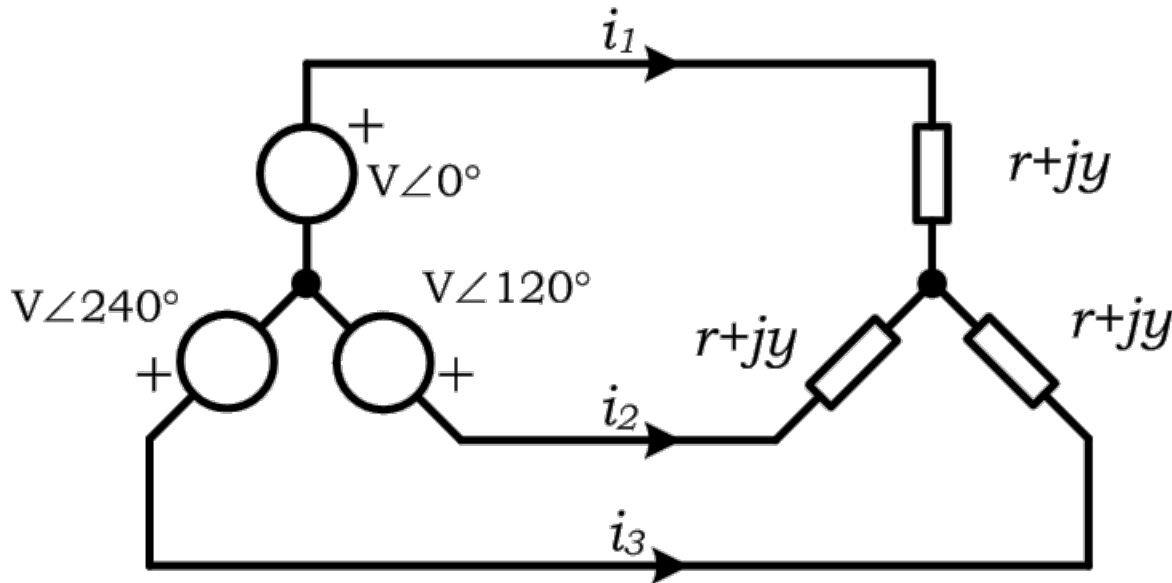


$$PF = \frac{r}{\sqrt{r^2 + y^2}}$$
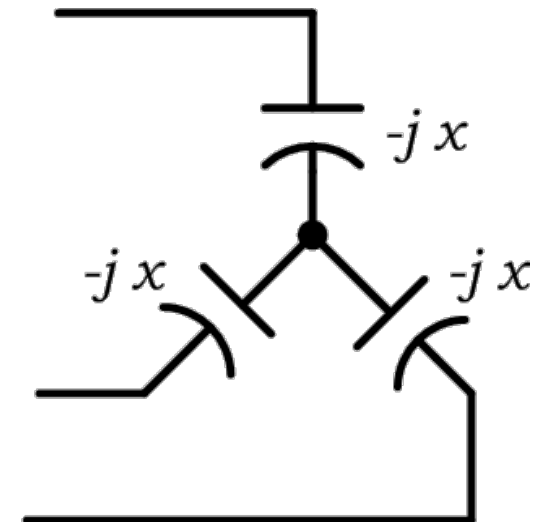
$$x = \frac{r^2 + y^2}{y} \rightarrow Z_{eq} = r + \frac{y^2}{r}$$




Power Factor Correction (Δ)

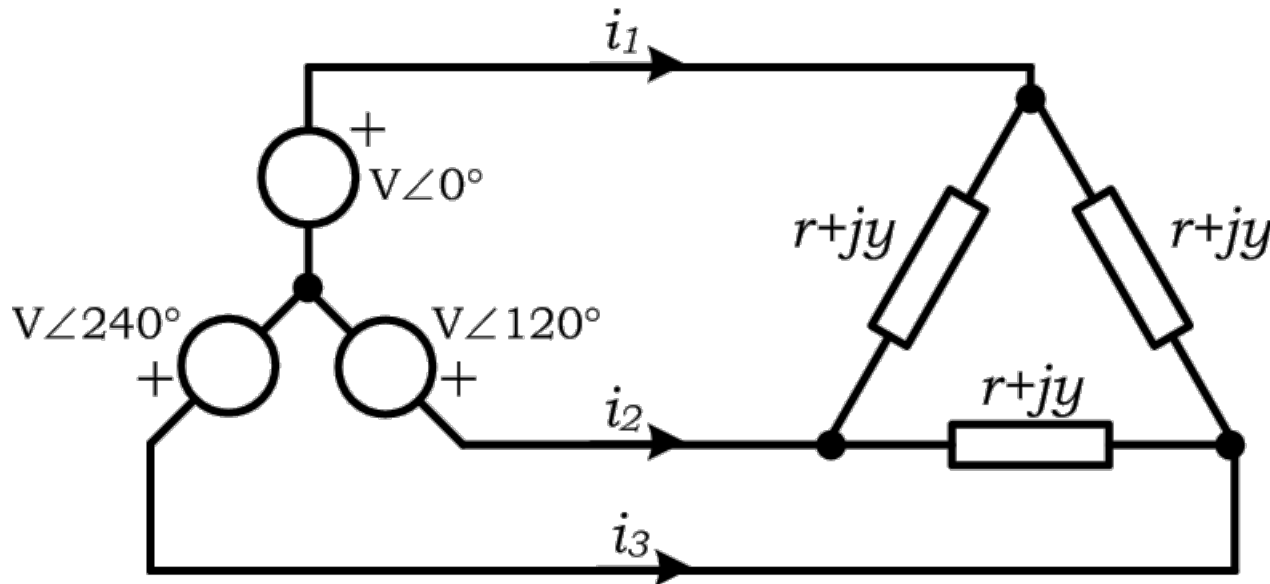

$$PF = \frac{r}{\sqrt{r^2 + y^2}}$$
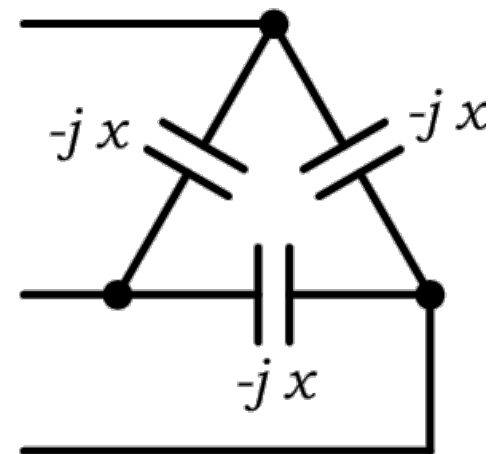
$$x = \frac{r^2 + y^2}{y} \rightarrow Z_{eq} = r + \frac{y^2}{r}$$



Example

