

Fundamental Notions About Electrical Transients

Note Title


2/3/2014

* Electrical transients occur when a switch opens or closes or during faults.

A New path for the current to flow is created or an existing path is disconnected.

* Although transients period is very short (in comparison to steady-state conditions), the voltage and current stresses are high that may damage some components in the power system.

* Transient (Surge):

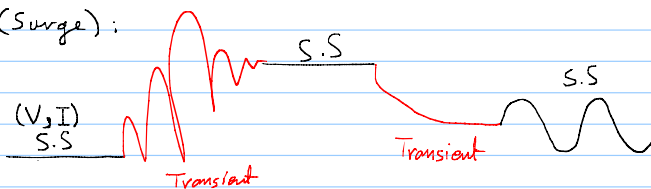

* Basic Circuit Relationship:

	Circuit	Model	Energy
Resistor (Ω)		$v(t) = R i(t)$	$E = R i^2 t$
Inductor (H)		$v(t) = L \frac{di(t)}{dt}$	$E = \frac{1}{2} L i^2$
Capacitor (F)		$i(t) = C \frac{dv(t)}{dt}$	$E = \frac{1}{2} C v^2$

* Three Fundamental Characteristics of Circuits with Lumped Parameters:

1) I_L doesn't change instantaneously. $\frac{I_L}{\text{min}}$

2) V_C " " " " $\frac{V_C}{\text{max}}$


3) At steady-state and transient conditions, the energy conservation is valid.

$$E_{\text{total}} = E_{\text{stored}} + E_{\text{dissipated}}$$


or

$$E_{\text{stored-before_event}} = E_{\text{stored-after_event}} + E_{\text{dissipated}}$$


Ex. Switching an RL Circuit:

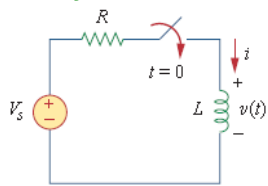
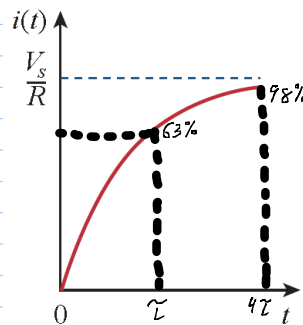
$$i(t) = \frac{V_s}{R}(1 - e^{-t/\tau}), \quad \tau = \frac{L}{R} \text{ (time constant)}$$




Ex. Switching an RC Circuit:

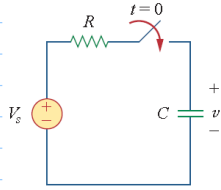


time constant

$$v(t) = V_s + (V_0 - V_s)e^{-t/\tau}, \quad \tau = RC$$

V_0 is the capacitor initial charge.

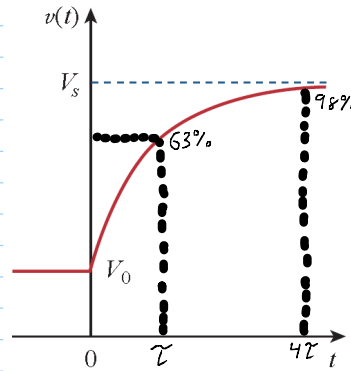


Ex. Switching an LC Circuit:

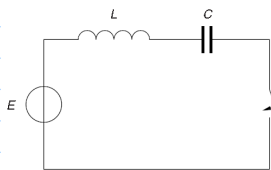

$$i(t) = E\sqrt{\frac{C}{L}} \sin(\omega_0 t)$$

oscillation frequency $\rightarrow \omega_0 = \sqrt{LC}$

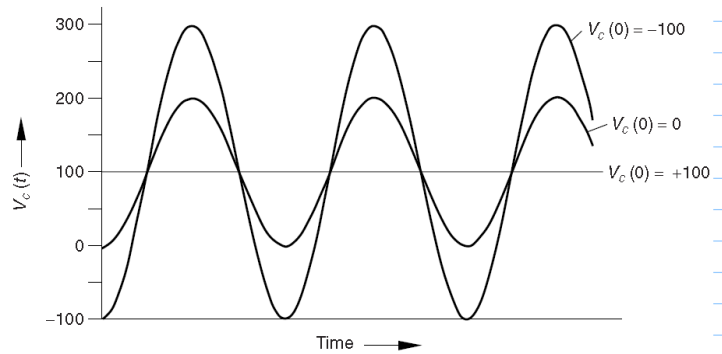characteristic impedance $Z_0 = (L/C)^{1/2}$



$$V_c(t) = E - [E - V_c(0)] \cos(\omega_0 t)$$