

Transients Solutions by Laplace Transform

Note Title

2/10/2014

* Laplace Transforms:

$f(s)$	$F(t)$	$f(s)$	$F(t)$
1 $\frac{1}{s}$	1	12 $\frac{1}{s(s+\alpha)^2}$	$\frac{1}{\alpha^2}(1 - e^{-\alpha t} - \alpha t e^{-\alpha t})$
2 $\frac{1}{s^2}$	t	13 $\frac{1}{s^2(s+\alpha)^2}$	$\frac{1}{\alpha^2}(\alpha t - 2 + \alpha t e^{-\alpha t} + 2e^{-\alpha t})$
3 $\frac{1}{s^n}$ ($n = 1, 2, \dots$)	$\frac{t^{n-1}}{(n-1)!}$	14 $\frac{1}{(s+\alpha)(s+\beta)^2}$	$\frac{1}{(\alpha-\beta)} \{e^{-\alpha t} + [(\alpha-\beta)t - 1]e^{-\beta t}\}$
4 $\frac{1}{s+\alpha}$	$e^{-\alpha t}$	15 $\frac{1}{(s+\alpha)(s+\beta)(s+\gamma)}$	$\frac{1}{(\beta-\alpha)(\gamma-\alpha)} e^{-\alpha t} + \frac{1}{(\alpha-\beta)(\gamma-\beta)} e^{-\beta t} + \frac{1}{(\alpha-\gamma)(\beta-\gamma)} e^{-\gamma t}$
5 $\frac{1}{s(s+\alpha)}$	$\frac{1}{\alpha}(1 - e^{-\alpha t})$	16 $\frac{1}{s^2 + \alpha^2}$	$\frac{1}{\alpha} \sin \alpha t$
6 $\frac{1}{(s+\alpha)^2}$	$t e^{-\alpha t}$	17 $\frac{s}{s^2 + \alpha^2}$	$\cos \alpha t$
7 $\frac{1}{(s+\alpha)^n}$ ($n = 1, 2, \dots$)	$\frac{t^{n-1} e^{-\alpha t}}{(n-1)!}$	18 $\frac{1}{s^2 + \alpha^2}$	$\frac{1}{\alpha^2}(1 - \cos \alpha t)$
8 $\frac{1}{s^2(s+\alpha)}$	$\frac{1}{\alpha^2}(e^{-\alpha t} + \alpha t - 1)$	19 $\frac{1}{s^2(s^2 + \alpha^2)}$	$\frac{1}{\alpha^3}(\alpha t - \sin \alpha t)$
9 $\frac{1}{s^2(s+\alpha)}$	$\frac{1}{\alpha^2}(\frac{1}{\alpha} - t + \frac{\alpha t^2}{2} - \frac{1}{\alpha} e^{-\alpha t})$	20 $\frac{1}{s^2(s^2 + \alpha^2)}$	$\frac{1}{2\alpha^3}(\sin \alpha t - \alpha t \cos \alpha t)$
10 $\frac{1}{(s+\alpha)(s+\beta)}$	$\frac{1}{(\beta-\alpha)}(e^{-\alpha t} - e^{-\beta t})$	21 $\frac{s^2}{(s^2 + \alpha^2)^2}$	$\frac{1}{2\alpha}(\sin \alpha t + \alpha t \cos \alpha t)$
11 $\frac{s}{(s+\alpha)(s+\beta)}$	$\frac{1}{(\beta-\alpha)}(\beta e^{-\beta t} - \alpha e^{-\alpha t})$	22 $\frac{s^2 - \alpha^2}{(s^2 + \alpha^2)^2}$	$t \cos \alpha t$
		23 $\frac{1}{s^2 - \alpha^2}$	$\frac{1}{\alpha} \sinh \alpha t$
		24 $\frac{s}{s^2 - \alpha^2}$	$\cosh \alpha t$

* Circuits Representain using Laplace:

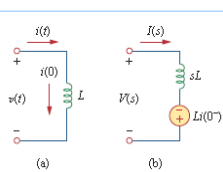


Figure 16.1 Representation of an inductor: (a) time-domain, (b, c) s-domain equivalents.

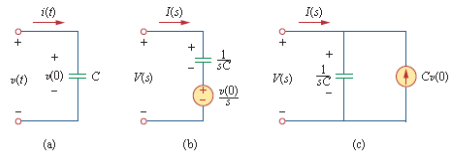


Figure 16.2 Representation of a capacitor: (a) time-domain, (b, c) s-domain equivalents.

Impedance of an element in the s-domain.*

Element	$Z(s) = V(s)/I(s)$
Resistor	R
Inductor	sL
Capacitor	$1/sC$

* Assuming zero initial conditions

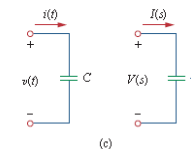
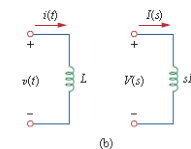
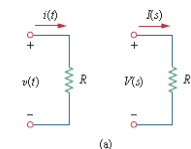


Figure 16.3 Time-domain and s-domain representations of passive elements under zero initial conditions.


Ex. RL Circuit:

Using KVL:

$$I(s)(R + sL) - LI_0 - \frac{V_0}{s} = 0$$

or
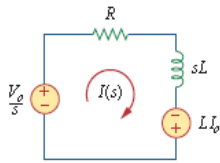
$$I(s) = \frac{LI_0}{R + sL} + \frac{V_0}{s(R + sL)} = \frac{I_0}{s + R/L} + \frac{V_0/L}{s(s + R/L)}$$



using partial fraction and rearranging the equation:

$$I(s) = \frac{I_0}{s + R/L} + \frac{V_0/R}{s} - \frac{V_0/R}{(s + R/L)}$$

The inverse Laplace transform of this gives

$$i(t) = \left(I_0 - \frac{V_0}{R} \right) e^{-t/\tau} + \frac{V_0}{R}, \quad t \geq 0$$


If $I_0 = 0$,

$$i(t) = \frac{V_0}{R} (1 - e^{-t/\tau}), \quad t \geq 0, \quad \tau = \frac{L}{R}$$

* Ex. RC Circuits:

KCL:
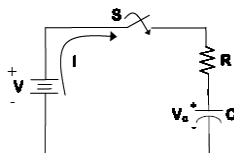
$$\frac{V - V_c}{R} = C \frac{dV_c}{dt} \text{ or } RC \frac{dV_c}{dt} + V_c = V$$



Rearranging:

$$V = V_c + RC \frac{dV_c}{dt}$$

Using Laplace table:

$$\frac{V}{s} = V_c(s) + RC(sV_c(s) - V_c(0)) \longrightarrow V_c(s) = \frac{V}{s} - \frac{V - V_c(0)}{\left(s + \frac{1}{RC} \right)} \longrightarrow V_c = V - [V - V_c(0)] e^{-\frac{t}{RC}}$$

Ex. LC Circuits:

Read section 2.3