

Simple Switching Transients

Note Title

2/15/2014


① Energizing a capacitor bank:

* L calculation:

$$MVA_{3\phi} = \frac{V_{LL}^2}{X_L}$$

$$X_L = \frac{V_{LL}^2}{MVA_{3\phi}} = \frac{(115k)^2}{800 MVA} = 16.53 \Omega$$
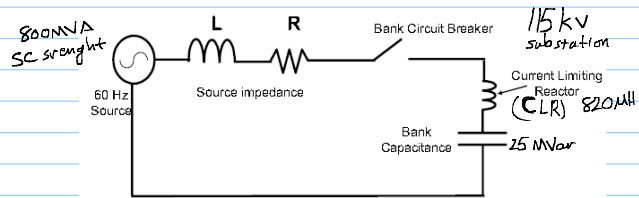
$$L = \frac{X_L}{2\pi f} = \frac{16.53}{377} = 43.85 \text{ mH}$$



* C calculation:

$$Mvar_{3\phi} = \frac{V_{LL}^2}{X_C}$$


$$X_C = \frac{V_{LL}^2}{Mvar_{3\phi}} = \frac{(115k)^2}{25M} = 529 \Omega$$

$$C = \frac{1}{2\pi f X_C} = \frac{1}{(377)(529)} = 5.01 \mu F$$

* Oscillation frequency calculation:

$$f = \frac{1}{2\pi \sqrt{LC}} = \frac{1}{2\pi \sqrt{(820\mu + 43.85m) * 5.01\mu}}$$

$$= 336 \text{ Hz}$$

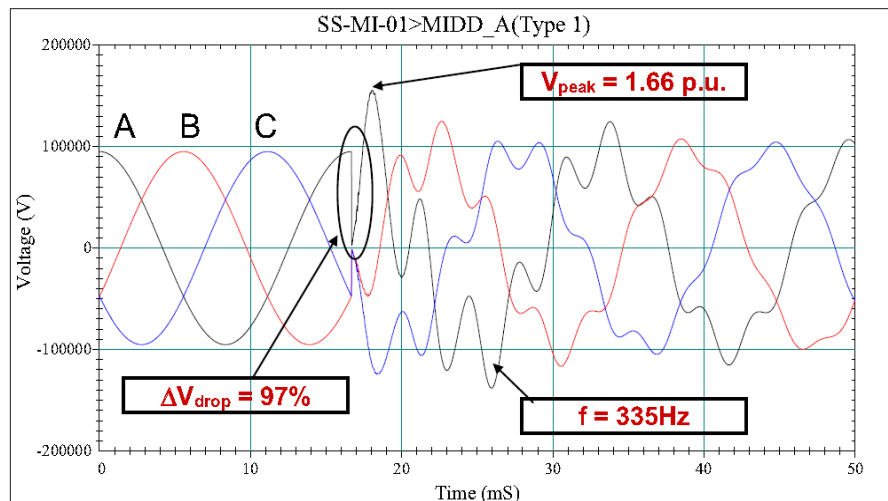

② Energizing transmission cable:

* L calculation:

$$MVA_{3\phi} = \frac{V_{LL}^2}{X_L}$$

$$X_L = \frac{V_{LL}^2}{MVA_{3\phi}} = \frac{(345k)^2}{3035} = 39.2 \Omega$$


$$L = \frac{X_L}{2\pi f} = \frac{39.2}{377} = 104 \text{ mH}$$

* C calculation:

$$Mvar_{3\phi} = \frac{V_{LL}^2}{X_C}$$

$$X_C = \frac{V_{LL}^2}{Mvar} = \frac{(345k)^2}{670 \text{ Mvar}} = 177.6 \Omega$$

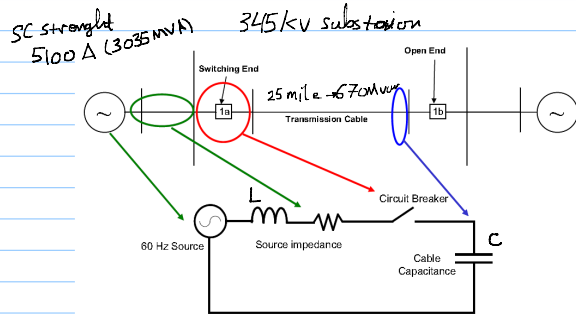
$$C = \frac{1}{2\pi f X_C} = \frac{1}{(377)(177.6)} = 14.93 \mu\text{F}$$



* Oscillation frequency calculation:

$$f = \frac{1}{2\pi \sqrt{LC}} = \frac{1}{2\pi \sqrt{(104 \text{ m})(14.93 \mu)}} = 128 \text{ Hz}$$

Source End Voltage

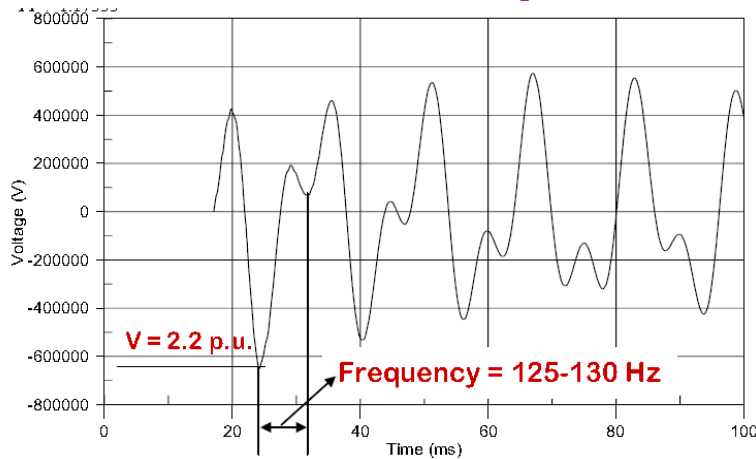


③ Energizing back-to-back capacitor bank:

6500 A SC strength Level at the CB (115kV)

* L Calculation:

$$L_{eq} = L_{CLR1} + L_{CLR2}$$

$$= 280 \mu H + 820 \mu H = 1100 \mu H$$

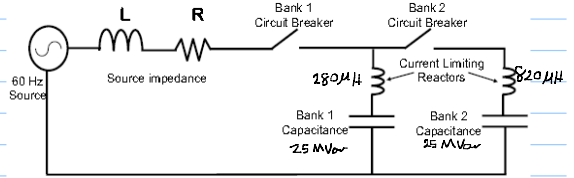


* C Calculation:

$$X_c = \frac{1}{2\pi f C} = \frac{V_{LL}^2}{MVar} = 529 \Omega$$

$$C = \frac{1}{2\pi f X_c} = \frac{1}{(377)(529)} = 5.01 \mu F$$

$$C_{eq} = \frac{C_1 C_2}{C_1 + C_2} = 2.505 \mu F$$

* Oscillation frequency calculation:
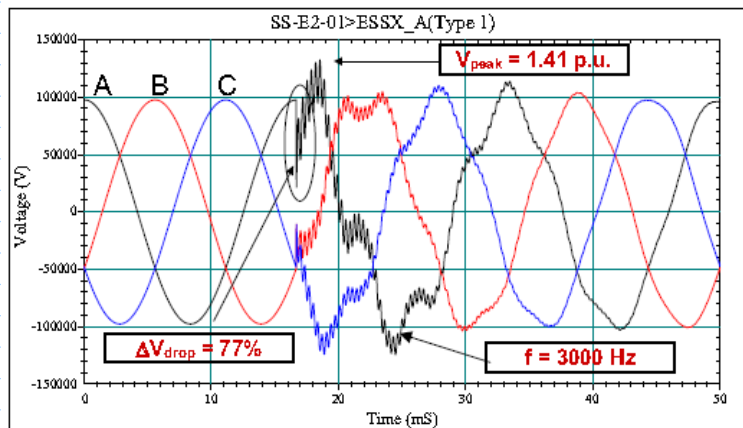
$$f = \frac{1}{2\pi \sqrt{(1100 \mu)(2.505 \mu)}} = 3030 \text{ Hz}$$


④ Clearing a fault

Read sec. 3.3