

Charging and Discharging Capacitors

Charging capacitors:

When a capacitor is charged through a resistor from a DC power supply, the charge on the capacitor and the voltage across the capacitor will increase with time. The voltage V , as a function of time is given by:

$$V = V_0(1 - e^{-t/RC})$$

Where: V_0 is the charging voltage.

After a time $t = RC$ (**one time constant**), the voltage across the capacitor has increased to **63%** its maximum value ($V = 0.63 V_0$ at $t=RC$).

Take the reading of the electrometer (voltage across the capacitor) at each second and tabulate your results as follows:

<i>Time (s)</i>	<i>Voltage (V)</i>
0	
10	
20	
30	
40	
50	
60	
70	
80	
90	
100	
110	
120	

<i>Time (s)</i>	<i>Voltage (V)</i>
130	
140	
150	
160	
170	
180	
190	
200	
210	
220	
230	
240	
250	

$$V_0 =$$

$$0.63 V_0 =$$

$$\tau_{theoretical} = RC =$$

Plot a graph of the voltage **V (y axis) vs. Time t (x axis)** and from the graph find the value of the time constant corresponding to $0.63 V_0$

$$\tau_{experimental} =$$

Discharging capacitors:

When a capacitor is discharged through a resistor, the charge on the capacitor and the voltage across the capacitor will decrease with time. The voltage V , as a function of time is given by:

$$V = V_0 e^{-t/RC}$$

Where: V_0 is the charging voltage.

After a time $t = RC$ (**one time constant**), the voltage across the capacitor has decreased to **37%** its maximum value ($V = 0.37 V_0$ at $t=RC$).

Take the reading of the electrometer (voltage across the capacitor) at each second and tabulate your results as follows:

<i>Time (s)</i>	<i>Voltage (V)</i>
0	
10	
20	
30	
40	
50	
60	
70	
80	
90	
100	
110	
120	

<i>Time (s)</i>	<i>Voltage (V)</i>
130	
140	
150	
160	
170	
180	
190	
200	
210	
220	
230	
240	
250	

$V_0 =$

$0.37 V_0 =$

$\tau_{theoretical} = RC =$

Plot a graph of the voltage **V (y axis) vs. Time t (x axis)** and from the graph find the value of the time constant corresponding to $0.63 V_0$

$\tau_{experimental} =$