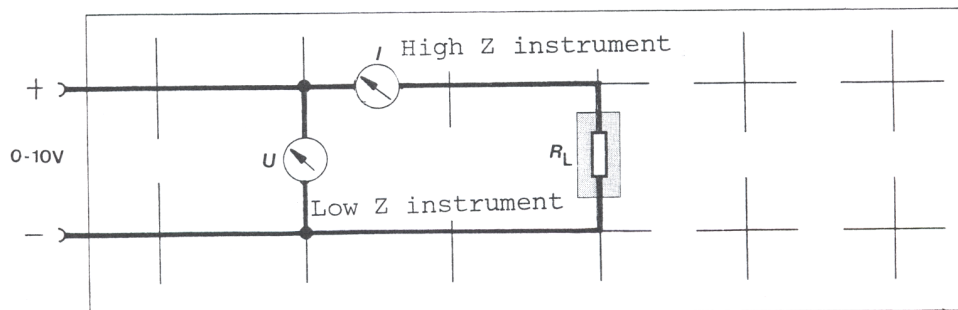


Ohm's Law

Aim of the experiment

Measuring the currents through different load resistors R_L as a function of the applied voltage

Circuit



Equipment and components

- 1 Rastered socket panel
- 1 Resistor R_{L1} , 10 k Ω
- 1 Resistor R_{L2} , 100 k Ω
- 1 Resistor R_{L3} , 470 k Ω
- 1 Low Z instrument
- 1 high Z instrument
- 1 D.C. power supply unit
- Bridging plugs
- Connecting leads

Conducting the experiment

1. Assemble the measuring circuit.
2. Measure the current for three different resistors R_L as a function of the applied voltage (voltage steps of 1 V), and arrange the measured values in a table. Then draw a graph based on the measured values. Use a high Z instrument when measuring the current.
3. From the graph find the value of the resistor R_L .

U/V	I/mA		
	10 k Ω	100 k Ω	470 k Ω

Slope =


R_L =

Series Connection of Resistors

Aim of the experiment

Measurement of the total voltage U and the voltage drops U_1 , U_2 , and U_3 across the resistors and the current I flowing through the circuit.

Circuit

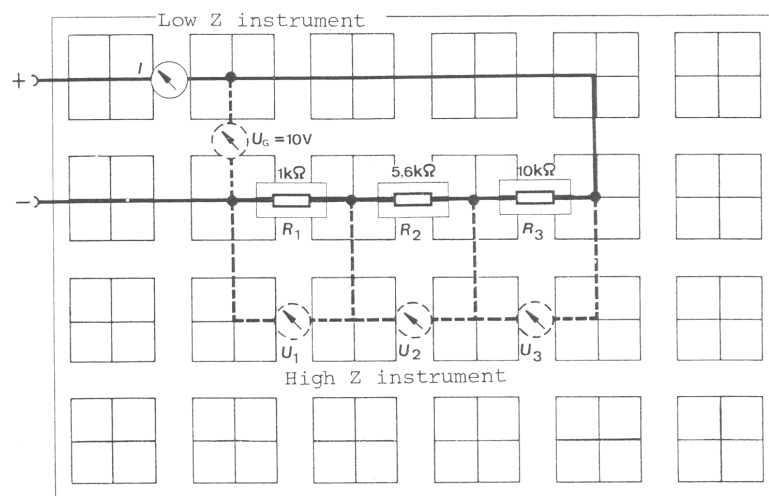

Equipment and components

- 1 Rastered socket panel
- 1 Resistor R_1 , 1 k Ω
- 1 Resistor R_2 , 5.6 k Ω
- 1 Resistor R_3 , 10 k Ω
- 1 Low Z instrument
- 1 high Z instrument
- 1 D.C. power supply unit
- Bridging plugs
- Connecting leads

Conducting the experiment

1. Assemble the circuit and connect a multi-meter in series for measurement of the current.
2. Adjust $U_G = 10 \text{ V}$. Measure all voltages with the high Z instrument. Then measure, one after the other, the voltage drops U_1 , U_2 and U_3 across the corresponding resistors R_1 , R_2 and R_3 .

Total current $I_G =$

Voltage $U_G =$

Resistor	Voltage
$R_1 = 1 \text{ k}\Omega$	
$R_2 = 5.6 \text{ k}\Omega$	
$R_3 = 10 \text{ k}\Omega$	

Exercise

- Calculate the total resistance R_G from the law of series connection of resistors; $R_G = R_1 + R_2 + R_3$.

$R_G =$

- Calculate the total voltage across the resistors $U_{\text{total}} = U_1 + U_2 + U_3$ and compare it with U_G .


$U_{\text{total}} =$

Parallel Connection of Resistors

Aim of the experiment

Measurement of the current I and the voltage U in a circuit and a number of circuit variations.

Circuit

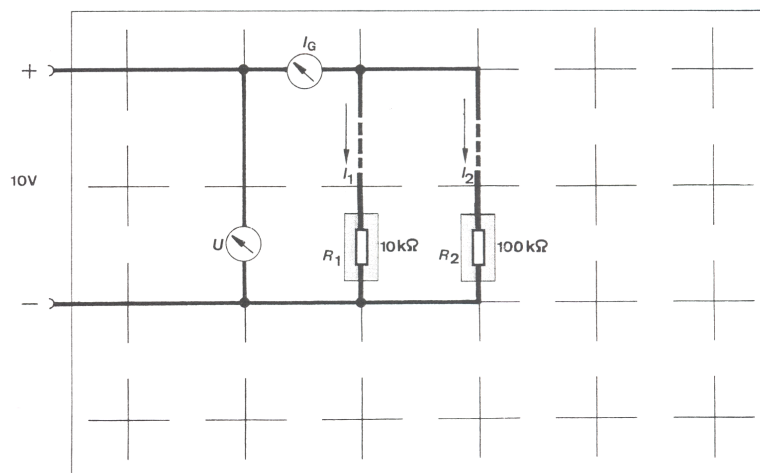

Equipment and components

1 Rastered socket panel

1 Resistor R_1 , 10 kΩ

1 Resistor R_2 , 100 kΩ

1 Low Z instrument

1 high Z instrument

1 D.C. power supply unit

Bridging plugs

Connecting leads

Conducting the experiment

3. Assemble the circuit step by step (the single stages are indicated by dotted lines).
4. Measure the current I and the voltage U as given in the table below.

Circuit with	U/V	I/mA	R/kΩ
R_1			
R_2			
$R_G = \frac{R_1 \times R_2}{R_1 + R_2}$			

Exercise

- Enter the resistance values into the table for each of the circuits.
- Calculate the total resistance R_G of the circuit from the law of parallel

connection of resistors; $\frac{1}{R_G} = \frac{1}{R_1} + \frac{1}{R_2}$,

$$R_G = \frac{R_1 \times R_2}{R_1 + R_2}$$

$R_G =$

- Calculate the total current using 1st law of Kirchhoff: $I_G = I_1 + I_2$.

$I_G =$