FREQUENCY RESPONSE

Frequency response *⇒* **divided into three frequency ranges**

- ∽ M.F.R ⇒ capacitances ⇒ can be neglected
- \bigcirc L.F.R \Rightarrow series capacitances $C_C \Rightarrow$ must be considered

Midfrequency Gain

<u>FET</u>



(a) FET

FET. Since $R_G \ge R_s$, $V_{gs} = V_s$ and R_G can be omitted in most cases. If, for convenience, we represent the parallel combination of R_D and R_L by R_o , the output voltage is

$$V_o = -g_m V_{gs}(R_D || R_L) = -g_m V_s R_o$$
(14-3)

and the midfrequency voltage gain is

$$A_{VO} = \frac{V_o}{V_s} = -g_m R_o$$
 (14-4)

where subscripts V and O are for "voltage" and "midfrequency." The negative sign indicates a 180° phase reversal of the output signal with respect to the input.

EXAMPLE 1

A JFET with $g_m = 2000 \ \mu\text{S}$, $C_{gs} = 20 \text{ pF}$, and $C_{gd} = 2 \text{ pF}$ is used in an *RC*-coupled amplifier with $R_G = 1 \ \text{M}\Omega$, $R_S = 2 \ \text{k}\Omega$, and $R_D = 5 \ \text{k}\Omega$. Signal source resistance $R_s =$ $1 \ \text{k}\Omega$ and load resistance $R_L = 5 \ \text{k}\Omega$. Coupling capacitance $C_{C1} = C_{C2} = 1 \ \mu\text{F}$ and $C_S = 20 \ \mu\text{F}$; the load capacitance (including wiring) $C_L = 20 \ \text{pF}$. Predict the voltage gain V_o/V_s at $\omega = 10^4 \ \text{rad/s}$ ($f = 1590 \ \text{Hz}$).



(a) General model



Figure 14.7 Midfrequency simplification.

At the given frequency,

$$1/\omega C_s = 1/10^4 \times 20 \times 10^{-6} = 5 \Omega$$

Therefore, $R_s = 2000 \Omega$ is effectively shorted and the model is as shown in Fig. 14.7a.

Since C_{C1} and C_{C2} are effectively in series with R_G and R_L , 1 M Ω and 5 k Ω respectively, the reactances

$$1/\omega C_{c} = 1/10^{4} \times 10^{-6} = 100 \ \Omega$$

are negligibly small (Eq. 14-1).

With C_{C1} and C_{C2} omitted, C_L is in parallel with $R_o = R_D || R_L = 2500 \ \Omega$ and C_{gs} is in series with R_s . The reactances

$$1/\omega C_L = 1/\omega C_{es} = 1/10^4 \times 20 \times 10^{-12} = 5 M\Omega$$

are so large that C_L and C_{gs} can be omitted.

The reactance

$$1/\omega C_{gd} = 1/10^4 \times 2 \times 10^{-12} = 50 \text{ M}\Omega$$

is so large that a negligible current will flow in C_{gd} .

In other words, 1590 Hz is in the "midfrequency" range of this amplifier and the model of Fig. 14.7b is appropriate. The midfrequency gain (Eq. 14-4) is

$$A_{VO} = -g_m R_o = -2000 \times 10^{-6} \times 2500 = -5$$

Conclusion: Working from the simplified model, calculation of the midfrequency gain is straightforward.

<u>BJT</u>

$$\frac{R_B + R_E}{\beta} \cong \frac{R_B}{\beta} \ll R_E \tag{12-12}$$





(b) BJT

🔶 The ideal condition 🖟

$$r_{\pi} \ll R_B \ll \beta R_E$$

b The circuit stable and simple to analyze

If R_B is neglected in Fig. 14.6b, r_{π} and R_s constitute a voltage divider the output voltage is

$$V_o = -g_m V_{be}(R_C || R_L) = -g_m \frac{r_\pi}{r_\pi + R_s} V_s R_o = -\beta \frac{V_s}{r_\pi + R_s} R_o \qquad (14-5)$$

Ch(6) Small-Signal Amplifiers

and the midfrequency voltage gain is

$$A_{VO} = \frac{V_o}{V_s} = -\frac{r_{\pi}}{r_{\pi} + R_s} g_m R_o = -\beta \frac{R_o}{r_{\pi} + R_s}$$
(14-6)

Performance of these one-stage amplifiers is influenced by the characteristics of the source (R_s) and the load (R_L) . In the multistage amplifiers discussed later, the source and the load for each stage are other similar stages.

Practice Problem 14-2

Low-Frequency Response

Below the midfrequencies

The susceptances of the parallel capacitors neglibly small \oint

$$Z_{\text{par}} = \frac{1}{\sqrt{(1/R)^2 + (\omega C)^2}} = \frac{R}{\sqrt{1 + (\omega CR)^2}}$$

The reactance of the coupling capacitance increasity <u>important</u>

$$Z_{\rm ser} = \sqrt{R^2 + (1/\omega C)^2} = R\sqrt{1 + (1/\omega CR)^2}$$

Coupling Capacitors

The general model \Rightarrow reduced to \Rightarrow simpler low frequency model



Provide a strain and a straight of the str

 $\clubsuit R_B \Rightarrow \text{omitted} \Rightarrow \text{large compared to } r_{\pi}$ $FET \overset{*}{\ast} BJT \Rightarrow \text{models are analogous} \Rightarrow \text{one analysis} \Rightarrow \text{serve}$ for both



(a) General circuit

(b) Thévenin form

(c) Norton form

• The general circuit \Rightarrow (a) \Rightarrow replaced by \clubsuit

Thevenin form ⇒ input circuit

OR

Norton form is output circuit

• The two forms \Rightarrow are equivalents $\Rightarrow C_C \Rightarrow$ effectively shorted

The output of ⇒ Thevenin circuit ↓

$$\mathbf{V} = \mathbf{V}_O = \frac{R}{R + R_T} \mathbf{V}_T$$

At low frequencies where C_c is significant, the output of the Thévenin circuit is

$$\mathbf{V}_{L} = \frac{R}{R + R_{T} - j\frac{1}{\omega C_{C}}} \mathbf{V}_{T} = \frac{\frac{R}{R + R_{T}} \mathbf{V}_{T}}{1 - j\frac{1}{\omega C_{C}(R + R_{T})}} = \frac{\mathbf{V}_{O}}{1 - j\frac{1}{\omega C_{C}(R + R_{T})}}$$
(14-8)

The low-frequency output V_L related to the midfrequency output by ⇒ complex factor dependent on ↓
frequency ♣ RC product
As frequency ⇒ decreased ⇒ large fraction of ⇒ V_T ⇒ appears ⇒ across C_C ⇒ V at the output ⇒ reduced
The cutoff ⇒ half - power frequency ↓

$$V_L/V_o = |1/(1 - j1)| = 1/\sqrt{2}$$

Defined by

$$\omega_{\rm co} = \frac{1}{C_C(R + R_T)}$$

Ch(6) Small-Signal Amplifiers

➡ The behavior of ⇒ FET # BJT ⇒ predicted at lowfrequency

•
$$\omega_{11} = \frac{1}{C_{C1}(R_s + R_G)}$$
 or $\omega_{11} = \frac{1}{C_{C1}(R_s + r_\pi)}$

 \blacksquare The input voltage \Rightarrow $V_{gs} \stackrel{*}{\ast} V_{be} \Rightarrow$ down to 70% of V_o at \downarrow

$$\omega_{12} = \frac{1}{C_{C2}(R_D + R_L)}$$
 or $\omega_{12} = \frac{1}{C_{C2}(R_C + R_L)}$

The output voltage ⇒ V_o ⇒ down to 70% of g_m V_{gs} R_o ** g_m V_{be} R_o ⇒ the corresponding amplifier gain ⇒ reduced
The overall ⇒ low-frequency voltage gain ⇒ for ↓
FET

$$\mathbf{A}_{L} = \mathbf{A}_{O} \cdot \frac{1}{1 - j \frac{1}{\omega C_{C1}(R_{s} + R_{G})}} \cdot \frac{1}{1 - j \frac{1}{\omega C_{C2}(R_{D} + R_{L})}}$$

P The relative gain for \Rightarrow BJT **OR** FET

Ch(6) Small-Signal Amplifiers



igstarrow To predict the behavior of a given circuit determine artheta

 $\bigcirc \quad \omega_{11} \stackrel{*}{*} \omega_{12} \stackrel{r}{\Rightarrow}$ the higher is

🌩 To design a circuit calculate 사

*∽ C*_{*C*1} **** *C*_{*C*2}

EXAMPLE 2

In the circuit of Fig. 14.8b, $R_s = 1 \text{ k}\Omega$, $r_{\pi} = 2 \text{ k}\Omega$, $R_C = 4.5 \text{ k}\Omega$, $R_L = 9 \text{ k}\Omega$, $g_m = 60 \text{ mS}$, and $C_{C1} = C_{C2} = 1 \mu\text{F}$. Predict the midfrequency voltage gain and the lower cutoff frequency. At midfrequencies the capacitors are effectively shorted and

$$A_{VO} = -\frac{r_{\pi}}{r_{\pi} + R_s} g_m(R_C \| R_L)$$

$$= -\frac{2}{2+1} (0.06)(4500 || 9000) = -120$$

The lower cutoff frequencies are

$$\omega_{11} = \frac{1}{C_{C1}(R_S + r_{\pi})} = \frac{1}{10^{-6} \times 3000} = 333.3 \text{ rad/s}$$
$$\omega_{12} = \frac{1}{C_{C2}(R_C + R_L)} = \frac{1}{10^{-6} \times 13,500} = 74.1 \text{ rad/s}$$

Therefore, the lower cutoff frequency of the amplifier is

 $\omega_{12} = 333.3 \text{ rad/s}$ or $f_{12} = 333.3/2\pi = 53 \text{ Hz}$

<u>H-W P.P 14-3</u>