

Application Specific Circuits

Section 06

Contents



- **Generators**
 - Square, Sine, Triangle, Pulse Generators
- **Converters**
 - AC/DC
 - Analog/Digital
- **Protection Circuits**
 - Voltage/Current Limiter
 - Reverse Polarity
 - ESD Protection

Contents

- Math Circuits
 - General adders (mixers)
 - Integrators, Differentiator
 - Transfer Functions
- Filters
 - Low/High Pass Filters
 - Band Pass/Stop Filters

Format

1. Circuits Schematic
2. Function
3. Usage
4. Design Equations
5. Design Example

EE251 Application Specific Circuits

Square Wave Generator

Function:	generates square wave at certain frequency
Use:	transmitters/receivers, digital communications
Design Equations:	$f \approx \frac{1}{2.2 RC}$

Example:
 A square wave signal is needed with 120 kHz, ±10V peak voltages.
Solution:
 We assume a capacitor of 0.1 μF. The resistors of the circuit will be:

$$f \approx \frac{1}{2.2 RC} \rightarrow R \approx \frac{1}{2.2 C f} = 37.94 \Omega$$
 which is in a good value range. For the op-amp, use LM741 and supply it with ±11V to guarantee ±10V.



© 2010 King Abdulaziz University
EE-251 Course Notes
Electrical & Computer Engineering Department

Note!!



- Some are Conceptual Designs
- Consider Ready-Made IC's available
- Or even PCBs

Op-Amp

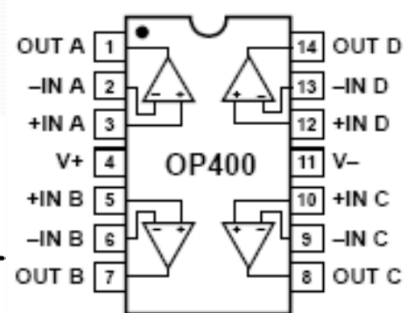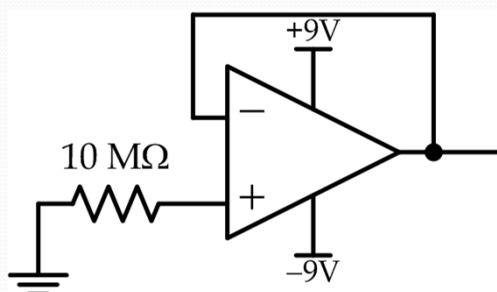- Needs Dual Power Supply
- Multiple op-amps in one IC



(1) Square Wave Generator

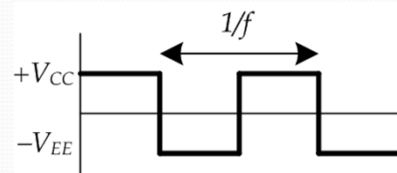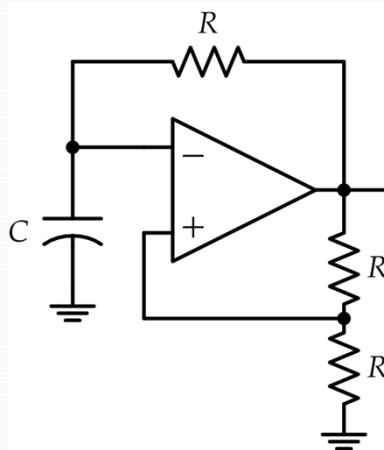



$$f \approx \frac{1}{2.2 RC} \text{ Hz}$$

Electrical & Computer Engineering

King Abdulaziz University

Slide 149

(2) Pulse Generator

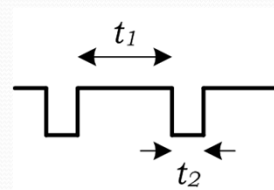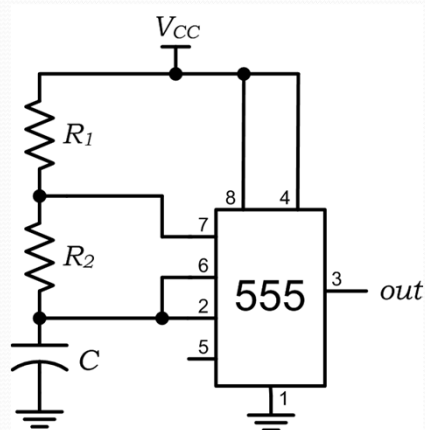

$$t_1 = \ln 2 \times (R_1 + R_2) \times C$$


$$t_2 = \ln 2 \times R_2 \times C$$

Electrical & Computer Engineering

King Abdulaziz University


Slide 150

(3) AC/DC Converter

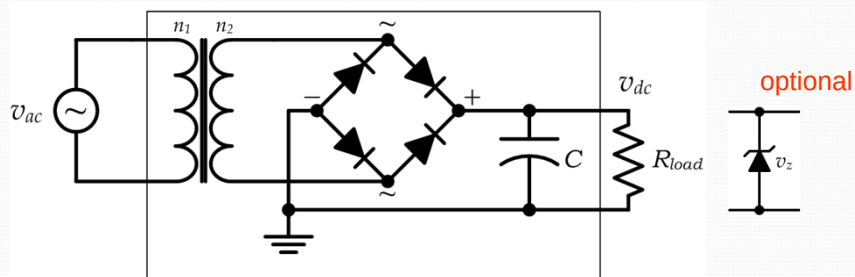

$$v_{dc} = v_{ac} \frac{n_2}{n_1} - 2 \cdot V_D$$
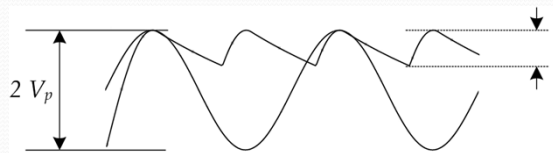
$$r \approx \frac{v_{dc}}{2 \cdot f \cdot C \cdot R_{load}} V$$



Electrical & Computer Engineering

King Abdulaziz University

Slide 151

Example

- Design an AC/DC converter to:
 - Produce 8.4 VDC
 - From the mains supply of 220Vrms
 - With Ripples of 1%
 - Diodes available $V_D = 0.6V$
 - Maximum load expected 2kΩ

$$v_{dc} = V_p \frac{n_2}{n_1} - 2 \cdot V_D$$

$$r \approx \frac{v_{dc}}{2 \cdot f \cdot C \cdot R_{load}}$$

Electrical & Computer Engineering

King Abdulaziz University

Slide 152

Solution

$$v_{dc} = 8.4 \quad V$$

$$V_D = 0.6 \quad V$$


$$V_p = \sqrt{2} \times 220 = 311V \quad \Rightarrow \quad \frac{n_2}{n_1} = 0.031 \approx \frac{1}{32}$$

$$r = 8.4 \times \frac{1}{100} = 84mV \quad C = 417 \quad \mu F$$

$$R_{load} = 2 \quad k\Omega$$


$$f = 60 \quad Hz$$

Clipping Protection

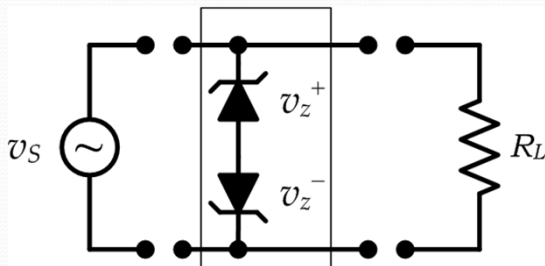

$$V_u = v_z^+ + v_f^-$$

$$V_l = v_z^- + v_f^+$$

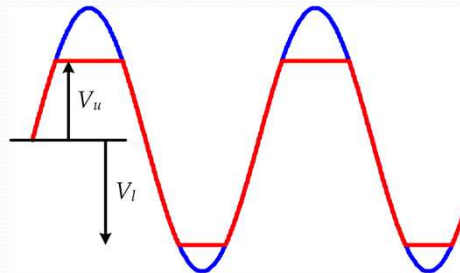


ESD Protection

- Simple Parallel Discharging Zener Diode
- Special Diodes for High speed Lines

+ve Signal Only



$\pm v$ Signal


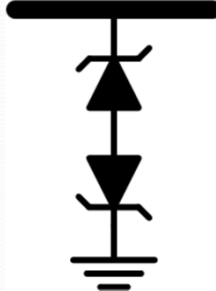


Electrical & Computer Engineering


King Abdulaziz University

Slide 155

Reverse Polarity Protection

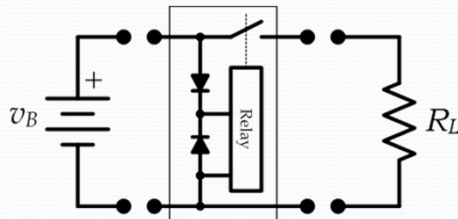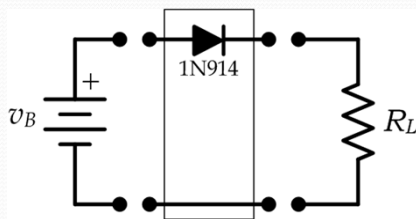

$$I_L \approx \frac{v_B}{R_L}$$

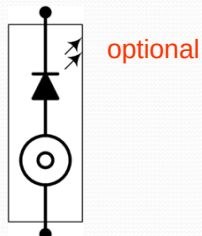


Electrical & Computer Engineering

King Abdulaziz University

Slide 156

General Adder (Mixer)

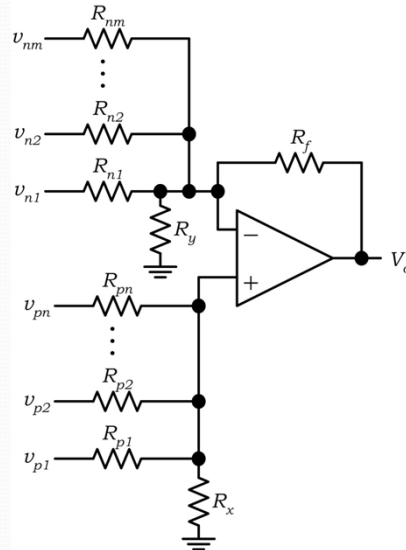

$$V_o = \sum_{i=1}^n A_i v_{pi} - \sum_{i=1}^m B_i v_{ni}$$

$$A_i = \frac{R_f}{R_{pi}}, B_i = \frac{R_f}{R_{ni}}$$

$$\text{Let } A = \sum A_i, B = \sum B_i, C = A - B - 1$$


$$\begin{cases} C \geq 0 & R_x = \infty & R_y = \frac{R_f}{C} \\ C < 0 & R_x = -\frac{R_f}{C} & R_y = \infty \end{cases}$$

Electrical & Computer Engineering

King Abdulaziz University

Slide 157

Integrator

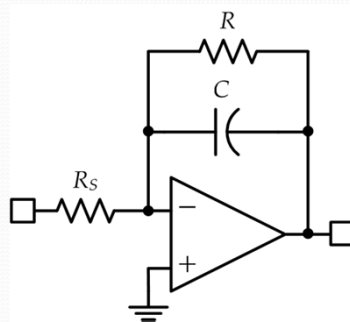

$$v_o = \begin{cases} -\frac{R}{R_s} \times v_s(t) & f \leq f_0 \\ -\frac{1}{R_s C} \int v_s(t) dt & f > f_0 \end{cases}$$


$$f_0 = \frac{1}{2\pi RC} \text{ Hz}$$

Electrical & Computer Engineering

King Abdulaziz University

Slide 158





Differentiator

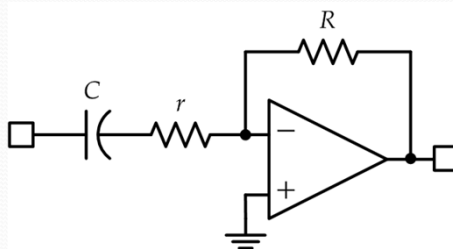

$$v_o = \begin{cases} -RC \frac{d}{dt} v_s(t) & f \leq f_0 \\ -\frac{R}{r} \times v_s(t) & f > f_0 \end{cases}$$

$$f_0 = \frac{1}{2\pi rC} \text{ Hz}$$

Filters

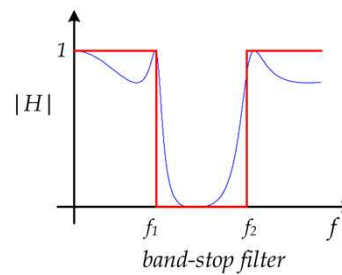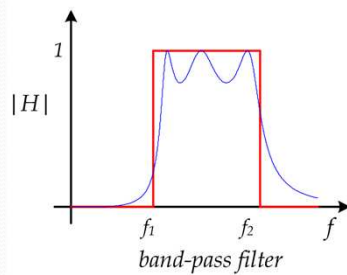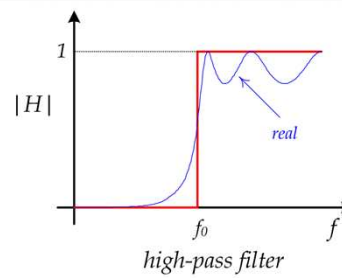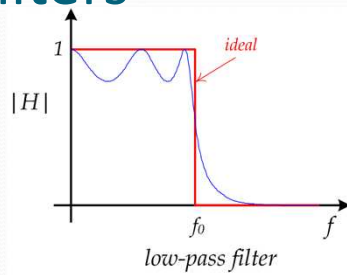

Process Check



- What circuits did you face in your field?
- Do you need more details?
- Where to find more Designs?

