
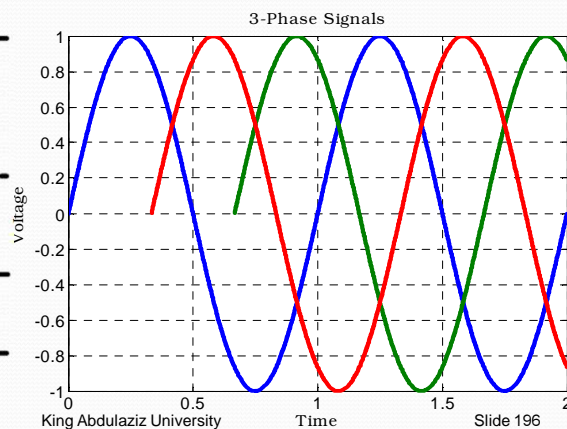


# 3-Phase Systems

## Section 09
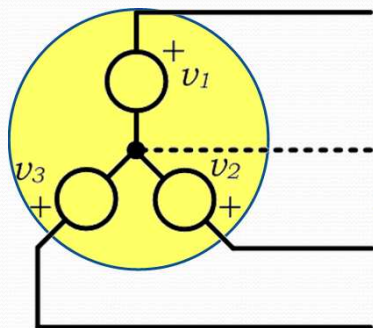
### 3-Phase Generators

- Method for transmitting alternating power
- Three conductors carrying three alternating currents with  $360/3=120^\circ$  shift between them



Electrical & Computer Engineering


King Abdulaziz University

Slide 196

# Why 3 $\phi$ System?

- Multi-Phase Generation
  - constant power generation all the time
  - cost effective
- Usage
  - 1 $\phi$  of each phase at homes
  - 3 $\phi$  loads at industry

# Vector Representation

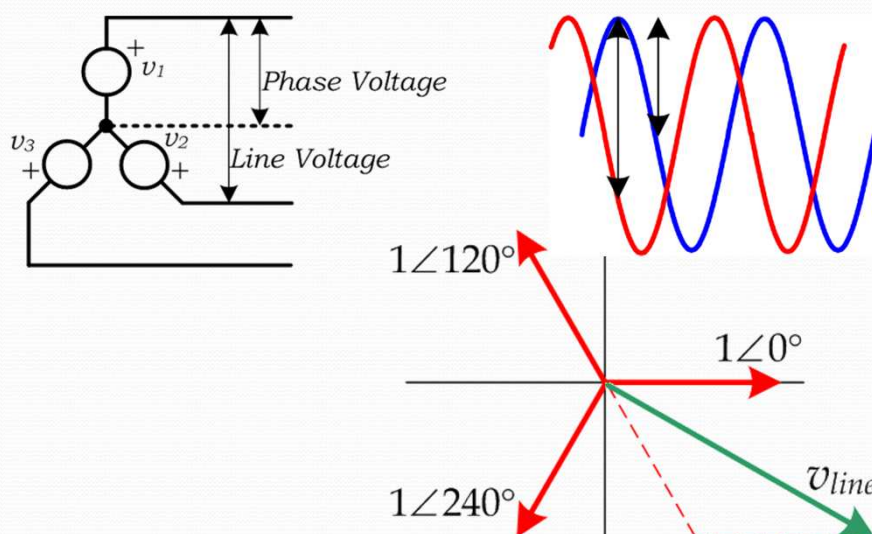

## Line Voltage



$$\begin{aligned}v_{12} &= v_1 - v_2 \\&= 1\angle 0^\circ - 1\angle 240^\circ \\&= 1 - (\cos 240 + j \sin 240) \\&= \frac{3}{2} + j \frac{\sqrt{3}}{2}\end{aligned}$$

$$v_{12} = \sqrt{3}\angle 30^\circ$$

$$v_{23} = \sqrt{3}\angle -90^\circ$$


$$v_{31} = \sqrt{3}\angle 150^\circ$$

## Examples



- If a phase voltage is 120V
  - Line Voltage =  $120 \cdot \sqrt{3} = 208V$
- If a line voltage is 220V
  - Phase Voltage =  $220 / \sqrt{3} = 127V$

## Load Distribution

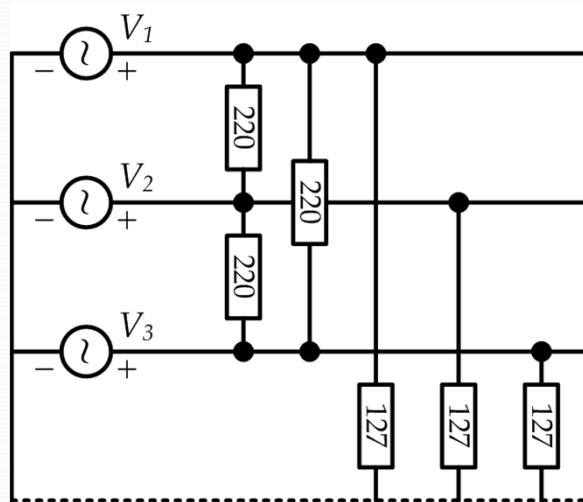


Electrical & Computer Engineering

King Abdulaziz University

Slide 201

## Star-Start Connection

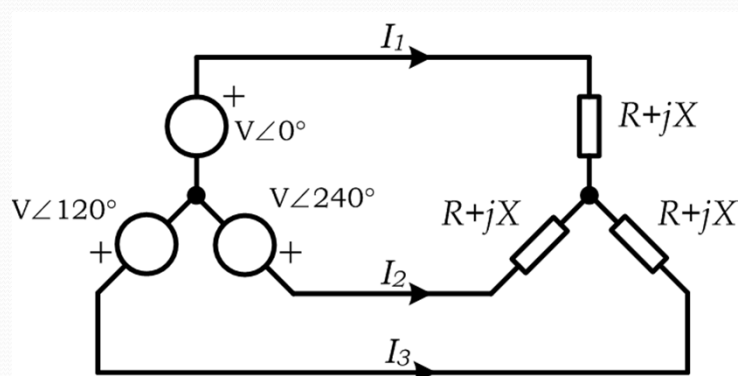


Electrical & Computer Engineering

King Abdulaziz University

Slide 202

## Star-Delta Connection

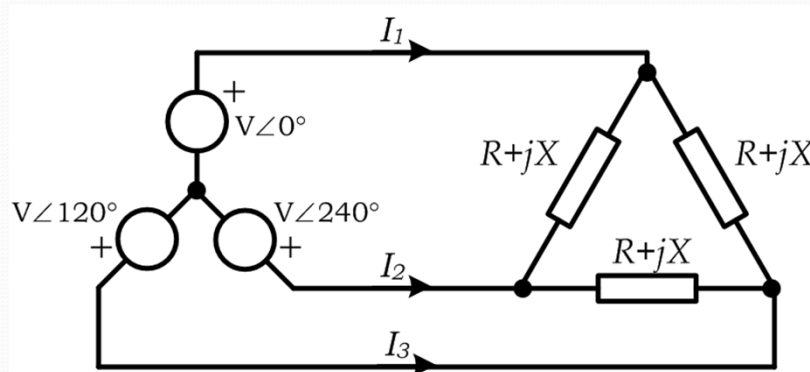

Electrical & Computer Engineering

King Abdulaziz University

Slide 203

## Power Factor (*pf*)



- Preferred Network when  $Q=0$
- Let the angle between Voltage and Current be  $\theta$

$$pf = \cos \theta = \begin{cases} 1 & \theta = 0^\circ \\ 0 & \theta = 90^\circ \end{cases}$$

Electrical & Computer Engineering

King Abdulaziz University

Slide 204



# Power Factor



- For a single load:

$$Z = R + jX_L$$


- The power factor can be expressed as:

$$pf = \frac{R}{\sqrt{R^2 + X_L^2}}$$
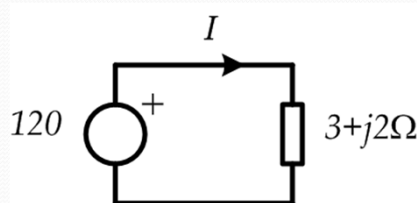
# Example



- What is the power factor of the circuit shown?




- Solution:

$$pf = \frac{R}{\sqrt{R^2 + X_L^2}} = \frac{3}{\sqrt{3^2 + 2^2}} = 0.832$$
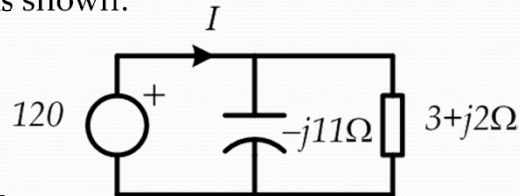
## Example

- Recalculate the power factor when a capacitor is added as shown:




- Solution:

$$Z_{eq} = (3 + j2) // (-j11) = 4.03 + j1.1\Omega$$

$$pf = 0.964$$

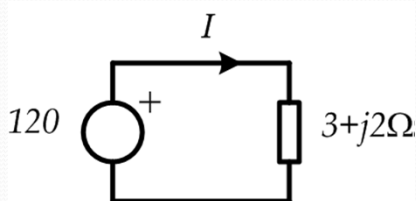
## Example

- Calculate the Power and the total Volt-Ampere (S)?



$$I = \frac{120}{3 + j2} = 33.3 \angle -34^\circ A$$


$$S = I^* \cdot V = 3310 + j2233 VA$$

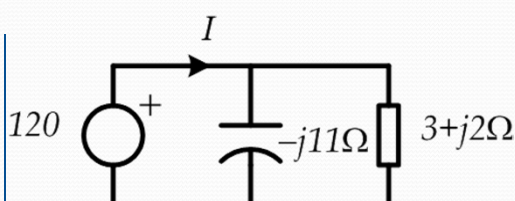

$$I = \frac{120}{4.03 + j1.1} = 28.7 \angle -15^\circ A$$

$$S = I^* \cdot V = 3327 + j891 VA$$

## Simulation

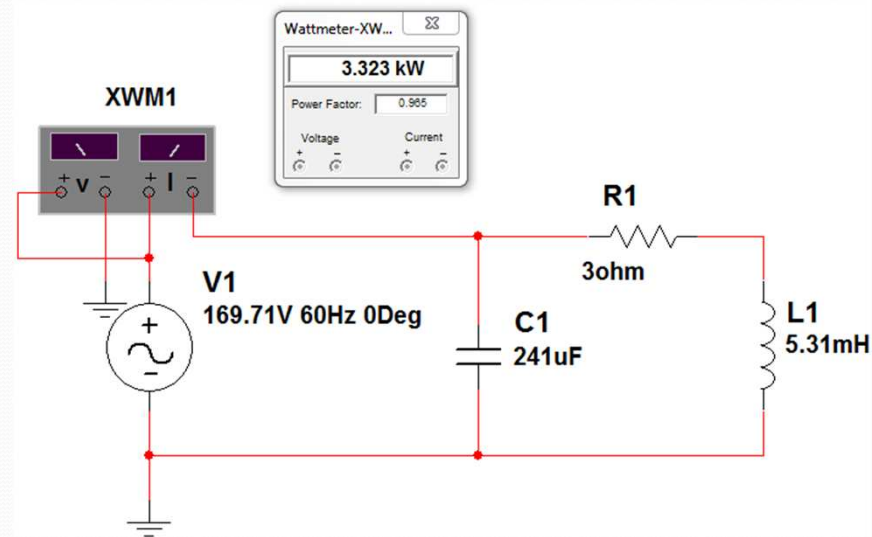

Electrical & Computer Engineering

King Abdulaziz University

Slide 209

## Power Factor Correction

- How much parallel Capacitance to improve  $pf$ ?

$$X_C = \left( X_L \cdot pf_{new} + R \cdot \sqrt{1 - pf_{new}^2} \right) \times \frac{pf_{new}}{pf_{new}^2 - pf_{old}^2}$$

- Example:

- $Z_L = 3 + j2\Omega$
- $pf_{new} = 0.964$

$$X_C = \left( 2 \times 0.964 + 3 \times \sqrt{1 - 0.964^2} \right) \times \frac{0.964}{0.964^2 - 0.832^2} = 11\Omega$$


Electrical & Computer Engineering

King Abdulaziz University

Slide 210



## Star-Start Connection

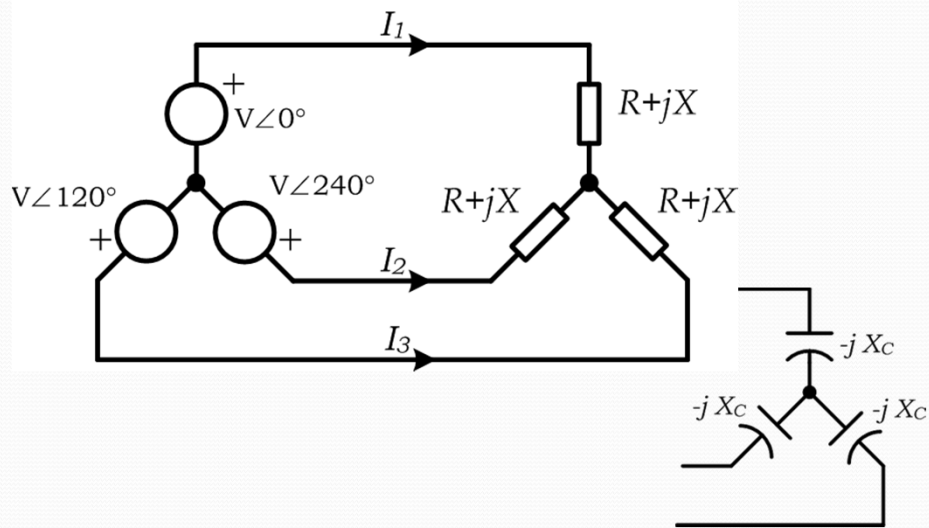


Electrical & Computer Engineering

King Abdulaziz University

Slide 211

## Star-Delta Connection

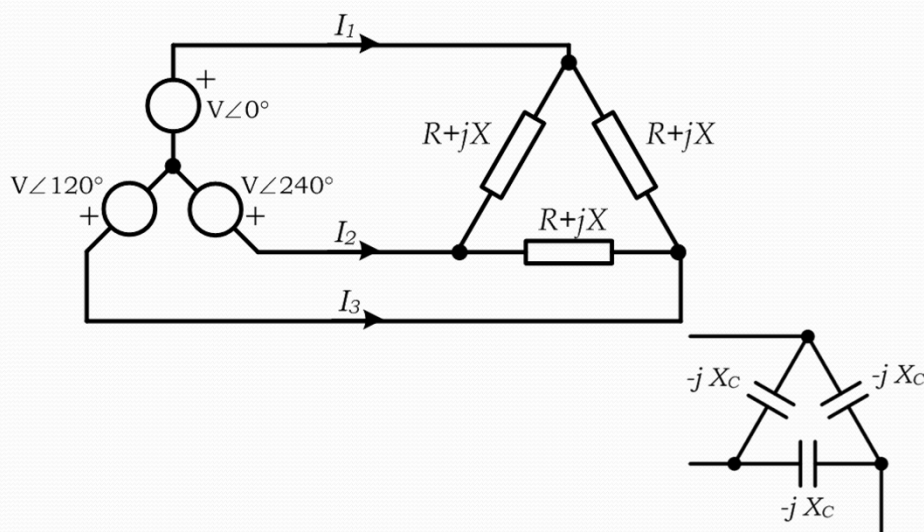

Electrical & Computer Engineering

King Abdulaziz University

Slide 212