

Behavior of Traveling Waves at Junctions

Note Title

2/19/2014

* Traveling waves (V_1, I_1) at junctions (discontinuity) are divided into two waves:

① Reflected Waves (Backward) (V_2, I_2)

② Refracted Transmitted waves (Forward) (V_3, I_3)


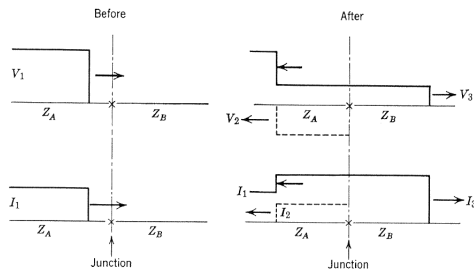


Fig. 9.7. Voltage and current waves being reflected and refracted at a junction between two lines.

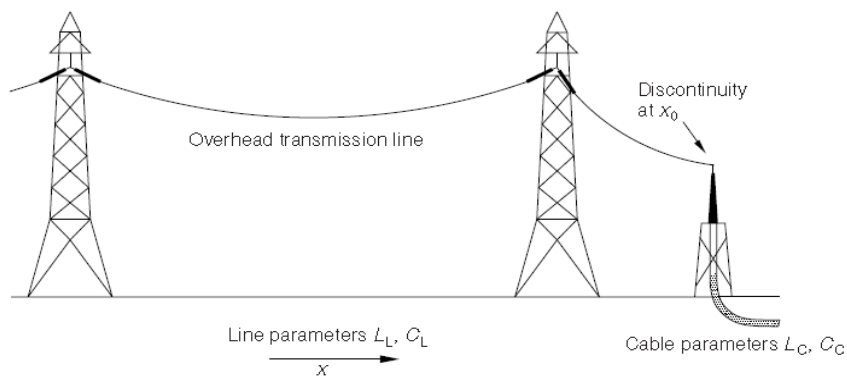* Junction (discontinuity): is a point where the characteristic impedance (Z) is unequal on the junction sides (e.g. $Z_A \neq Z_B$)



$$I_1 = \frac{V_1}{Z_A}, \quad I_2 = -\frac{V_2}{Z_A}, \quad I_3 = \frac{V_3}{Z_B}$$

* If the current and the voltage are continuous at the junction:

$$V_3 = V_1 + V_2 \quad \& \quad I_3 = I_1 + I_2$$

$$\frac{V_3}{Z_B} = \frac{V_1}{Z_A} - \frac{V_2}{Z_A}$$

$$V_2 \left(\frac{Z_B + Z_A}{Z_B Z_A} \right) = V_1 \left(\frac{Z_B - Z_A}{Z_B Z_A} \right) \implies V_2 = V_1 \left(\frac{Z_B - Z_A}{Z_B + Z_A} \right) = a V_1$$



where a is the reflection coefficient, $-1 \leq a \leq 1$

$$V_3 \left(\frac{Z_B + Z_A}{Z_B Z_A} \right) = \frac{2V_1}{Z_A}$$



$$\implies V_3 = \left(\frac{2Z_B}{Z_B + Z_A} \right) V_1 = b V_1$$

where b is the refraction coefficient, $a = 1 + b$


* Termination ($Z_1 > Z_2$)

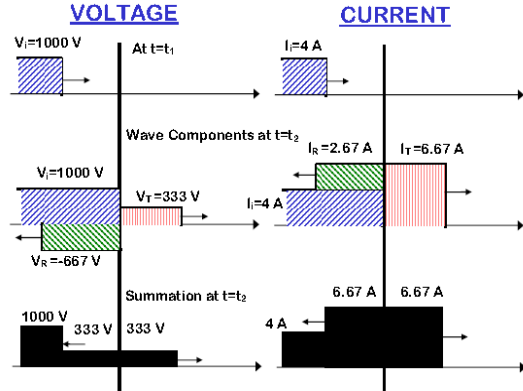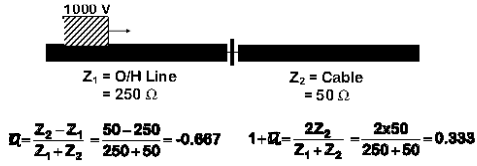


* Termination ($Z_1 < Z_2$):

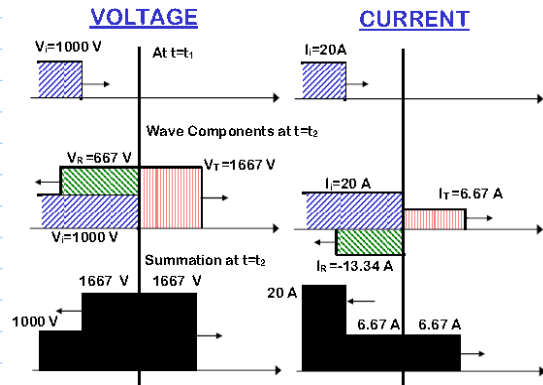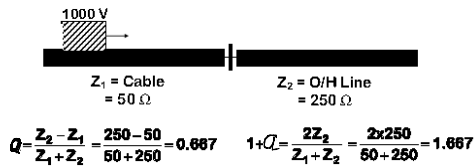

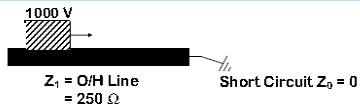
* Termination into a short circuit ($Z_0=0$)



$a = -1$ $1+a=0$

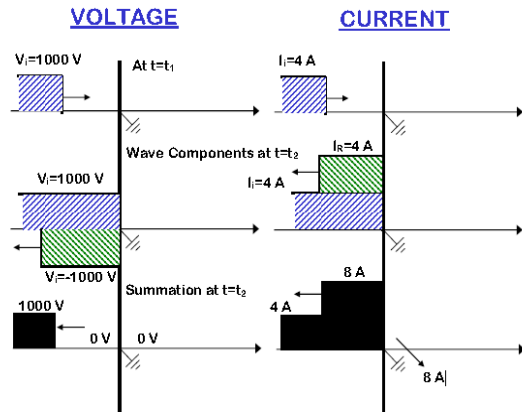

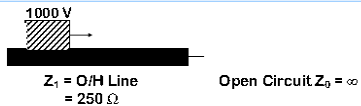* Termination into open circuit ($Z_0=\infty$)



$a = 1$ $b = 2$

