
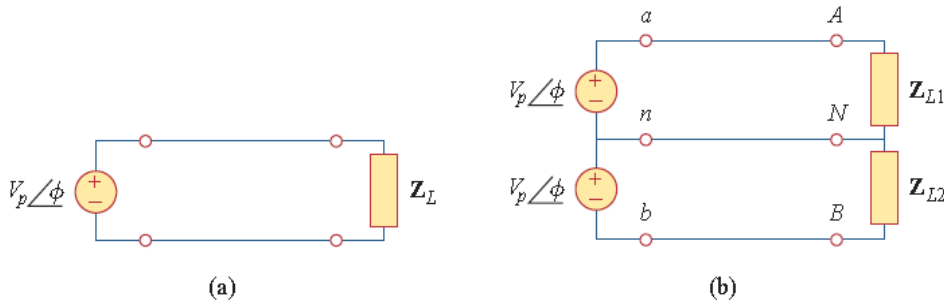


# Ch. 12 3 $\phi$ Circuits


## 12.1 Introduction:

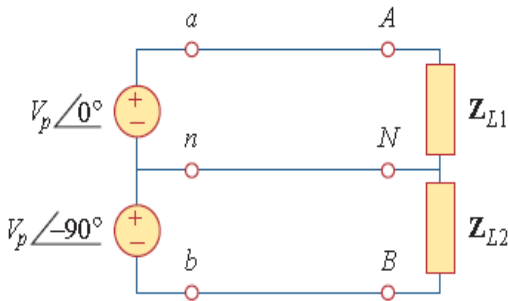

**Figure 12.1**  
Single-phase systems: (a) two-wire type, (b) three-wire type.



**Figure 12.2**  
Two-phase three-wire system.

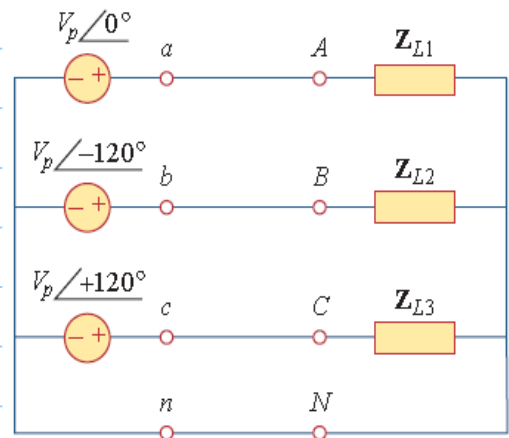


**Figure 12.3**  
Three-phase four-wire system.

\* polyphase Circuits or systems in which the ac sources operate at the same frequency but different phases

- Why 3 $\phi$ :
- ① Can take 1 $\phi$ , 2 $\phi$ , or multiples of 3 $\phi$
  - ② Instantaneous power is constant (no pulsating)
  - ③ Less wire required  $\rightarrow$  economical.

## 12.2) Balanced Three-phase Voltages:


What is 3 $\phi$ :

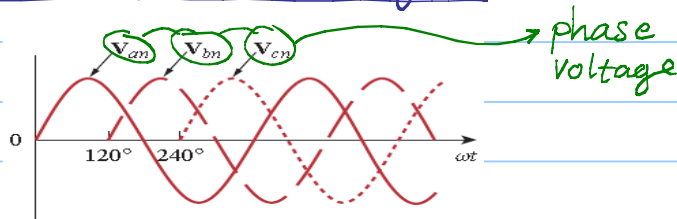

**Figure 12.5**  
The generated voltages are 120 $^\circ$  apart from each other.
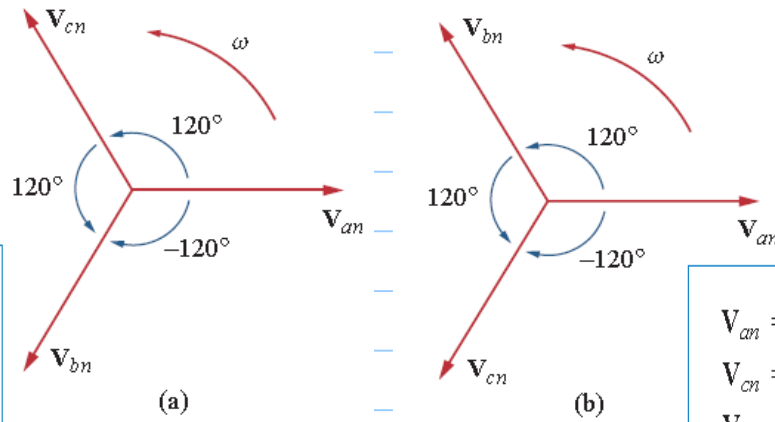
# \* 3Ø Sources:

**Balanced phase voltages** are equal in magnitude and are out of phase with each other by 120°.




$$\begin{aligned}
 V_{an} &= V_p \angle 0^\circ \\
 V_{bn} &= V_p \angle -120^\circ \\
 V_{cn} &= V_p \angle -240^\circ = V_p \angle +120^\circ
 \end{aligned}$$

$$\begin{aligned}
 V_{an} &= V_p \angle 0^\circ \\
 V_{cn} &= V_p \angle -120^\circ \\
 V_{bn} &= V_p \angle -240^\circ = V_p \angle +120^\circ
 \end{aligned}$$

**Figure 12.7**  
Phase sequences: (a) *abc* or positive sequence, (b) *acb* or negative sequence.

## Balanced 3Ø :


$$\left. \begin{aligned}
 V_{an} + V_{bn} + V_{cn} &= 0 \\
 |V_{an}| &= |V_{bn}| = |V_{cn}|
 \end{aligned} \right\} \text{because the angles are } 120^\circ \text{ - out of phase}$$

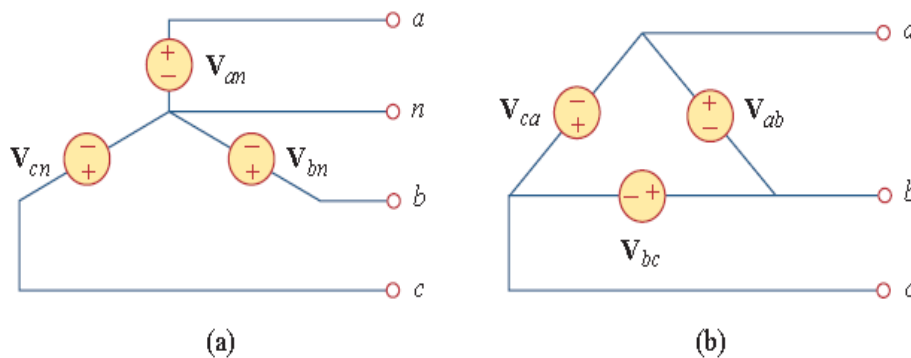

**Figure 12.6**  
Three-phase voltage sources: (a) Y-connected source, (b) Δ-connected source.

## 3 $\phi$ Loads:

A **balanced load** is one in which the phase impedances are equal in magnitude and in phase.

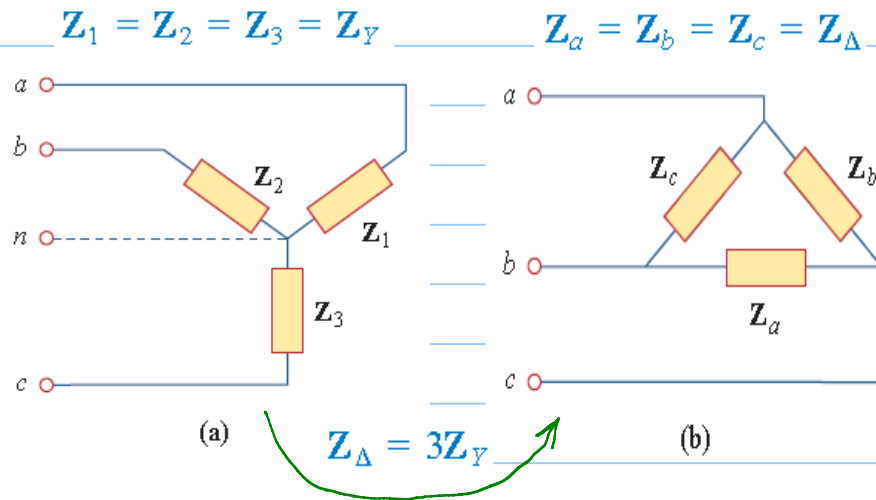

**Figure 12.8**

Two possible three-phase load configurations: (a) a Y-connected load, (b) a  $\Delta$ -connected load.

### Example 12.1

Determine the phase sequence of the set of voltages

$$v_{an} = 200 \cos(\omega t + 10^\circ)$$

$$v_{bn} = 200 \cos(\omega t - 230^\circ), \quad v_{cn} = 200 \cos(\omega t - 110^\circ)$$

#### Solution:

The voltages can be expressed in phasor form as

$$V_{an} = 200 \angle 10^\circ \text{ V}, \quad V_{bn} = 200 \angle -230^\circ \text{ V}, \quad V_{cn} = 200 \angle -110^\circ \text{ V}$$


We notice that  $V_{an}$  leads  $V_{cn}$  by  $120^\circ$  and  $V_{cn}$  in turn leads  $V_{bn}$  by  $120^\circ$ . Hence, we have an  $acb$  sequence.

### \* Four Source - Load Configurations:

- Y-Y connection (i.e., Y-connected source with a Y-connected load).
- Y- $\Delta$  connection.
- $\Delta$ - $\Delta$  connection.
- $\Delta$ -Y connection.


## 12.3 Balanced Wye-Wye Connection:

A **balanced Y-Y system** is a three-phase system with a balanced Y-connected source and a balanced Y-connected load.

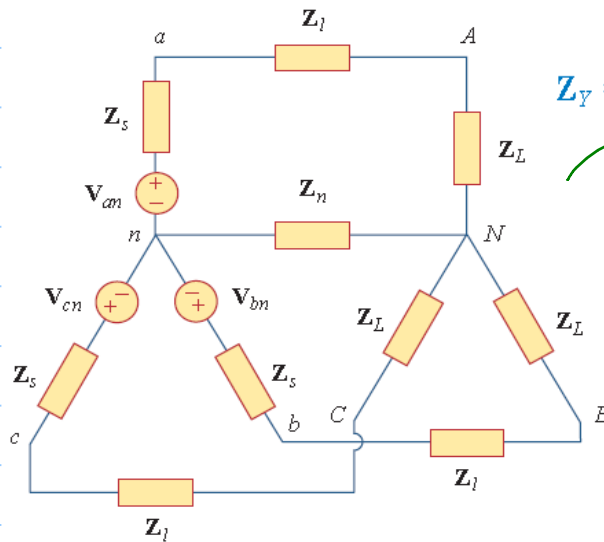

**Figure 12.9**  
A balanced Y-Y system, showing the source, line, and load impedances.

$$Z_Y = Z_s + Z_\ell + Z_L$$

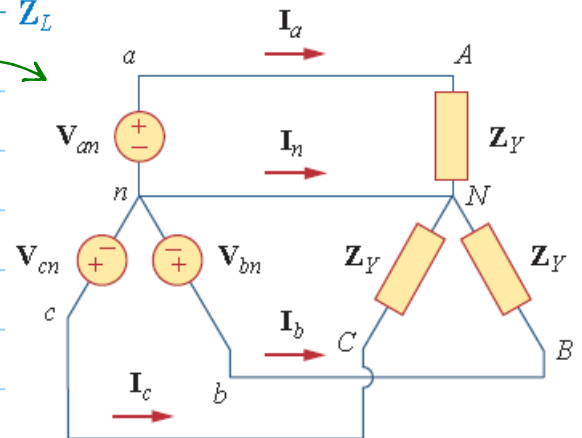

**Figure 12.10**  
Balanced Y-Y connection.

### \* Y-Y Voltages:

#### \* Phase Voltages:

$$* V_{an} = V_p / 0^\circ$$

$$* V_{bn} = V_p / -120^\circ$$

$$* V_{cn} = V_p / +120^\circ$$

#### (L-L) \* Line-Line Voltages: (or line voltages)


$$* V_{ab} = V_{an} + V_{nb} = V_{an} - V_{bn} = V_p / 0^\circ - V_p / -120^\circ$$

$$= V_p \left( 1 + \frac{1}{2} + j \frac{\sqrt{3}}{2} \right) = \sqrt{3} V_p / 30^\circ$$


$$* V_{bc} = V_{bn} - V_{cn} = \sqrt{3} V_p / -90^\circ$$

$$* V_{ca} = V_{cn} - V_{an} = \sqrt{3} V_p / -210^\circ$$

$$V_L = \sqrt{3} V_p$$

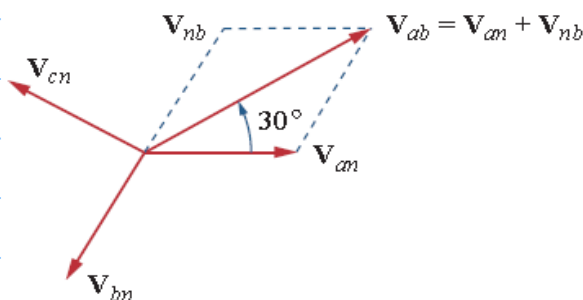

(a)

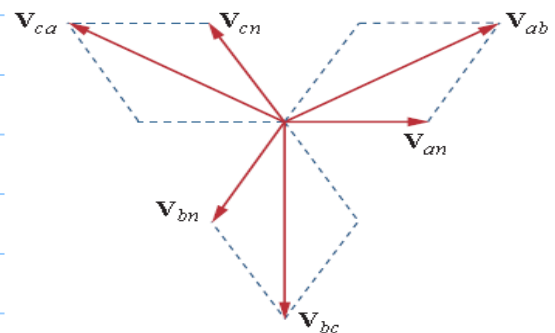

(b)

**Figure 12.11**

Phasor diagrams illustrating the relationship between line voltages and phase voltages.

## \* Y-Y Currents:

$$I_a = \frac{V_{an}}{Z_Y}, \quad I_b = \frac{V_{bn}}{Z_Y} = \frac{V_{an}/-120^\circ}{Z_Y} = I_a/-120^\circ, \quad I_c = \frac{V_{cn}}{Z_Y} = \frac{V_{an}/-240^\circ}{Z_Y} = I_a/-240^\circ$$


$$I_a + I_b + I_c = 0$$

$$I_n = -(I_a + I_b + I_c) = 0$$

$$V_{nN} = Z_n I_n = 0$$

## \* Alternative way to solve Y-Y systems: (single-phase)

$$I_a = \frac{V_{an}}{Z_Y}$$

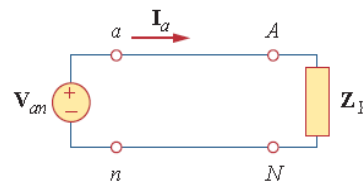


**Figure 12.12**

A single-phase equivalent circuit.

Calculate the line currents in the three-wire Y-Y system of Fig. 12.13.

### Example 12.2

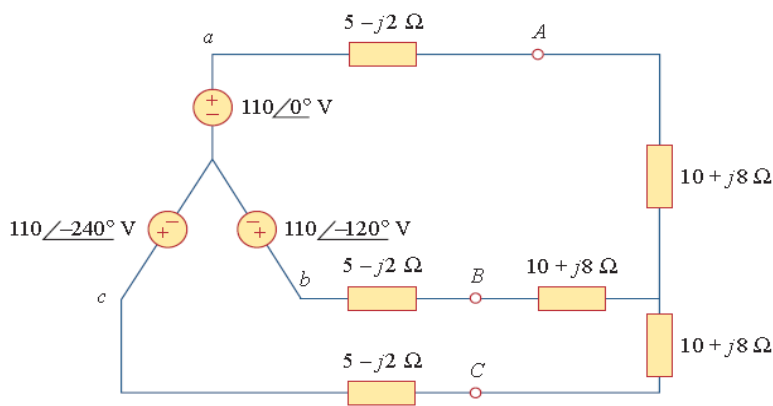

**Figure 12.13**

Three-wire Y-Y system; for Example 12.2.

#### Solution:

The three-phase circuit in Fig. 12.13 is balanced; we may replace it with its single-phase equivalent circuit such as in Fig. 12.12. We obtain  $I_a$  from the single-phase analysis as

$$I_a = \frac{V_{an}}{Z_Y}$$

where  $Z_Y = (5 - j2) + (10 + j8) = 15 + j6 = 16.155/21.8^\circ$ . Hence,

$$I_a = \frac{110/0^\circ}{16.155/21.8^\circ} = 6.81/-21.8^\circ \text{ A}$$

Since the source voltages in Fig. 12.13 are in positive sequence, the line currents are also in positive sequence:

$$I_b = I_a/-120^\circ = 6.81/-141.8^\circ \text{ A}$$

$$I_c = I_a/-240^\circ = 6.81/-261.8^\circ \text{ A} = 6.81/98.2^\circ \text{ A}$$

## 12.4 Balanced Wye-Delta Connection:

A **balanced Y-Δ system** consists of a balanced Y-connected source feeding a balanced Δ-connected load.


$$V_{an} = V_p / 0^\circ$$

$$V_{bn} = V_p / -120^\circ, \quad V_{cn} = V_p / +120^\circ$$

$$V_{ab} = \sqrt{3}V_p / 30^\circ = V_{AB}, \quad V_{bc} = \sqrt{3}V_p / -90^\circ = V_{BC}$$

$$V_{ca} = \sqrt{3}V_p / -150^\circ = V_{CA}$$

$$I_{AB} = \frac{V_{AB}}{Z_\Delta}, \quad I_{BC} = \frac{V_{BC}}{Z_\Delta}, \quad I_{CA} = \frac{V_{CA}}{Z_\Delta}$$

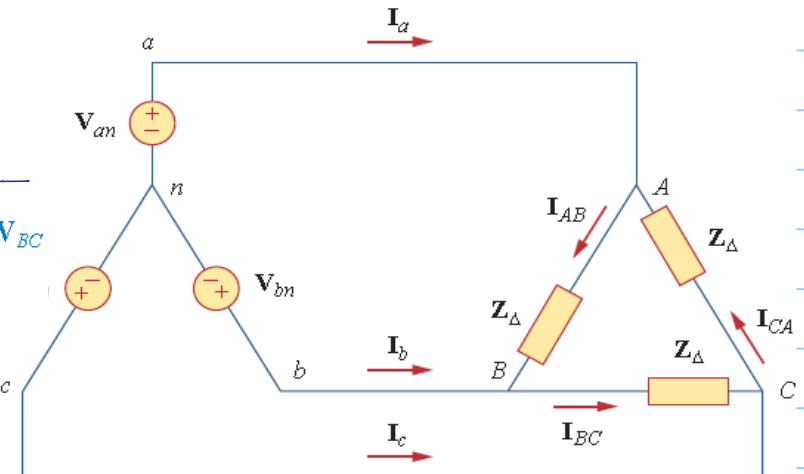


**Figure 12.14**  
Balanced Y-Δ connection.

$$I_a = I_{AB} - I_{CA}, \quad I_b = I_{BC} - I_{AB}, \quad I_c = I_{CA} - I_{BC}$$

$$I_a = I_{AB} - I_{CA} = I_{AB}(1 - 1 / -240^\circ)$$

$$= I_{AB}(1 + 0.5 - j0.866) = I_{AB} \sqrt{3} / -30^\circ$$

$$I_L = \sqrt{3}I_p$$

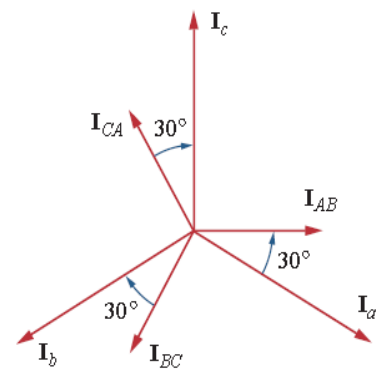


**Figure 12.15**  
Phasor diagram illustrating the relationship between phase and line currents.

\* Alternative way to solve Y-Δ system:

1) transform Δ load to Y load.

$$Z_Y = \frac{Z_\Delta}{3}$$

2) Solve the single-phase system.

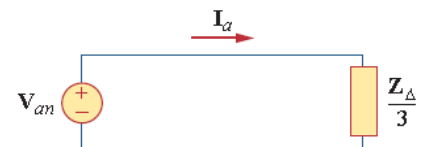

**Figure 12.16**  
A single-phase equivalent circuit of a balanced Y-Δ circuit.

A balanced *abc*-sequence Y-connected source with  $V_{an} = 100/\underline{10^\circ}$  V is connected to a  $\Delta$ -connected balanced load  $(8 + j4) \Omega$  per phase. Calculate the phase and line currents.

**Solution:**

This can be solved in two ways.

■ **METHOD 1** The load impedance is

$$Z_{\Delta} = 8 + j4 = 8.944/\underline{26.57^\circ} \Omega$$

If the phase voltage  $V_{an} = 100/\underline{10^\circ}$ , then the line voltage is

$$V_{ab} = V_{an}\sqrt{3}/\underline{30^\circ} = 100\sqrt{3}/\underline{10^\circ + 30^\circ} = V_{AB}$$

or

$$V_{AB} = 173.2/\underline{40^\circ} \text{ V}$$

The phase currents are

$$I_{AB} = \frac{V_{AB}}{Z_{\Delta}} = \frac{173.2/\underline{40^\circ}}{8.944/\underline{26.57^\circ}} = 19.36/\underline{13.43^\circ} \text{ A}$$

$$I_{BC} = I_{AB}/\underline{-120^\circ} = 19.36/\underline{-106.57^\circ} \text{ A}$$

$$I_{CA} = I_{AB}/\underline{+120^\circ} = 19.36/\underline{133.43^\circ} \text{ A}$$

The line currents are

$$I_{\alpha} = I_{AB}\sqrt{3}/\underline{-30^\circ} = \sqrt{3}(19.36)/\underline{13.43^\circ - 30^\circ} \\ = 33.53/\underline{-16.57^\circ} \text{ A}$$

$$I_{CA} = I_{AB}/\underline{+120^\circ} = 19.36/\underline{133.43^\circ} \text{ A}$$

The line currents are

$$I_{\alpha} = I_{AB}\sqrt{3}/\underline{-30^\circ} = \sqrt{3}(19.36)/\underline{13.43^\circ - 30^\circ} \\ = 33.53/\underline{-16.57^\circ} \text{ A}$$

$$I_b = I_{\alpha}/\underline{-120^\circ} = 33.53/\underline{-136.57^\circ} \text{ A}$$

$$I_c = I_{\alpha}/\underline{+120^\circ} = 33.53/\underline{103.43^\circ} \text{ A}$$

■ **METHOD 2** Alternatively, using single-phase analysis,

$$I_{\alpha} = \frac{V_{an}}{Z_{\Delta}/3} = \frac{100/\underline{10^\circ}}{2.981/\underline{26.57^\circ}} = 33.54/\underline{-16.57^\circ} \text{ A}$$

as above. Other line currents are obtained using the *abc* phase sequence.

## 12.5 Balanced Delta-Delta Connection :

A **balanced  $\Delta$ - $\Delta$  system** is one in which both the balanced source and balanced load are  $\Delta$ -connected.

$$V_{ab} = V_p / 0^\circ$$

$$V_{bc} = V_p / -120^\circ, \quad V_{ca} = V_p / +120^\circ$$



---


$$V_{ab} = V_{AB}, \quad V_{bc} = V_{BC}, \quad V_{ca} = V_{CA}$$


---


$$I_{AB} = \frac{V_{AB}}{Z_\Delta} = \frac{V_{ab}}{Z_\Delta}, \quad I_{BC} = \frac{V_{BC}}{Z_\Delta} = \frac{V_{bc}}{Z_\Delta}$$

$$I_{CA} = \frac{V_{CA}}{Z_\Delta} = \frac{V_{ca}}{Z_\Delta}$$

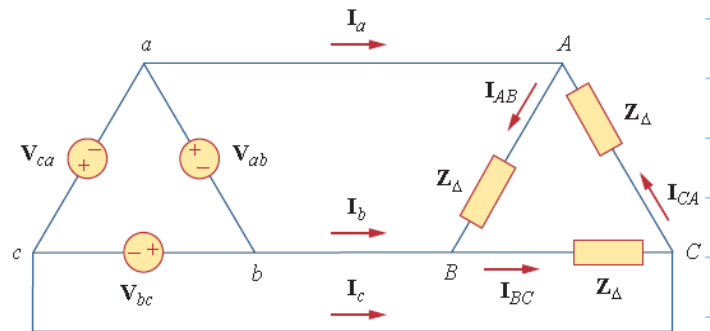

**Figure 12.17**  
A balanced  $\Delta$ - $\Delta$  connection.

$$I_a = I_{AB} - I_{CA}, \quad I_b = I_{BC} - I_{AB}, \quad I_c = I_{CA} - I_{BC} \Rightarrow I_L = \sqrt{3}I_p$$

A balanced  $\Delta$ -connected load having an impedance  $20 - j15 \Omega$  is connected to a  $\Delta$ -connected, positive-sequence generator having  $V_{ab} = 330 \angle 0^\circ$  V. Calculate the phase currents of the load and the line currents.

### Example 12.4

#### Solution:

The load impedance per phase is

$$Z_\Delta = 20 - j15 = 25 \angle -36.87^\circ \Omega$$

Since  $V_{AB} = V_{ab}$ , the phase currents are

$$I_{AB} = \frac{V_{AB}}{Z_\Delta} = \frac{330 \angle 0^\circ}{25 \angle -36.87^\circ} = 13.2 \angle 36.87^\circ \text{ A}$$

$$I_{BC} = I_{AB} \angle -120^\circ = 13.2 \angle -83.13^\circ \text{ A}$$

$$I_{CA} = I_{AB} \angle +120^\circ = 13.2 \angle 156.87^\circ \text{ A}$$

For a delta load, the line current always lags the corresponding phase current by  $30^\circ$  and has a magnitude  $\sqrt{3}$  times that of the phase current. Hence, the line currents are

$$I_a = I_{AB} \sqrt{3} \angle -30^\circ = (13.2 \angle 36.87^\circ)(\sqrt{3} \angle -30^\circ)$$

$$= 22.86 \angle 6.87^\circ \text{ A}$$

$$I_b = I_a \angle -120^\circ = 22.86 \angle -113.13^\circ \text{ A}$$

$$I_c = I_a \angle +120^\circ = 22.86 \angle 126.87^\circ \text{ A}$$




## 12.6 Balanced Delta-Wye Connection:

A **balanced  $\Delta$ -Y system** consists of a balanced  $\Delta$ -connected source feeding a balanced Y-connected load.

$$V_{ab} = V_p / 0^\circ, \quad V_{bc} = V_p / -120^\circ$$

$$V_{ca} = V_p / +120^\circ$$

$$I_a = \frac{V_p / \sqrt{3} / -30^\circ}{Z_Y}$$

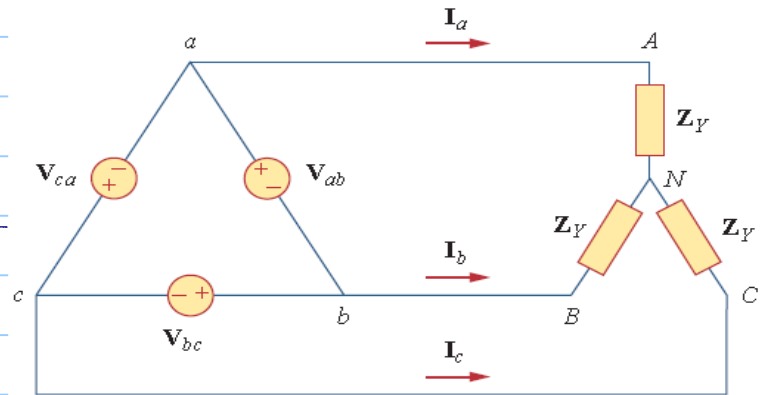


**Figure 12.18**  
A balanced  $\Delta$ -Y connection.

\* Alternative way to solve  $\Delta$ -Y system:

1) Transform the  $\Delta$  source to Y source:

$$V_{an} = \frac{V_p}{\sqrt{3}} / -30^\circ$$


$$V_{bn} = \frac{V_p}{\sqrt{3}} / -150^\circ, \quad V_{cn} = \frac{V_p}{\sqrt{3}} / +90^\circ$$

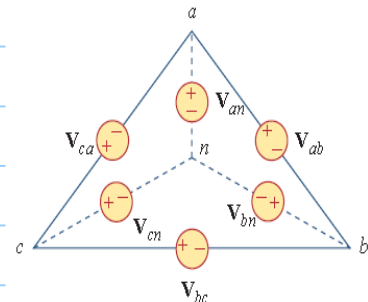

**Figure 12.19**  
Transforming a  $\Delta$ -connected source to an equivalent Y-connected source.

2) Solve the single-phase system.

$$I_a = \frac{V_p / \sqrt{3} / -30^\circ}{Z_Y}$$

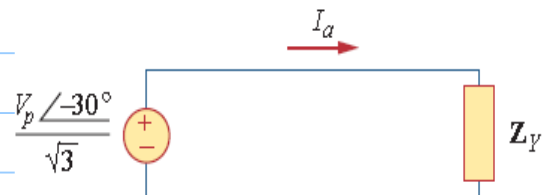

**Figure 12.20**  
The single-phase equivalent circuit.

A balanced Y-connected load with a phase impedance of  $40 + j25 \Omega$  is supplied by a balanced, positive sequence  $\Delta$ -connected source with a line voltage of 210 V. Calculate the phase currents. Use  $V_{ab}$  as reference.

**Solution:**

The load impedance is

$$Z_Y = 40 + j25 = 47.17/32^\circ \Omega$$

and the source voltage is

$$V_{ab} = 210/0^\circ \text{ V}$$

When the  $\Delta$ -connected source is transformed to a Y-connected source,

$$V_{an} = \frac{V_{ab}}{\sqrt{3}}/-30^\circ = 121.2/-30^\circ \text{ V}$$

The line currents are

$$I_a = \frac{V_{an}}{Z_Y} = \frac{121.2/-30^\circ}{47.12/32^\circ} = 2.57/-62^\circ \text{ A}$$

$$I_b = I_a/-120^\circ = 2.57/-178^\circ \text{ A}$$

$$I_c = I_a/120^\circ = 2.57/58^\circ \text{ A}$$

which are the same as the phase currents.

TABLE 12.1

Summary of phase and line voltages/currents for balanced three-phase systems.<sup>1</sup>

Connection	Phase voltages/currents	Line voltages/currents
Y-Y	$V_{an} = V_p/0^\circ$ $V_{bn} = V_p/-120^\circ$ $V_{cn} = V_p/+120^\circ$ Same as line currents	$V_{ab} = \sqrt{3}V_p/30^\circ$ $V_{bc} = V_{ab}/-120^\circ$ $V_{ca} = V_{ab}/+120^\circ$ $I_a = V_{an}/Z_Y$ $I_b = I_a/-120^\circ$ $I_c = I_a/+120^\circ$
Y- $\Delta$	$V_{an} = V_p/0^\circ$ $V_{bn} = V_p/-120^\circ$ $V_{cn} = V_p/+120^\circ$ $I_{AB} = V_{AB}/Z_\Delta$ $I_{BC} = V_{BC}/Z_\Delta$ $I_{CA} = V_{CA}/Z_\Delta$	$V_{ab} = V_{AB} = \sqrt{3}V_p/30^\circ$ $V_{bc} = V_{BC} = V_{ab}/-120^\circ$ $V_{ca} = V_{CA} = V_{ab}/+120^\circ$ $I_a = I_{AB}\sqrt{3}/-30^\circ$ $I_b = I_a/-120^\circ$ $I_c = I_a/+120^\circ$
$\Delta$ - $\Delta$	$V_{ab} = V_p/0^\circ$ $V_{bc} = V_p/-120^\circ$ $V_{ca} = V_p/+120^\circ$ $I_{AB} = V_{ab}/Z_\Delta$ $I_{BC} = V_{bc}/Z_\Delta$ $I_{CA} = V_{ca}/Z_\Delta$	Same as phase voltages  $I_a = I_{AB}\sqrt{3}/-30^\circ$ $I_b = I_a/-120^\circ$ $I_c = I_a/+120^\circ$
$\Delta$ -Y	$V_{ab} = V_p/0^\circ$ $V_{bc} = V_p/-120^\circ$ $V_{ca} = V_p/+120^\circ$  Same as line currents	Same as phase voltages  $I_a = \frac{V_p/-30^\circ}{\sqrt{3}Z_Y}$ $I_b = I_a/-120^\circ$ $I_c = I_a/+120^\circ$

<sup>1</sup> Positive or abc sequence is assumed.

## 12.7 Power in a Balanced System:

\* The **average** power per phase

$$P_p = V_p I_p \underbrace{\cos\theta}_{\text{pf}}$$

\* The **reactive** power per phase

$$Q_p = V_p I_p \sin\theta$$

\* The **complex** power per phase

$$S_p = V_p I_p$$

\* The **complex** power per phase

$$S_p = P_p + jQ_p = V_p I_p^*$$

\* The total **average** power per phase

$$P = P_a + P_b + P_c = 3P_p = 3V_p I_p \cos\theta = \sqrt{3}V_L I_L \underbrace{\cos\theta}_{\text{pf}}$$

\* The total **reactive** power per phase

$$Q = 3V_p I_p \sin\theta = 3Q_p = \sqrt{3}V_L I_L \sin\theta$$

\* The total **complex** power per phase

$$S = 3S_p = 3V_p I_p^* = 3I_p^2 Z_p = \frac{3V_p^2}{Z_p^*}$$

$$S = P + jQ = \sqrt{3}V_L I_L / \theta$$

A three-phase motor can be regarded as a balanced Y-load. A three-phase motor draws 5.6 kW when the line voltage is 220 V and the line current is 18.2 A. Determine the power factor of the motor.

### Example 12.7

#### Solution:

The apparent power is

$$S = \sqrt{3}V_L I_L = \sqrt{3}(220)(18.2) = 6935.13 \text{ VA}$$

Since the real power is

$$P = S \cos\theta = 5600 \text{ W}$$

the power factor is

$$\text{pf} = \cos\theta = \frac{P}{S} = \frac{5600}{6935.13} = 0.8075$$

## Example 12.8

Two balanced loads are connected to a 240-kV rms 60-Hz line, as shown in Fig. 12.22(a). Load 1 draws 30 kW at a power factor of 0.6 lagging, while load 2 draws 45 kVAR at a power factor of 0.8 lagging. Assuming the  $abc$  sequence, determine: (a) the complex, real, and reactive powers absorbed by the combined load, (b) the line currents, and (c) the kVAR rating of the three capacitors  $\Delta$ -connected in parallel with the load that will raise the power factor to 0.9 lagging and the capacitance of each capacitor.


### Solution:

(a) For load 1, given that  $P_1 = 30$  kW and  $\cos\theta_1 = 0.6$ , then  $\sin\theta_1 = 0.8$ . Hence,


$$S_1 = \frac{P_1}{\cos\theta_1} = \frac{30 \text{ kW}}{0.6} = 50 \text{ kVA}$$

and  $Q_1 = S_1 \sin\theta_1 = 50(0.8) = 40$  kVAR. Thus, the complex power due to load 1 is
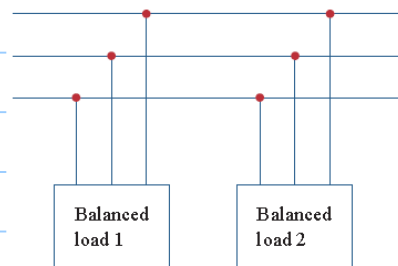
$$\mathbf{S}_1 = P_1 + jQ_1 = 30 + j40 \text{ kVA} \quad (12.8.1)$$



(a)

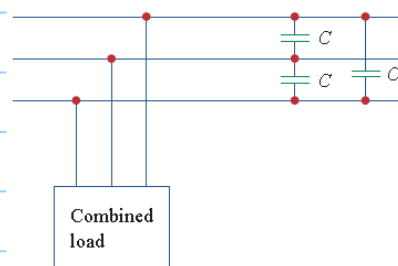

For load 2, if  $Q_2 = 45$  kVAR and  $\cos\theta_2 = 0.8$ , then  $\sin\theta_2 = 0.6$ . We find

$$S_2 = \frac{Q_2}{\sin\theta_2} = \frac{45 \text{ kVA}}{0.6} = 75 \text{ kVA}$$

and  $P_2 = S_2 \cos\theta_2 = 75(0.8) = 60$  kW. Therefore the complex power due to load 2 is

$$\mathbf{S}_2 = P_2 + jQ_2 = 60 + j45 \text{ kVA} \quad (12.8.2)$$

From Eqs. (12.8.1) and (12.8.2), the total complex power absorbed by the load is

$$\mathbf{S} = \mathbf{S}_1 + \mathbf{S}_2 = 90 + j85 \text{ kVA} = 123.8/43.36^\circ \text{ kVA} \quad (12.8.3)$$

which has a power factor of  $\cos 43.36^\circ = 0.727$  lagging. The real power is then 90 kW, while the reactive power is 85 kVAR.

(b) Since  $S = \sqrt{3}V_L I_L$ , the line current is

$$I_L = \frac{S}{\sqrt{3}V_L} \quad (12.8.4)$$

We apply this to each load, keeping in mind that for both loads,  $V_L = 240$  kV. For load 1,

$$I_{L1} = \frac{50,000}{\sqrt{3} 240,000} = 120.28 \text{ mA}$$

Since the power factor is lagging, the line current lags the line voltage by  $\theta_1 = \cos^{-1} 0.6 = 53.13^\circ$ . Thus,

$$\mathbf{I}_{\alpha 1} = 120.28 / -53.13^\circ$$

For load 2,

$$I_{L2} = \frac{75,000}{\sqrt{3} 240,000} = 180.42 \text{ mA}$$

and the line current lags the line voltage by  $\theta_2 = \cos^{-1} 0.8 = 36.87^\circ$ . Hence,

$$\mathbf{I}_{\alpha 2} = 180.42 / -36.87^\circ$$

The total line current is

$$\begin{aligned} \mathbf{I}_\alpha &= \mathbf{I}_{\alpha 1} + \mathbf{I}_{\alpha 2} = 120.28 / -53.13^\circ + 180.42 / -36.87^\circ \\ &= (72.168 - j96.224) + (144.336 - j108.252) \\ &= 216.5 - j204.472 = 297.8 / -43.36^\circ \text{ mA} \end{aligned}$$

Alternatively, we could obtain the current from the total complex power using Eq. (12.8.4) as

$$I_L = \frac{123,800}{\sqrt{3} 240,000} = 297.82 \text{ mA}$$

and

$$I_a = 297.82 \angle -43.36^\circ \text{ mA}$$

which is the same as before. The other line currents,  $I_{b2}$  and  $I_{ca}$ , can be obtained according to the *abc* sequence (i.e.,  $I_b = 297.82 \angle -163.36^\circ \text{ mA}$  and  $I_c = 297.82 \angle 76.64^\circ \text{ mA}$ ).

(c) We can find the reactive power needed to bring the power factor to 0.9 lagging using Eq. (11.59),

$$Q_C = P(\tan\theta_{\text{old}} - \tan\theta_{\text{new}})$$

where  $P = 90 \text{ kW}$ ,  $\theta_{\text{old}} = 43.36^\circ$ , and  $\theta_{\text{new}} = \cos^{-1} 0.9 = 25.84^\circ$ . Hence,

$$Q_C = 90,000(\tan 43.36^\circ - \tan 25.84^\circ) = 41.4 \text{ kVAR}$$

This reactive power is for the three capacitors. For each capacitor, the rating  $Q'_C = 13.8 \text{ kVAR}$ . From Eq. (11.60), the required capacitance is

$$C = \frac{Q'_C}{\omega V_{\text{rms}}^2}$$

Since the capacitors are  $\Delta$ -connected as shown in Fig. 12.22(b),  $V_{\text{rms}}$  in the above formula is the line-to-line or line voltage, which is 240 kV. Thus,

$$C = \frac{13,800}{(2\pi 60)(240,000)^2} = 635.5 \text{ pF}$$