

Ch 13. Magnetically Coupled Circuits

13.2 Mutual Inductance:

* Single Inductor case:

Faraday's Law:

* of turns $\leftarrow v = N \frac{d\phi}{dt}$ \rightarrow self-inductance (L)

$$v = N \frac{d\phi}{dt} \frac{di}{dt}$$

$$v = L \frac{di}{dt}$$

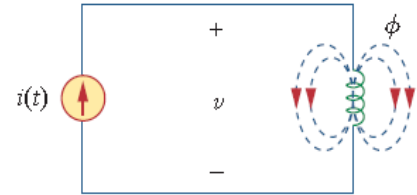


Figure 13.1

Magnetic flux produced by a single coil with N turns.

* Two Inductors case:

L_1 & L_2 are magnetically coupled

a) $i_2 = 0$:

$$\phi_1 = \phi_{11} + \phi_{12}$$

$$v_1 = N_1 \frac{d\phi_1}{di_1} \frac{di_1}{dt} = L_1 \frac{di_1}{dt}$$

$$v_2 = N_2 \frac{d\phi_{12}}{di_1} \frac{di_1}{dt} = M_{21} \frac{di_1}{dt}$$

mutual inductance

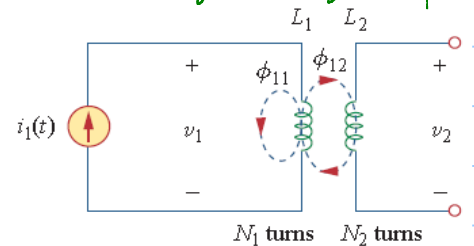


Figure 13.2

Mutual inductance M_{21} of coil 2 with respect to coil 1.

b) $i_1 = 0$:

$$\phi_2 = \phi_{21} + \phi_{22}$$

$$v_2 = N_2 \frac{d\phi_2}{di_2} \frac{di_2}{dt} = L_2 \frac{di_2}{dt}$$

$$v_1 = N_1 \frac{d\phi_{21}}{di_2} \frac{di_2}{dt} = M_{12} \frac{di_2}{dt}$$

mutual inductance

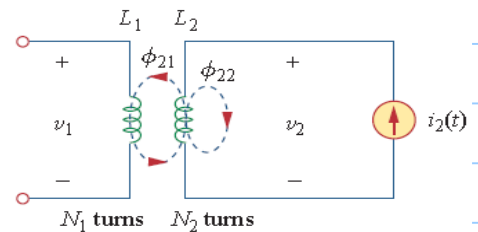


Figure 13.3

Mutual inductance M_{12} of coil 1 with respect to coil 2.

$$M_{12} = M_{21} = M \rightarrow \text{measures in Henrys (H)}$$

Mutual inductance is the ability of one inductor to induce a voltage across a neighboring inductor, measured in henrys (H).

* Dot Convention:

If a current **enters** the dotted terminal of one coil, the reference polarity of the mutual voltage in the second coil is **positive** at the dotted terminal of the second coil.

If a current **leaves** the dotted terminal of one coil, the reference polarity of the mutual voltage in the second coil is **negative** at the dotted terminal of the second coil.

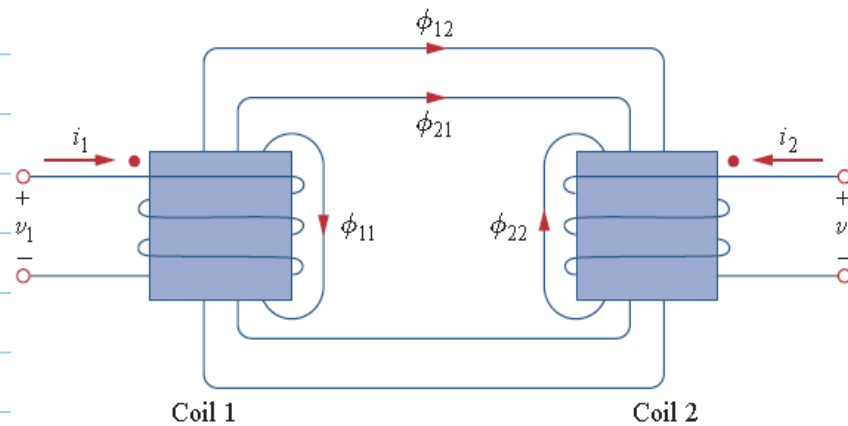


Figure 13.4
Illustration of the dot convention.

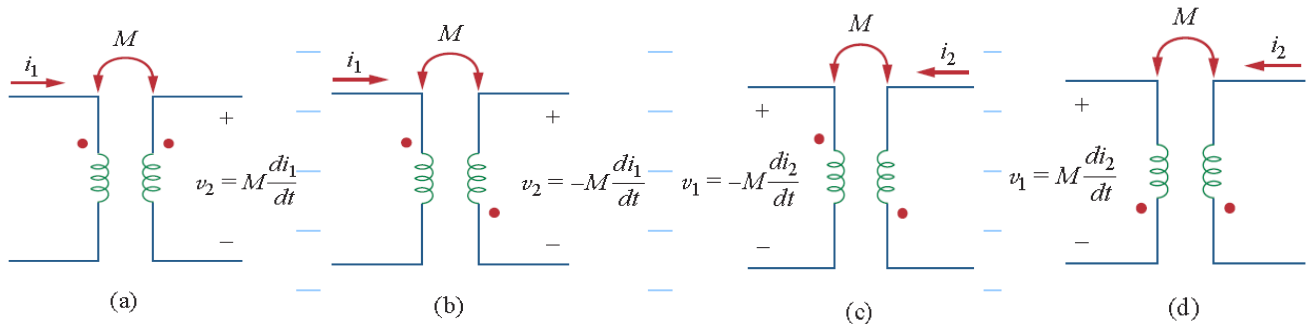


Figure 13.5
Examples illustrating how to apply the dot convention.

$$L = L_1 + L_2 + 2M \quad (\text{Series-aiding connection})$$

$$L = L_1 + L_2 - 2M \quad (\text{Series-opposing connection})$$

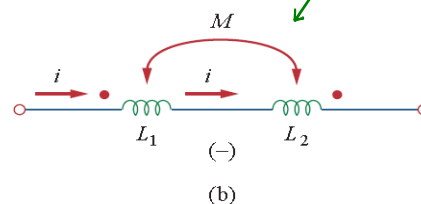
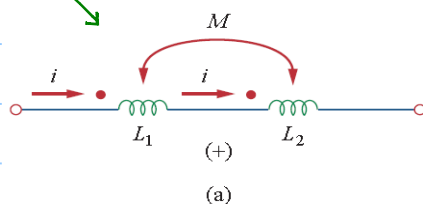


Figure 13.6
Dot convention for coils in series; the sign indicates the polarity of the mutual voltage:
(a) series-aiding connection, (b) series-opposing connection.

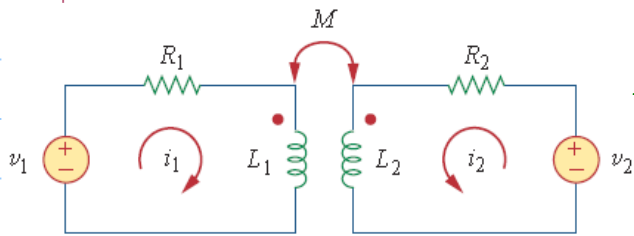


Figure 13.7
Time-domain analysis of a circuit containing coupled coils.

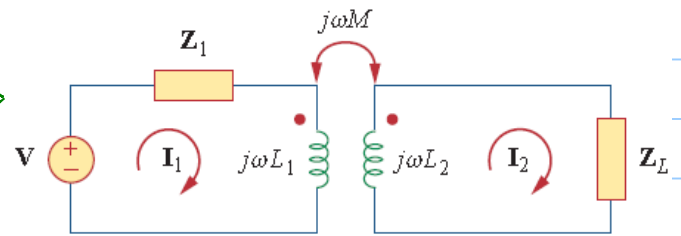


Figure 13.8
Frequency-domain analysis of a circuit containing coupled coils.

Calculate the phasor currents I_1 and I_2 in the circuit of Fig. 13.9.

Example 13.1

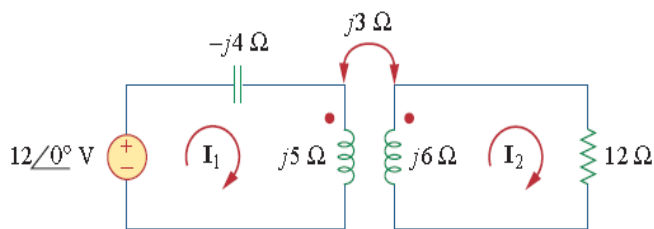


Figure 13.9
For Example 13.1.

Solution:

For coil 1, KVL gives

$$-12 + (-j4 + j5)I_1 - j3I_2 = 0$$

or

$$jI_1 - j3I_2 = 12 \quad (13.1.1)$$

For coil 2, KVL gives.

$$-j3I_1 + (12 + j6)I_2 = 0$$

or

$$I_1 = \frac{(12 + j6)I_2}{j3} = (2 - j4)I_2 \quad (13.1.2)$$

Substituting this in Eq. (13.1.1), we get

$$(j2 + 4 - j3)I_2 = (4 - j)I_2 = 12$$

or

$$I_2 = \frac{12}{4 - j} = 2.91 \angle 14.04^\circ \text{ A}$$

From Eqs. (13.1.2) and (13.1.3),

$$\begin{aligned} I_1 &= (2 - j4)I_2 = (4.472 \angle -63.43^\circ)(2.91 \angle 14.04^\circ) \\ &= 13.01 \angle -49.39^\circ \text{ A} \end{aligned}$$

Example 13.2

Calculate the mesh currents in the circuit of Fig. 13.11.

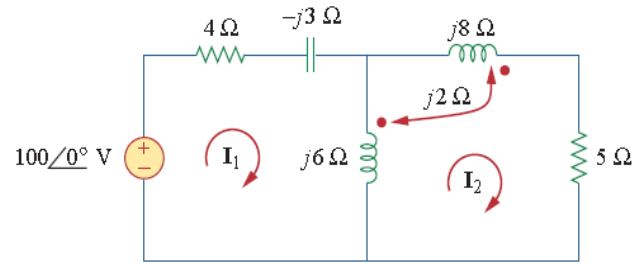


Figure 13.11
For Example 13.2.

Solution:

Thus, for mesh 1 in Fig. 13.11, KVL gives

$$-100 + I_1(4 - j3 + j6) - j6I_2 - j2I_2 = 0$$

or

$$100 = (4 + j3)I_1 - j8I_2 \quad (13.2.1)$$

Therefore, for mesh 2 in Fig. 13.11, KVL gives

$$0 = -2jI_1 - j6I_1 + (j6 + j8 + j2 \times 2 + 5)I_2$$

or

$$0 = -j8I_1 + (5 + j18)I_2 \quad (13.2.2)$$

Putting Eqs. (13.2.1) and (13.2.2) in matrix form, we get

$$\begin{bmatrix} 100 \\ 0 \end{bmatrix} = \begin{bmatrix} 4 + j3 & -j8 \\ -j8 & 5 + j18 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

The determinants are

$$\Delta = \begin{vmatrix} 4 + j3 & -j8 \\ -j8 & 5 + j18 \end{vmatrix} = 30 + j87$$

$$\Delta_1 = \begin{vmatrix} 100 & -j8 \\ 0 & 5 + j18 \end{vmatrix} = 100(5 + j18)$$

$$\Delta_2 = \begin{vmatrix} 4 + j3 & 100 \\ -j8 & 0 \end{vmatrix} = j800$$

Thus, we obtain the mesh currents as

$$I_1 = \frac{\Delta_1}{\Delta} = \frac{100(5 + j18)}{30 + j87} = \frac{1,868.2 \angle 74.5^\circ}{92.03 \angle 71^\circ} = 20.3 \angle 3.5^\circ \text{ A}$$

$$I_2 = \frac{\Delta_2}{\Delta} = \frac{j800}{30 + j87} = \frac{800 \angle 90^\circ}{92.03 \angle 71^\circ} = 8.693 \angle 19^\circ \text{ A}$$


13.3 Energy in a Coupled Circuit:

Energy in one coil $\rightarrow w = \frac{1}{2}Li^2$

Total energy:

$$w = \frac{1}{2}L_1i_1^2 + \frac{1}{2}L_2i_2^2 \pm Mi_1i_2$$

If i_1 & i_2 enter or leave the dots

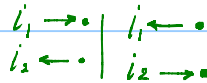

$$M \leq \sqrt{L_1L_2}$$

geometric mean

$$k = \frac{M}{\sqrt{L_1L_2}} = \frac{\phi_{12}}{\phi_1} = \frac{\phi_{12}}{\phi_{11} + \phi_{12}}$$

If the entire flux produced by one coil links another coil, then $k = 1$ and we have 100 percent coupling, or the coils are said to be *perfectly coupled*. For $k < 0.5$, coils are said to be *loosely coupled*; and for $k > 0.5$, they are said to be *tightly coupled*. Thus,

The **coupling coefficient** k is a measure of the magnetic coupling between two coils; $0 \leq k \leq 1$.

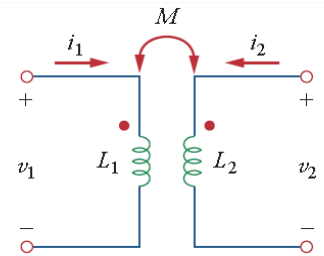


Figure 13.14

The circuit for deriving energy stored in a coupled circuit.

Example 13.3

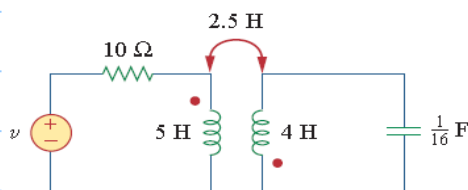


Figure 13.16
For Example 13.3.

Consider the circuit in Fig. 13.16. Determine the coupling coefficient. Calculate the energy stored in the coupled inductors at time $t = 1$ s if $v = 60 \cos(4t + 30^\circ)$ V.

Solution:

The coupling coefficient is

$$k = \frac{M}{\sqrt{L_1L_2}} = \frac{2.5}{\sqrt{20}} = 0.56$$

indicating that the inductors are tightly coupled. To find the energy stored, we need to calculate the current. To find the current, we need to obtain the frequency-domain equivalent of the circuit.

$$60 \cos(4t + 30^\circ) \Rightarrow 60\angle 30^\circ, \quad \omega = 4 \text{ rad/s}$$

$$5 \text{ H} \Rightarrow j\omega L_1 = j20 \Omega$$

$$2.5 \text{ H} \Rightarrow j\omega M = j10 \Omega$$

$$4 \text{ H} \Rightarrow j\omega L_2 = j16 \Omega$$

$$\frac{1}{16} \text{ F} \Rightarrow \frac{1}{j\omega C} = -j4 \Omega$$

The frequency-domain equivalent is shown in Fig. 13.17. We now apply mesh analysis. For mesh 1,

$$(10 + j20)I_1 + j10I_2 = 60\angle 30^\circ \quad (13.3.1)$$

For mesh 2,

$$j10I_1 + (j16 - j4)I_2 = 0$$

or

$$I_1 = -1.2I_2 \quad (13.3.2)$$

Substituting this into Eq. (13.3.1) yields

$$I_2(-12 - j14) = 60\angle 30^\circ \Rightarrow I_2 = 3.254\angle 160.6^\circ \text{ A}$$

and

$$I_1 = -1.2I_2 = 3.905\angle -19.4^\circ \text{ A}$$

In the time-domain,

$$i_1 = 3.905 \cos(4t - 19.4^\circ), \quad i_2 = 3.254 \cos(4t + 160.6^\circ)$$

At time $t = 1$ s, $4t = 4$ rad = 229.2° , and

$$i_1 = 3.905 \cos(229.2^\circ - 19.4^\circ) = -3.389 \text{ A}$$

$$i_2 = 3.254 \cos(229.2^\circ + 160.6^\circ) = 2.824 \text{ A}$$

The total energy stored in the coupled inductors is

$$\begin{aligned} w &= \frac{1}{2}L_1i_1^2 + \frac{1}{2}L_2i_2^2 + Mi_1i_2 \\ &= \frac{1}{2}(5)(-3.389)^2 + \frac{1}{2}(4)(2.824)^2 + 2.5(-3.389)(2.824) = 20.73 \text{ J} \end{aligned}$$

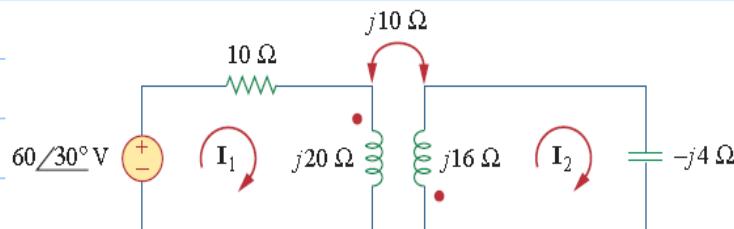


Figure 13.17

Frequency-domain equivalent of the circuit in Fig. 13.16.

13.4 Linear Transformer:

A **transformer** is generally a four-terminal device comprising two (or more) magnetically coupled coils.


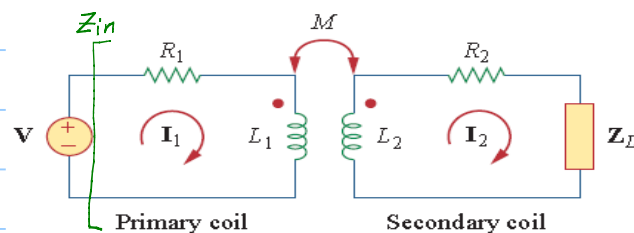


Figure 13.19

A linear transformer.

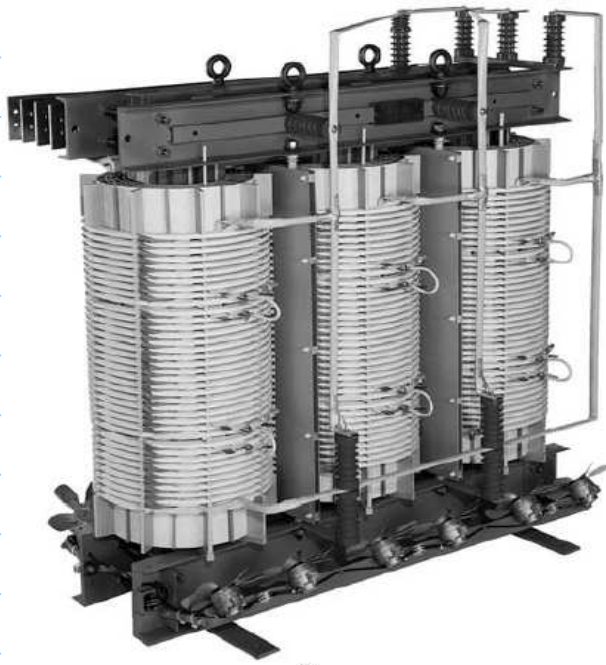

(a)



(b)

Figure 13.20

Different types of transformers: (a) copper wound dry power transformer, (b) audio transformers.
 Courtesy of: (a) Electric Service Co., (b) Jensen Transformers.

$$Z_{in} = \frac{V}{I_1} = R_1 + j\omega L_1 + \frac{\omega^2 M^2}{R_2 + j\omega L_2 + Z_L} \quad Z_R = \frac{\omega^2 M^2}{R_2 + j\omega L_2 + Z_L}$$

(no dot rule)
reflected impedance or coupled ~

Example 13.4

In the circuit of Fig. 13.24, calculate the input impedance and current I_1 . Take $Z_1 = 60 - j100 \Omega$, $Z_2 = 30 + j40 \Omega$, and $Z_L = 80 + j60 \Omega$.

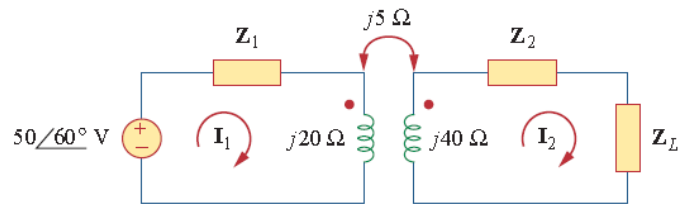


Figure 13.24

For Example 13.4.

Solution:

From Eq. (13.41),

$$\begin{aligned} Z_{in} &= Z_1 + j20 + \frac{(5)^2}{j40 + Z_2 + Z_L} \\ &= 60 - j100 + j20 + \frac{25}{110 + j140} \\ &= 60 - j80 + 0.14 \angle -51.84^\circ \\ &= 60.09 - j80.11 = 100.14 \angle -53.1^\circ \Omega \end{aligned}$$

Thus,

$$I_1 = \frac{V}{Z_{in}} = \frac{50 \angle 60^\circ}{100.14 \angle -53.1^\circ} = 0.5 \angle 113.1^\circ \text{ A}$$

* Convert the linear transformer into T or Π equivalent circuit:

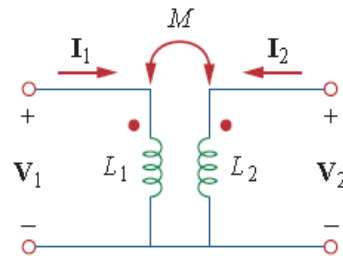


Figure 13.21

Determining the equivalent circuit of a linear transformer.

T-Model

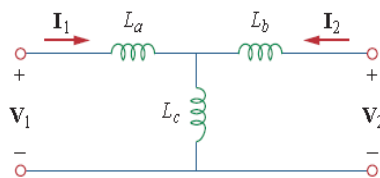


Figure 13.22

An equivalent T circuit.

Π -Model

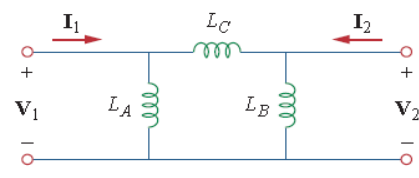


Figure 13.23

An equivalent Π circuit.

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} \frac{L_2}{j\omega(L_1L_2 - M^2)} & \frac{-M}{j\omega(L_1L_2 - M^2)} \\ \frac{-M}{j\omega(L_1L_2 - M^2)} & \frac{L_1}{j\omega(L_1L_2 - M^2)} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} \frac{1}{j\omega L_A} + \frac{1}{j\omega L_C} & \frac{-1}{j\omega L_C} \\ -\frac{1}{j\omega L_C} & \frac{1}{j\omega L_B} + \frac{1}{j\omega L_C} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} j\omega(L_a + L_c) & j\omega L_c \\ j\omega L_c & j\omega(L_b + L_c) \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$L_A = \frac{L_1L_2 - M^2}{L_2 - M}, \quad L_B = \frac{L_1L_2 - M^2}{L_1 - M}$$

$$L_C = \frac{L_1L_2 - M^2}{M}$$

$$L_a = L_1 - M, \quad L_b = L_2 - M, \quad L_c = M$$

Example 13.6

Solve for I_1 , I_2 , and V_o in Fig. 13.27 (the same circuit as for Practice Prob. 13.1) using the T-equivalent circuit for the linear transformer.

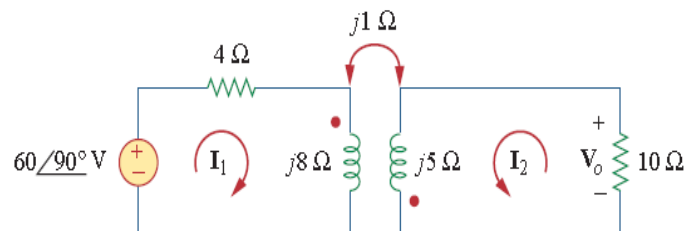



Figure 13.27

For Example 13.6.

Solution:

$$L_a = L_1 - (-M) = 8 + 1 = 9 \text{ H}$$
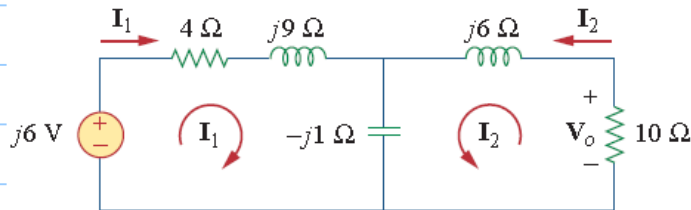
$$L_b = L_2 - (-M) = 5 + 1 = 6 \text{ H}, \quad L_c = -M = -1 \text{ H}$$



$$j6 = I_1(4 + j9 - j1) + I_2(-j1) \quad (13.6.1)$$

and

$$0 = I_1(-j1) + I_2(10 + j6 - j1) \quad (13.6.2)$$

From Eq. (13.6.2),

$$I_1 = \frac{(10 + j5)}{j} I_2 = (5 - j10)I_2 \quad (13.6.3)$$

Substituting Eq. (13.6.3) into Eq. (13.6.1) gives

$$j6 = (4 + j8)(5 - j10)I_2 - jI_2 = (100 - j)I_2 \approx 100I_2$$

Since 100 is very large compared with 1, the imaginary part of $(100 - j)$ can be ignored so that $100 - j \approx 100$. Hence,

$$I_2 = \frac{j6}{100} = j0.06 = 0.06 \angle 90^\circ \text{ A}$$

From Eq. (13.6.3),

$$I_1 = (5 - j10)j0.06 = 0.6 + j0.3 \text{ A}$$

and

$$V_o = -10I_2 = -j0.6 = 0.6 \angle -90^\circ \text{ V}$$

13.5 Ideal Transformers:

An **ideal transformer** is a unity-coupled, lossless transformer in which the primary and secondary coils have infinite self-inductances.

1. Coils have very large reactances ($L_1, L_2, M \rightarrow \infty$).
2. Coupling coefficient is equal to unity ($k = 1$).
3. Primary and secondary coils are lossless ($R_1 = 0 = R_2$).

Turns ratio: (Transformation ratio)

$$\frac{V_2}{V_1} = \frac{N_2}{N_1} = n$$

$$\frac{I_2}{I_1} = \frac{N_1}{N_2} = \frac{1}{n}$$

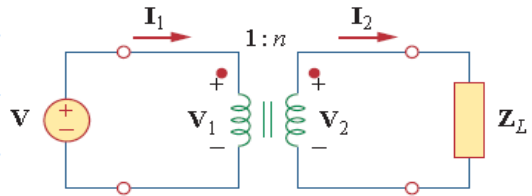



Figure 13.31
Relating primary and secondary quantities in an ideal transformer.

A **step-down transformer** is one whose secondary voltage is less than its primary voltage.

A **step-up transformer** is one whose secondary voltage is greater than its primary voltage.

* Dot Rule:

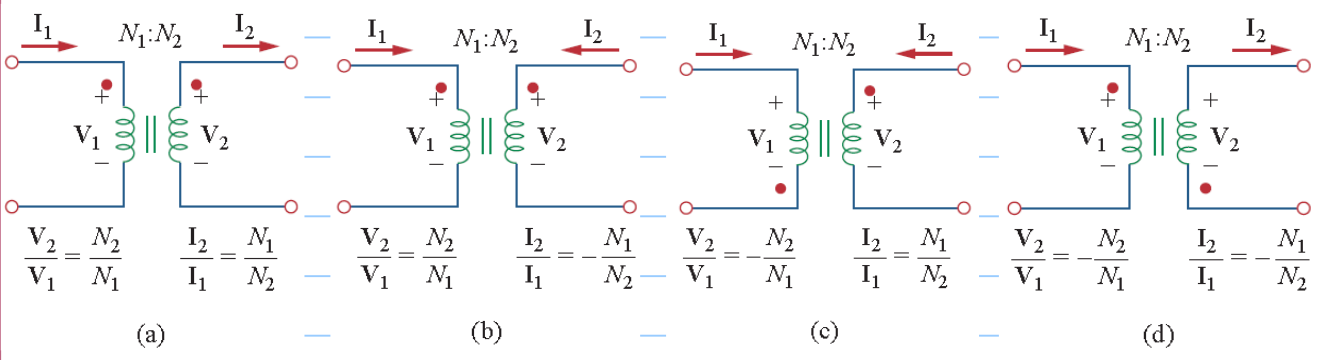1. If V_1 and V_2 are both positive or both negative at the dotted terminals, use $+n$ in Eq. (13.52). Otherwise, use $-n$.
2. If I_1 and I_2 both enter into or both leave the dotted terminals, use $-n$ in Eq. (13.55). Otherwise, use $+n$.



* The Complex Power:

$$S_1 = V_1 I_1^* = \frac{V_2}{n} (n I_2)^* = V_2 I_2^* = S_2$$

* The Input Impedance: (Reflected Impedance)

$$Z_{in} = \frac{V_1}{I_1} = \frac{1}{n^2} \frac{V_2}{I_2} \quad \text{or} \quad Z_{in} = \frac{Z_L}{n^2}$$

* Equivalent Circuit:


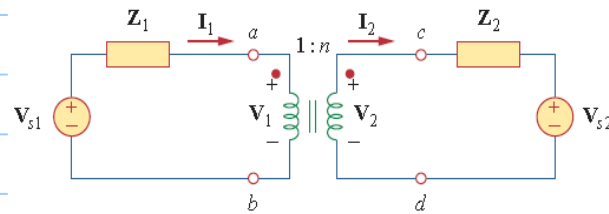


Figure 13.33

Ideal transformer circuit whose equivalent circuits are to be found.

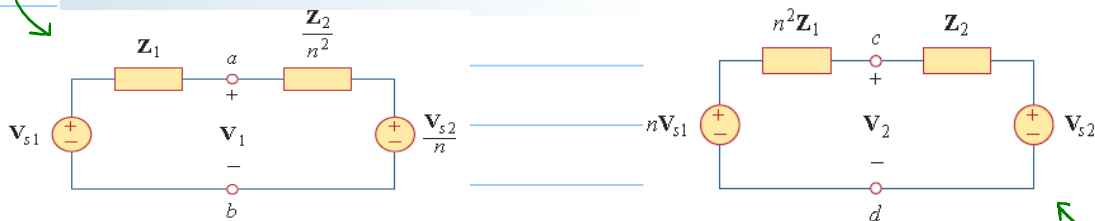The general rule for eliminating the transformer and reflecting the secondary circuit to the primary side is: divide the secondary impedance by n^2 , divide the secondary voltage by n , and multiply the secondary current by n .



The rule for eliminating the transformer and reflecting the primary circuit to the secondary side is: multiply the primary impedance by n^2 , multiply the primary voltage by n , and divide the primary current by n .

Example 13.8

For the ideal transformer circuit of Fig. 13.37, find: (a) the source current I_1 , (b) the output voltage V_o , and (c) the complex power supplied by the source.

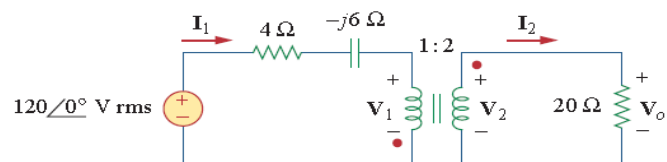


Figure 13.37

For Example 13.8.

Solution:

(a) The $20\text{-}\Omega$ impedance can be reflected to the primary side and we get

$$Z_R = \frac{20}{n^2} = \frac{20}{4} = 5\ \Omega$$

Thus,

$$Z_{in} = 4 - j6 + Z_R = 9 - j6 = 10.82\angle-33.69^\circ\ \Omega$$

$$I_1 = \frac{120\angle 0^\circ}{Z_{in}} = \frac{120\angle 0^\circ}{10.82\angle-33.69^\circ} = 11.09\angle 33.69^\circ\ \text{A}$$

(b) Since both I_1 and I_2 leave the dotted terminals,

$$I_2 = -\frac{1}{n}I_1 = -5.545\angle 33.69^\circ\ \text{A}$$

$$V_o = 20I_2 = 110.9\angle 213.69^\circ\ \text{V}$$

(c) The complex power supplied is

$$S = V_s I_1^* = (120\angle 0^\circ)(11.09\angle-33.69^\circ) = 1,330.8\angle-33.69^\circ\ \text{VA}$$